

# **CH-3: Working With Combinational Logic**

*Contemporary Logic Design*

YONSEI UNIVERSITY


Fall 2016

# Working with Combinational Logic

---

- Simplification
  - ◆ two-level simplification
  - ◆ exploiting don't cares
  - ◆ algorithm for simplification
- Logic realization
  - ◆ two-level logic and canonical forms realized with NANDs and NORs
  - ◆ multi-level logic, converting between ANDs and ORs
- Time behavior
- Hardware description languages (HDL)

# Design Example: Two-bit Comparator

 

Block diagram  
and  
truth table

A	B	C	D	LT	EQ	GT
0	0	0	0	0	1	0
		0	1	1	0	0
		1	0	1	0	0
		1	1	1	0	0
0	1	0	0	0	0	1
		0	1	0	1	0
		1	0	1	0	0
		1	1	1	0	0
1	0	0	0	0	0	1
		0	1	0	0	1
		1	0	0	1	0
		1	1	1	0	0
1	1	0	0	0	0	1
		0	1	0	0	1
		1	0	0	0	1
		1	1	0	1	0

we'll need a 4-variable Karnaugh map  
for each of the 3 output functions

# Design Example: Two-bit Comparator

AB		A			
		00	01	11	10
CD	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0
		B		D	

K-map for LT

AB		A			
		00	01	11	10
CD	00	1	0	0	0
	01	0	1	0	0
	11	0	0	1	0
	10	0	0	0	1
		B			D

K-map for EQ

		AB				A	D
		00	01	11	10		
CD	00	0	1	1	1	C	
	01	0	0	1	1		
	11	0	0	0	0		
	10	0	0	1	0		
		B					

K-map for GT


$$LT = A' B' D + A' C + B' C D$$

$$EQ = A' B' C' D' + A' B C' D + A B C D + A B' C D' = (A \text{ xnor } C) \cdot (B \text{ xnor } D)$$


$$GT = B C' D' + A C' + A B D'$$

LT and GT are similar (flip A/C and B/D)

# Design Example: Two-bit Comparator

 


 two alternative  
implementations of EQ  
with and without XOR



XNOR is implemented with  
at least 3 simple gates

# Design Example: 2x2-bit Multiplier

 


Block diagram  
and  
truth table



A2	A1	B2	B1	P8	P4	P2	P1
0	0	0	0	0	0	0	0
		0	1	0	0	0	0
		1	0	0	0	0	0
		1	1	0	0	0	0
0	1	0	0	0	0	0	0
		0	1	0	0	0	1
		1	0	0	0	1	0
		1	1	0	0	1	1
1	0	0	0	0	0	0	0
		0	1	0	0	1	0
		1	0	0	1	0	0
		1	1	0	1	1	0
1	1	0	0	0	0	0	0
		0	1	0	0	1	1
		1	0	0	1	1	0
		1	1	1	0	0	1

4-variable K-map  
for each of the 4  
output functions


# Design Example: 2x2-bit Multiplier

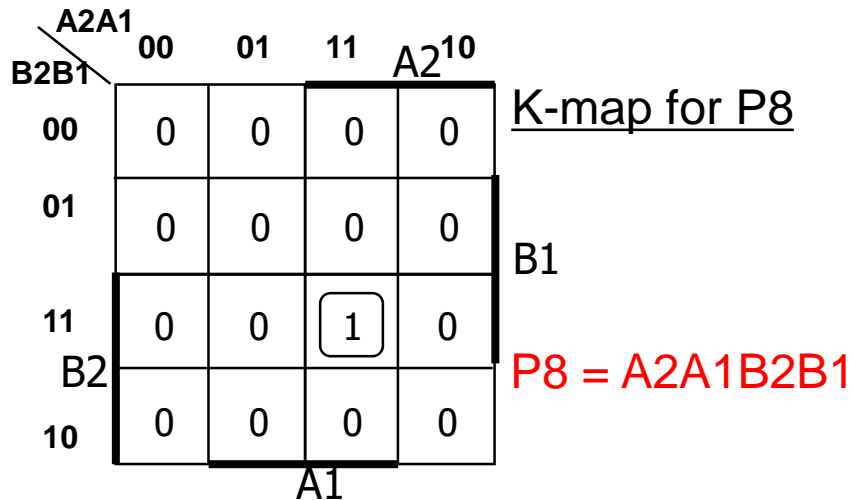


K-map for P4

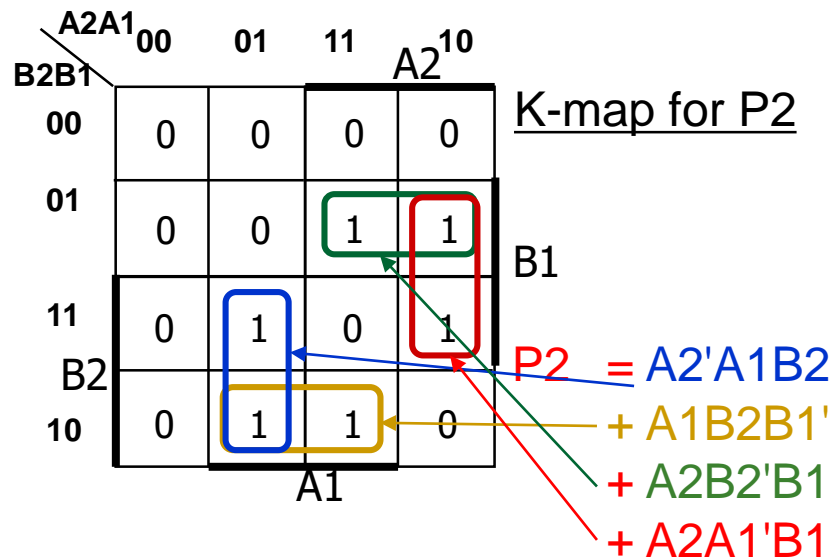 

K-map for P1

 

# Design Example: BCD Increment by 1

 

Block diagram  
and  
truth table

I8	I4	I2	I1	O8	O4	O2	O1
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

4-variable K-map for each of  
the 4 output functions



# Design Example: BCD Increment by 1

	00	01	11	$I_8^{10}$
00	0	0	X	1
01	0	0	X	0
11	0	1	X	X
$I_2^{10}$	0	0	X	X

$I_4$

$$O_8 = I_4 I_2 I_1 + I_8 I_1'$$

$$O_4 = I_4 I_2' + I_4 I_1' + I_4' I_2 I_1$$

$$O_2 = I_8' I_2' I_1 + I_2 I_1'$$

$$O_1 = I_1'$$

	00	01	11	$I_8^{10}$
00	0	0	X	0
01	1	1	X	0
11	0	0	X	X
$I_2^{10}$	1	1	X	X

$I_4$

	00	01	11	$I_8^{10}$
00	0	1	X	0
01	0	1	X	0
11	1	0	X	X
$I_2^{10}$	0	1	X	X

$I_4$

	00	01	11	$I_8^{10}$
00	1	1	X	1
01	0	0	X	0
11	0	0	X	X
$I_2^{10}$	1	1	X	X

$I_4$

# Defining Terms for 2-level Simplification

- *Implicant*
  - ◆ single element of ON-set or DC-set or any group of these elements that can be combined to form a subcube
- *Prime implicant*
  - ◆ implicant that can't be combined with another to form a larger subcube
- *Essential prime implicant*
  - ◆ prime implicant is *essential* if it alone covers an element of ON-set
  - ◆ will participate in ALL possible covers of the ON-set
  - ◆ DC-set used to form prime implicants but not to make implicant essential
- Objective:
  - ◆ grow implicant into prime implicants (minimize literals per term)
  - ◆ cover the ON-set with as few prime implicants as possible (minimize number of product terms)

# Examples to Illustrate Terms

AB \ CD	00	01	11	10
00	0	X	1	0
01	1	1	1	0
11	1	0	1	1
10	0	0	1	1

6 prime implicants:

$A'B'D$ ,  $BC'$ ,  $AC$ ,  $A'C'D$ ,  $AB$ ,  $B'CD$

essential

minimum cover:  $AC + BC' + A'B'D$

5 prime implicants:

$BD$ ,  $ABC'$ ,  $ACD$ ,  $A'BC$ ,  $A'C'D$

essential

minimum cover: 4 essential implicants

AB \ CD	00	01	11	10
00	0	0	1	0
01	1	1	1	0
11	0	1	1	1
10	0	1	0	0

# Algorithm for Two-level Simplification

- Algorithm: minimum sum-of-products expression from a Karnaugh map
  - ◆ Step 1: choose an element of the ON-set
  - ◆ Step 2: find "maximal" groupings of 1s and Xs adjacent to that element
    - consider top/bottom row, left/right column, and corner adjacencies
    - this forms prime implicants (number of elements always a power of 2)
  - ◆ Repeat Steps 1 and 2 to find all prime implicants
  - ◆ Step 3: revisit the 1s in the K-map
    - if covered by single prime implicant, it is essential, and participates in final cover
    - 1s covered by essential prime implicant do not need to be revisited
  - ◆ Step 4: if there remain 1s not covered by essential prime implicants
    - select the smallest number of prime implicants that cover the remaining 1s

# Algorithm for 2-level Simplification: EX

		A		
	X	1	0	1
	0	1	1	1
	0	X	X	0
C	0	1	0	1
		B		

		A		
	X	1	0	1
	0	1	1	1
	0	X	X	0
C	0	1	0	1
		B		

2 primes around  $A'BC'D'$

		A		
	X	1	0	1
	0	1	1	1
	0	X	X	0
C	0	1	0	1
		B		

2 primes around  $ABC'D$

		A		
	X	1	0	1
	0	1	1	1
	0	X	X	0
C	0	1	0	1
		B		

3 primes around  $AB'C'D'$

		A		
	X	1	0	1
	0	1	1	1
	0	X	X	0
C	0	1	0	1
		B		

2 essential primes

		A		
	X	1	0	1
	0	1	1	1
	0	X	X	0
C	0	1	0	1
		B		

minimum cover (3 primes)

# Activity

- List all prime implicants for the following K-map:

			A	
	X	0	X	0
	0	1	X	1
	0	X	X	0
C	X	1	1	1
		B		

- Which are essential prime implicants?
- What is the minimum cover?

# 5 Variable K-Map

## 5-Variable K-maps

		BC			
		DE	00	01	11
A=0	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10
		BC			
		DE	00	01	11
A=1	00	16	20	28	24
	01	17	21	29	25
	11	19	23	31	27
	10	18	22	30	26

		BC				
		DE	00	01	11	10
A=0	00					1
	01		1		1	
	11		1		1	
	10	1				1



		BC				
		DE	00	01	11	10
A=1	00					1
	01	1	1	1		
	11	1	1	1		
	10					

$$F(A,B,C,D,E) = \sum m(2,5,7,8,10, 13,15,17,19,21,23,24,29,31)$$

=

# 5 Variable K-Map

## 5-Variable K-maps

  

$$F(A,B,C,D,E) = \sum m(2,5,7,8,10, 13,15,17,19,21,23,24,29,31)$$

$$= CE + AB'E + BC'D'E' + A'C'DE'$$



# 6 Variable K-Map


		CD			
		00	01	11	10
AB=00	EF=00	0	4	12	8
	EF=01	1	5	13	9
	EF=11	3	7	15	11
	EF=10	2	6	14	10
AB=01	EF=00	16	20	28	24
	EF=01	17	21	29	25
	EF=11	19	23	31	27
	EF=10	18	22	30	26
AB=11	EF=00	48	52	60	56
	EF=01	49	53	61	57
	EF=11	51	55	63	59
	EF=10	50	54	62	58
AB=10	EF=00	32	36	44	40
	EF=01	33	37	45	41
	EF=11	35	39	47	43
	EF=10	34	38	46	42

## 6- Variable K-Maps

$$F(A,B,C,D,E,F) = \Sigma m(2,8,10,18,24, 26,34,37,42,45,50, 53,58,61)$$

=


# 6 Variable K-Map

 

## 6- Variable K-Maps

$$F(A,B,C,D,E,F) = \Sigma m(2,8,10,18,24, 26,34,37,42,45,50, 53,58,61)$$

$$= D' E F' + A D E' F + A' C D' F'$$

 

# Gate Logic: CAD Tools for Simplification

## *Quine-McCluskey Method*

Tabular method to systematically find all prime implicants

$$F(A,B,C,D) = \Sigma m(4,5,6,8,9,10,13) + \Sigma d(0,7,15)$$

Stage 1: Find all prime implicants

**Step 1:** Fill Column 1 with ON-set and DC-set minterm indices. Group by number of 1's.

Implication Table	
Column 1	
0000	
0100	
1000	
0101	
0110	
1001	
1010	
0111	
1101	
1111	

# Gate Logic: CAD Tools for Simplification

## Quine-McCluskey Method

$$F(A,B,C,D) = \Sigma m(4,5,6,8,9,10,13) + \Sigma d(0,7,15)$$

Stage 1: Find all prime implicants

Step 1: Fill Column 1 with ON-set and DC-set minterm indices. Group by number of 1's.

### Step 2: Apply Uniting Theorem

Compare elements of group w/ N 1's against those with N+1 1's. Differ by one bit implies adjacent. Eliminate variable and place in next column.

E.g., 0000 vs. 0100 yields 0-00  
0000 vs. 1000 yields -000

When used in a combination, mark with a check. If cannot be combined, mark with a star. These are the prime implicants.

Repeat until no further combinations can be made.

Implication Table		
Column I	Column II	
0000 ✓	0-00 -000	
0100 ✓ 1000 ✓	010- 01-0	
0101 ✓ 0110 ✓ 1001 ✓ 1010 ✓	100- 10-0  01-1 -101	
0111 ✓ 1101 ✓	011- 1-01	
1111 ✓	-111 11-1	

# Gate Logic: CAD Tools for Simplification

## Quine-McCluskey Method

$$F(A,B,C,D) = \Sigma m(4,5,6,8,9,10,13) + \Sigma d(0,7,15)$$

**Stage 1: Find all prime implicants**

**Step 1: Fill Column 1 with ON-set and DC-set minterm indices. Group by number of 1's.**

**Step 2: Apply Uniting Theorem**  
Compare elements of group w/ N 1's against those with N+1 1's.  
Differ by one bit implies adjacent.  
Eliminate variable and place in next column.

E.g., 0000 vs. 0100 yields 0-00  
0000 vs. 1000 yields -000

When used in a combination, mark with a check. If cannot be combined, mark with a star. These are the prime implicants.

**Repeat until no further combinations can be made.**

Implication Table		
Column I	Column II	Column III
0000 ✓	0-00 *	01-- *
	-000 *	
0100 ✓		-1-1 *
1000 ✓	010- ✓	
	01-0 ✓	
0101 ✓	100- *	
0110 ✓	10-0 *	
1001 ✓		
1010 ✓	01-1 ✓	
	-101 ✓	
0111 ✓	011- ✓	
1101 ✓	1-01 *	
1111 ✓	-111 ✓	
	11-1 ✓	

# Gate Logic: CAD Tools for Simplification

## Quine-McCluskey Method Continued

AB \ CD		A			
		00	01	11	10
C	00	X	1	0	1
	01	0	1	1	1
	11	0	X	X	0
	10	0	1	0	1

### Prime Implicants:

$$0-00 = A' C' D'$$

$$100- = A B' C'$$

$$1-01 = A C' D$$

$$-1-1 = B D$$

$$-000 = B' C' D'$$

$$10-0 = A B' D'$$

$$01-- = A' B$$

# Gate Logic: CAD Tools for Simplification

## Quine-McCluskey Method Continued

AB CD		A			
		00	01	11	10
C	00	X	1	0	1
	01	0	1	1	1
	11	0	X	X	0
	10	0	1	0	1
		B			

Prime Implicants:

$$0-00 = A' C' D'$$

$$-000 = B' C' D'$$

$$100- = A B' C'$$

$$10-0 = A B' D'$$

$$1-01 = A C' D$$

$$01-- = A' B$$

$$-1-1 = B D$$

**Stage 2:** find smallest set of prime implicants that cover the ON-set  
recall that essential prime implicants must be in all covers  
another tabular method? the prime implicant chart

# Gate Logic: CAD Tools for Simplification

*Prime Implicant Chart*

	4	5	6	8	9	10	13
0,4(0_00)	x						
0,8(_000)				x			
8,9(100_)				x	x		
8,10(10_0)				x		x	
9,13(1_01)					x		x
4,5,6,7(01__)	x	x	x				
5,7,13,16(_1_1)		x					x

**rows = prime implicants**  
**columns = ON-set elements**  
**place an "X" if ON-set element is**  
**covered by the prime implicant**



# Gate Logic: CAD Tools for Simplification

*Prime Implicant Chart*

	4	5	6	8	9	10	13
0,4(0_00)	X						
0,8(_000)				X			
8,9(100_)				X	X		
8,10(10_0)				X		X	
9,13(1_01)					X		X
4,5,6,7(01_ _)	X	X	X				
5,7,13,16(_1_1)		X					X


	4	5	6	8	9	10	13
0,4(0_00)	X						
0,8(_000)				X			
8,9(100_)				X	X		
8,10(10_0)				X		X	
9,13(1_01)					X		X
4,5,6,7(01_ _)	X	X	X				
5,7,13,16(_1_1)		X					X

rows = prime implicants  
columns = ON-set elements  
place an "X" if ON-set element is covered by the prime implicant

If column has a single X, then the implicant associated with the row is essential. It must appear in minimum cover

# Gate Logic: CAD Tools for Simplification


*Prime Implicant Chart (Continued)*

 


**Eliminate all columns covered by essential primes**

# Gate Logic: CAD Tools for Simplification

*Prime Implicant Chart (Continued)*

 

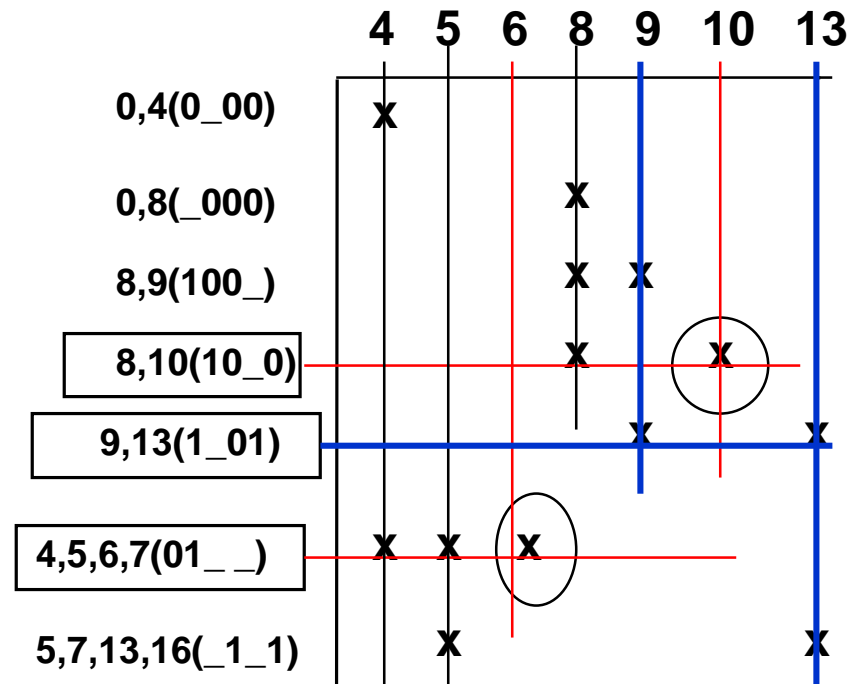**Eliminate all columns covered by essential primes**




**Find minimum set of rows that cover the remaining columns**

$$F = A B' D' + A C' D + A' B$$
 
# Implementations of Two-level Logic


- Sum-of-products

- ◆ AND gates to form product terms (minterms)
- ◆ OR gate to form sum





- Product-of-sums

 - ◆ OR gates to form sum terms (maxterms)
- ◆ AND gates to form product



  
# Two-level Logic using NAND Gates

- Replace minterm AND gates with NAND gates
- Place compensating inversion at inputs of OR gate




 
# Two-level Logic using NAND Gates

- OR gate with inverted inputs is a NAND gate
  - ◆ de Morgan's:  $A' + B' = (A \cdot B)'$
- Two-level NAND-NAND network
  - ◆ inverted inputs are not counted
  - ◆ in a typical circuit, inversion is done once and signal distributed




 
 
# Two-level Logic using NOR Gates

- Replace maxterm OR gates with NOR gates
- Place compensating inversion at inputs of AND gate


   
# Two-level Logic using NOR Gates

- AND gate with inverted inputs is a NOR gate
  - ◆ de Morgan's:  $A' \cdot B' = (A + B)'$
- Two-level NOR-NOR network
  - ◆ inverted inputs are not counted
  - ◆ in a typical circuit, inversion is done once and signal distributed







# Two-level Logic using NAND/NOR Gates

- NAND-NAND and NOR-NOR networks

- ◆ de Morgan's law:  $(A + B)' = A' \cdot B'$        $(A \cdot B)' = A' + B'$
- ◆ written differently:  $A + B = (A' \cdot B')'$        $(A \cdot B) = (A' + B')'$



- In other words —

  - ◆ OR is the same as NAND with complemented inputs
- ◆ AND is the same as NOR with complemented inputs
- ◆ NAND is the same as OR with complemented inputs
- ◆ NOR is the same as AND with complemented inputs



 
 
# Conversion Between Forms

- Convert from networks of ANDs and ORs to networks of NANDs and NORs
  - ◆ introduce appropriate inversions ("bubbles")
- Each introduced "bubble" must be *matched* by a corresponding "bubble"
  - ◆ conservation of inversions
  - ◆ do not alter logic function
- Example: AND/OR to NAND/NAND



# Conversion Between Forms

 
 
- Example: verify equivalence of two forms



$$\begin{aligned} Z &= [ (A \cdot B)' \cdot (C \cdot D)' ]' \\ &= [ (A' + B') \cdot (C' + D') ]' \\ &= [ (A' + B')' + (C' + D')' ] \\ &= (A \cdot B) + (C \cdot D) \quad \checkmark \end{aligned}$$


# Conversion Between Forms

  - Example: map AND/OR network to NOR/NOR network



Step 1

conserve  
"bubbles"


 


Step 2

conserve  
"bubbles"

# Conversion Between Forms

  
- Example: verify equivalence of two forms



$$\begin{aligned} Z &= \{ [(A' + B')' + (C' + D')'] \}' \\ &= \{ (A' + B') \cdot (C' + D') \}' \\ &= (A' + B')' + (C' + D')' \\ &= (A \cdot B) + (C \cdot D) \quad \checkmark \end{aligned}$$

 
# Multi-level Logic

- $x = A D F + A E F + B D F + B E F + C D F + C E F + G$   
 $G = [(A+B+C)D + (A+B+C)E]F + G = (A+B+C)(D+E)F + G$ 
  - ◆ 6 x 3-input AND gates + 1 x 7-input OR gate (that may not even exist!)
  - ◆ 25 wires (19 literals plus 6 internal wires)


 
# Multi-level Logic

- $x = A D F + A E F + B D F + B E F + C D F + C E F + G$   
 $G = [(A+B+C)D + (A+B+C)E]F + G = (A+B+C)(D+E)F + G$
- $x = (A + B + C) (D + E) F + G$ 
  - ◆ factored form – not written as two-level S-o-P
  - ◆ 1 x 3-input OR gate, 2 x 2-input OR gates, 1 x 3-input AND gate
  - ◆ 10 wires (7 literals plus 3 internal wires)




# Multi-level Logic to NAND Gates

- $F = A(B + CD) + BC'$

original  
AND-OR  
network

introduction and  
conservation of  
bubbles

 
redrawn in terms  
of conventional  
NAND gates






# Conversion of Multi-level Logic to NORs

■  $F = A(B + CD) + BC'$

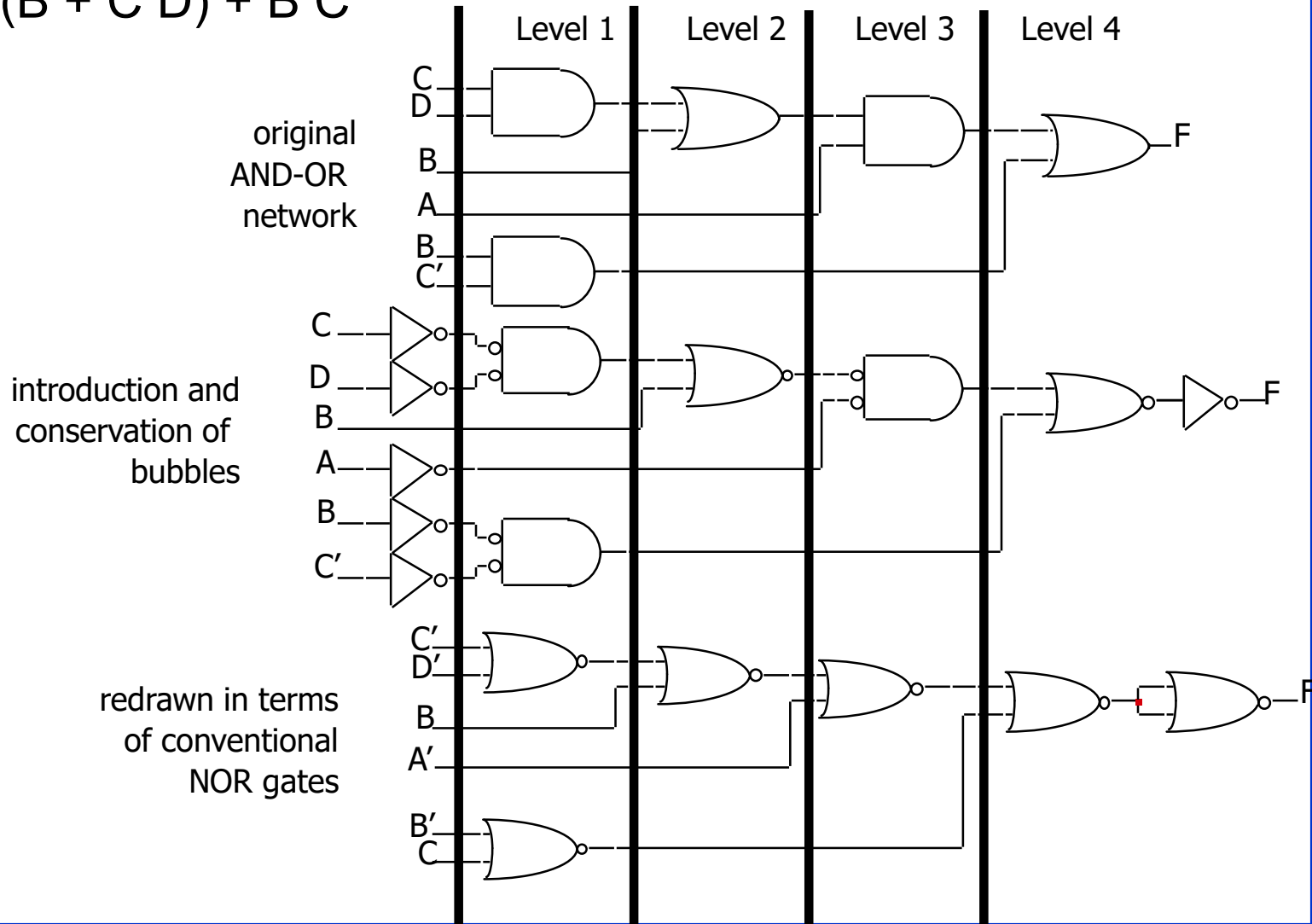


# Conversion Between Forms


## ■ Example

 


original circuit

 

 add double bubbles to  
invert all inputs of OR gate



 add double bubble to  
invert output of AND gate




insert inverters to eliminate  
double bubbles on a wire


# AND-OR-invert Gates

- AOI function: three stages of logic — AND, OR, Invert
  - ◆ multiple gates "packaged" as a single circuit block


logical concept

 


possible implementation

 

2x2 AOI gate symbol

 


3x2 AOI gate symbol

 
 
# Conversion to AOI Forms

- General procedure to place in AOI form
  - ◆ compute the *complement* of the function in sum-of-products form
  - ◆ by grouping the 0s in the Karnaugh map
- Example: XOR implementation
  - ◆  $F = A \text{ xor } B = A' B + A B'$ ,  $F' = \text{XNOR} = A' B' + AB$
  - ◆ AOI form:
    - $F = (A' B' + A B)'$



# Examples of using AOI Gates

## ■ Example:

- ◆  $F' = A' B' + A' C + B' C$
- ◆  $F = (A' B' + A' C + B' C)'$
- ◆ Implemented by 2-input 3-stack AOI gate

- ◆  $F' = (A' + B') (A' + C) (B' + C)$
- ◆  $F = [(A' + B') (A' + C) (B' + C)]'$
- ◆ Implemented by 2-input 3-stack OAI gate


## ■ Example: 4-bit equality function

- ◆  $Z = (A_0 B_0 + A_0' B_0')(A_1 B_1 + A_1' B_1')(A_2 B_2 + A_2' B_2')(A_3 B_3 + A_3' B_3')$

each implemented in a single 2x2 AOI gate

# Examples of using AOI Gates

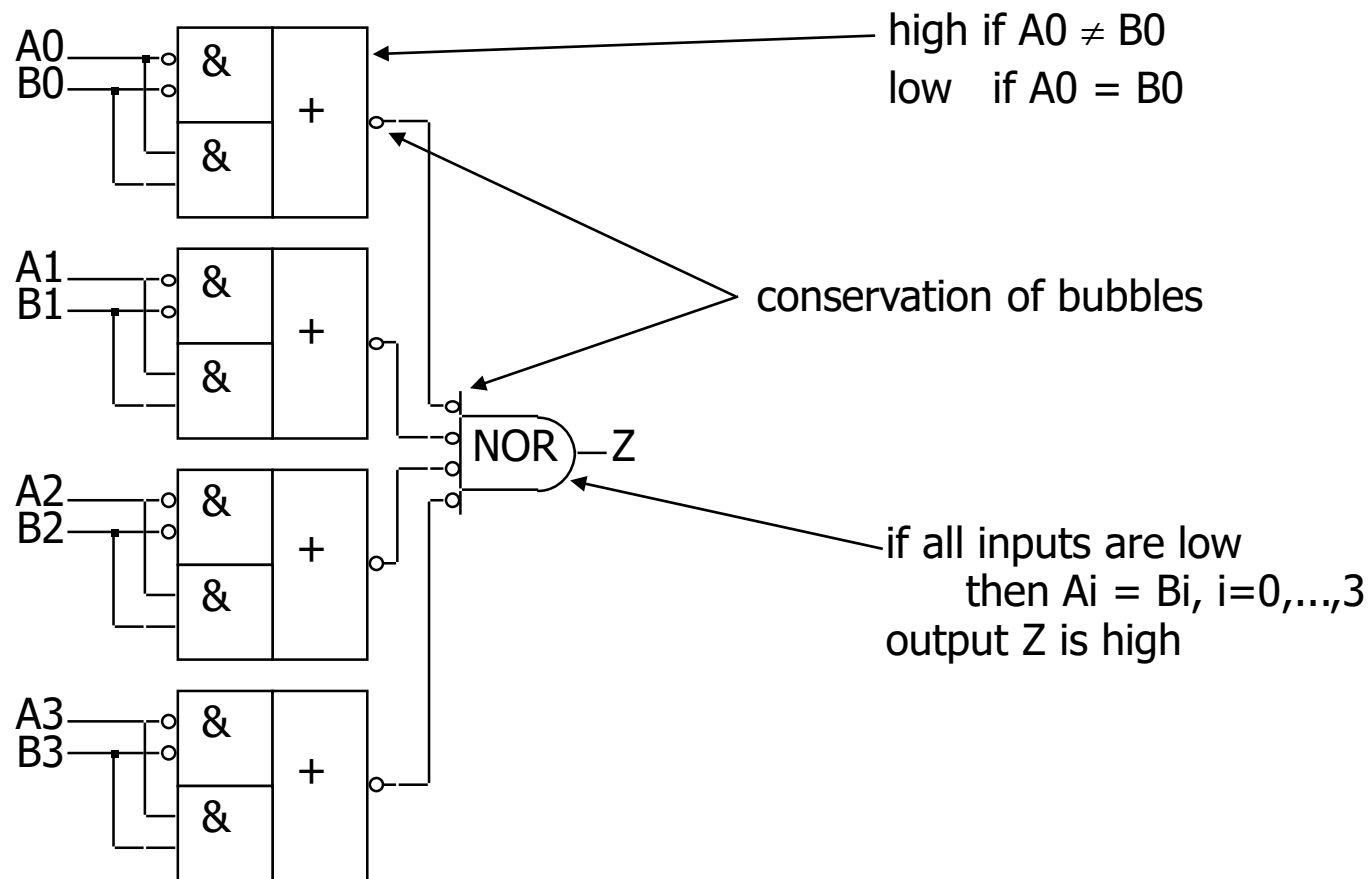- Example: AOI implementation of 4-bit equality function



# Summary for Multi-level Logic

---

- Advantages

- ◆ circuits may be smaller
- ◆ gates have smaller fan-in
- ◆ circuits may be faster

- Disadvantages

- ◆ more difficult to design
- ◆ tools for optimization are not as good as for two-level
- ◆ analysis is more complex

# Time Behavior of Comb-Networks



---

- Waveforms
  - ◆ visualization of values carried on signal wires over time
  - ◆ useful in explaining sequences of events (changes in value)
- Simulation tools are used to create these waveforms
  - ◆ input to the simulator includes gates and their connections
  - ◆ input stimulus, that is, input signal waveforms
- Some terms
  - ◆ gate delay — time for change at input to cause change at output
    - min delay – typical/nominal delay – max delay
    - careful designers design for the worst case
  - ◆ rise time — time for output to transition from low to high voltage
  - ◆ fall time — time for output to transition from high to low voltage
  - ◆ pulse width — time that an output stays high or stays low between changes



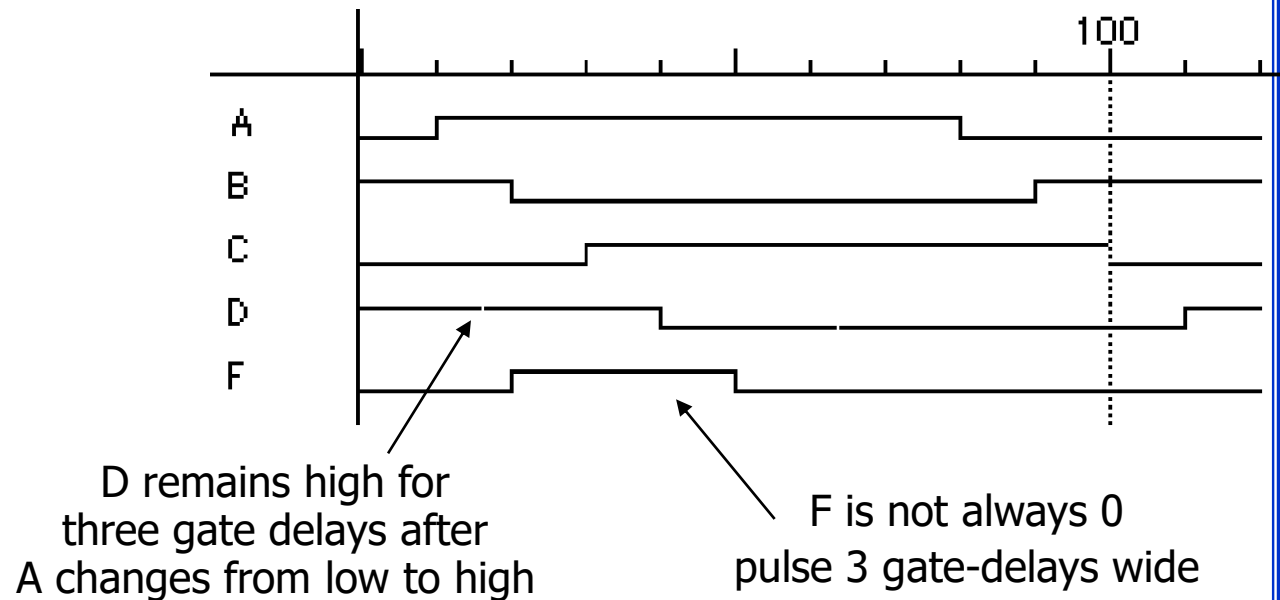
 
# Momentary Changes in Outputs

- Can be useful — pulse shaping circuits
- Can be a problem — incorrect circuit operation (glitches/hazards)
- Example: pulse shaping circuit
  - ◆  $A' \cdot A = 0$
  - ◆ delays matter



# Oscillatory Behavior

- Another pulse shaping circuit

  


# Hazards/Glitches and How to Avoid Them


---

- Unwanting switching at the outputs
- Occur because
  - ◆ delay paths through the circuit experience
  - ◆ different propagation delays
- Danger if logic "makes a decision" while output is unstable  
*asynchronous* input :these respond immediately to changes rather than waiting for a synchronizing signal called a *clock*)
- Solutions
  - ◆ wait until signals are stable (by using a clock)
  - ◆ never use circuits with asynchronous inputs
  - ◆ design hazard-free circuits


# Hazards/Glitches and How to Avoid Them

 

 
Input change causes output to go from 1 to 0 to 1



 Input change causes output to go from 0 to 1 to 0



 Input change causes a double change  
from 0 to 1 to 0 to 1 OR  
from 1 to 0 to 1 to 0





Kinds of Hazards


**Assumption:** the unexpected changes in the outputs are in response to single-bit changes in the inputs

# Hazards/Glitches and How to Avoid Them

## Glitch Example

 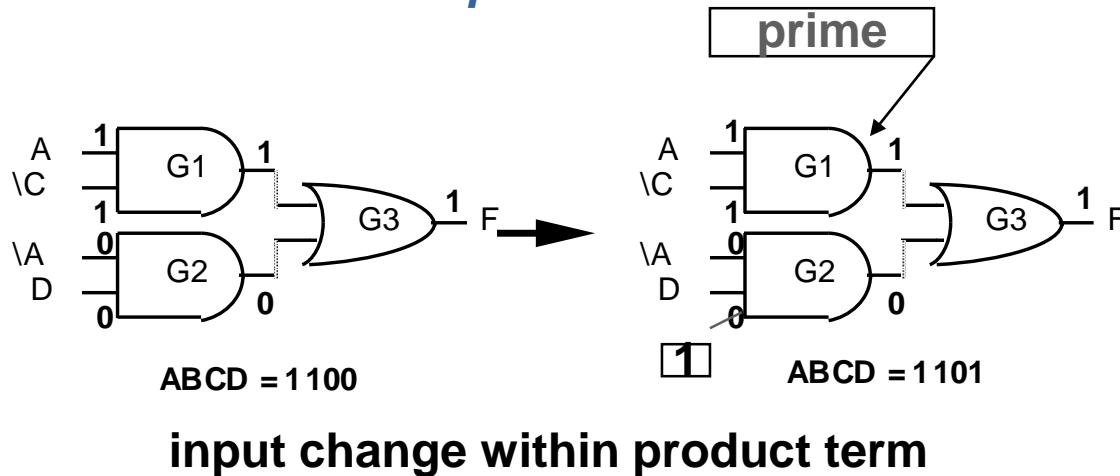

## Gate delay

 

## Static 1-hazard


# Hazards/Glitches and How to Avoid Them

- Static 1-hazard : occurs in sum of products form.
- Solution

General Strategy: *add redundant terms*

$F = A' D + A C'$  becomes  $A' D + A C' + C' D$

 $ABCD=1101 \rightarrow 0101, C'D=1 \quad F=1$



# Hazards/Glitches and How to Avoid Them

- How about 0-hazard? Occurs in POS form

Re-express F in PoS form:

$$F' = AC + A'D'$$


$$F = (A' + C')(A + D)$$

Glitch present!: 0110 to 1110

Add term:  $(C' + D)$

This expression is equivalent to the hazard-free SoP form of F

 All single-bit input changes should be covered by one implicant



# Hazards/Glitches and How to Avoid Them

---

- Start with expression that is free of static 1-hazards

$$F = A C' + A' D + C' D$$

Work with complement:

$$F' = (A C' + A' D + C' D)'$$

$$= (A' + C) (A + D') (C + D')$$

$$= A C + A C D' + C D' + A' C D' + A' D'$$

$$= A C + C D' + A' D'$$

*covers all the adjacent 0's in the K-map*

**free of static-1 and static-0 hazards!**



# Hardware Description Languages (HDL)

---

- Describe hardware at varying levels of abstraction
- Structural description
  - ◆ textual replacement for schematic
  - ◆ hierarchical composition of modules from primitives
- Behavioral/functional description
  - ◆ describe what module does, not how
  - ◆ synthesis generates circuit for module
- Simulation semantics

# HDLs

---

- Abel (circa 1983) - developed by Data-I/O
  - ◆ targeted to programmable logic devices
  - ◆ not good for much more than state machines
- ISP (circa 1977) - research project at CMU
  - ◆ simulation, but no synthesis
- Verilog (circa 1985) - developed by Gateway (absorbed by Cadence)
  - ◆ similar to Pascal and C
  - ◆ delays is only interaction with simulator
  - ◆ fairly efficient and easy to write
  - ◆ IEEE standard
- VHDL (circa 1987) - DoD sponsored standard
  - ◆ similar to Ada (emphasis on re-use and maintainability)
  - ◆ simulation semantics visible
  - ◆ very general but verbose
  - ◆ IEEE standard

# Verilog

---

- Supports structural and behavioral descriptions
- Structural
  - ◆ explicit structure of the circuit
  - ◆ e.g., each logic gate instantiated and connected to others
- Behavioral
  - ◆ program describes input/output behavior of circuit
  - ◆ many structural implementations could have same behavior
  - ◆ e.g., different implementation of one Boolean function
- We'll mostly be using behavioral Verilog in Aldec ActiveHDL
  - ◆ rely on schematic when we want structural descriptions

# Working with Comb-Logic Summary

---

- Design problems
  - ◆ filling in truth tables
  - ◆ incompletely specified functions
  - ◆ simplifying two-level logic
- Realizing two-level logic
  - ◆ NAND and NOR networks
  - ◆ networks of Boolean functions and their time behavior
- Time behavior
- Hardware description languages
- Later
  - ◆ combinational logic technologies
  - ◆ more design case studies