

# **CH-5: Combinational Logic** **Design Cases**

*Contemporary Logic Design*

YONSEI UNIVERSITY

Fall 2016

# Combinational Logic Design EXs

---

- General design procedure
- *Case studies*
  - ◆ BCD to 7-segment display controller
  - ◆ logical function unit
  - ◆ process line controller
  - ◆ calendar subsystem
- *Arithmetic circuits*
  - ◆ integer representations
  - ◆ addition/subtraction
  - ◆ arithmetic/logic units

# General Design Procedure for Comb-Logic

## 1. *Understand the problem*

- ◆ what is the circuit supposed to do?
- ◆ write down inputs (data, control) and outputs
- ◆ draw block diagram or other picture

## 2. *Formulate the problem* using a suitable design representation

- ◆ truth table or waveform diagram are typical
- ◆ may require encoding of symbolic inputs and outputs

## 3. *Choose implementation target*



- ◆ ROM, PAL, PLA
- ◆ mux, decoder and OR-gate
- ◆ discrete gates

## 4. *Follow implementation procedure*

- ◆ K-maps for two-level, multi-level
- ◆ design tools and hardware description language (e.g., Verilog)
 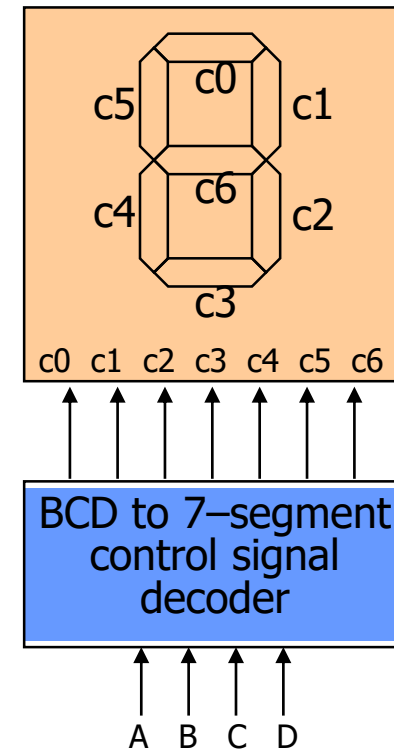
# BCD to 7-Segment Display Controller

- *Understanding the problem*
  - ◆ *input* is a 4 bit bcd digit (A, B, C, D)
  - ◆ *output* is the control signals for the display (7 outputs C0 – C6)
- Block diagram



# Formalize the Problem

- *Truth table*
  - ◆ show don't cares
- Choose *implementation target*
  - ◆ if ROM, we are done
  - ◆ don't cares imply PAL/PLA may be attractive
- *Follow implementation procedure*
  - ◆ minimization using K-maps

A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	—	—	—	—	—	—	—	—
1	1	—	—	—	—	—	—	—	—	—

- 15 unique product terms when minimized individually

$$\begin{aligned}C0 &= A + B D + C + B' D' \\C1 &= C' D' + C D + B' \\C2 &= B + C' + D \\C3 &= B' D' + C D' + B C' D + B' C \\C4 &= B' D' + C D' \\C5 &= A + C' D' + B D' + B C' \\C6 &= A + C D' + B C' + B' C\end{aligned}$$

# Implementation as Minimized S-o-P

## ■ Can do better

- ◆ 9 unique product terms (instead of 15)
- ◆ share terms among outputs
- ◆ each output not necessarily in minimized form


		00	01	11	10	A
00	C2	1	1	X	1	
01		1	1	X	1	
11	C	1	1	X	X	
10		0	1	X	X	D
						B

$$\begin{aligned}
 C0 &= A + B D + C + B' D' \\
 C1 &= C' D' + C D + B' \\
 C2 &= B + C' + D \\
 C3 &= B' D' + C D' + B C' D + B' C \\
 C4 &= B' D' + C D' \\
 C5 &= A + C' D' + B D' + B C' \\
 C6 &= A + C D' + B C' + B' C
 \end{aligned}$$

		00	01	11	10	A
00	C2	1	1	X	1	
01		1	1	X	1	
11	C	1	1	X	X	
10		0	1	X	X	D
						B

$$\begin{aligned}
 C0 &= B C' D + C D + B' D' + B C D' + A \\
 C1 &= B' D + C' D' + C D + B' D' \\
 C2 &= B' D + B C' D + C' D' + C D + B C D' \\
 C3 &= B C' D + B' D + B' D' + B C D' \\
 C4 &= B' D' + B C D' \\
 C5 &= B C' D + C' D' + A + B C D' \\
 C6 &= B' C + B C' + B C D' + A
 \end{aligned}$$

# PLA Implementation

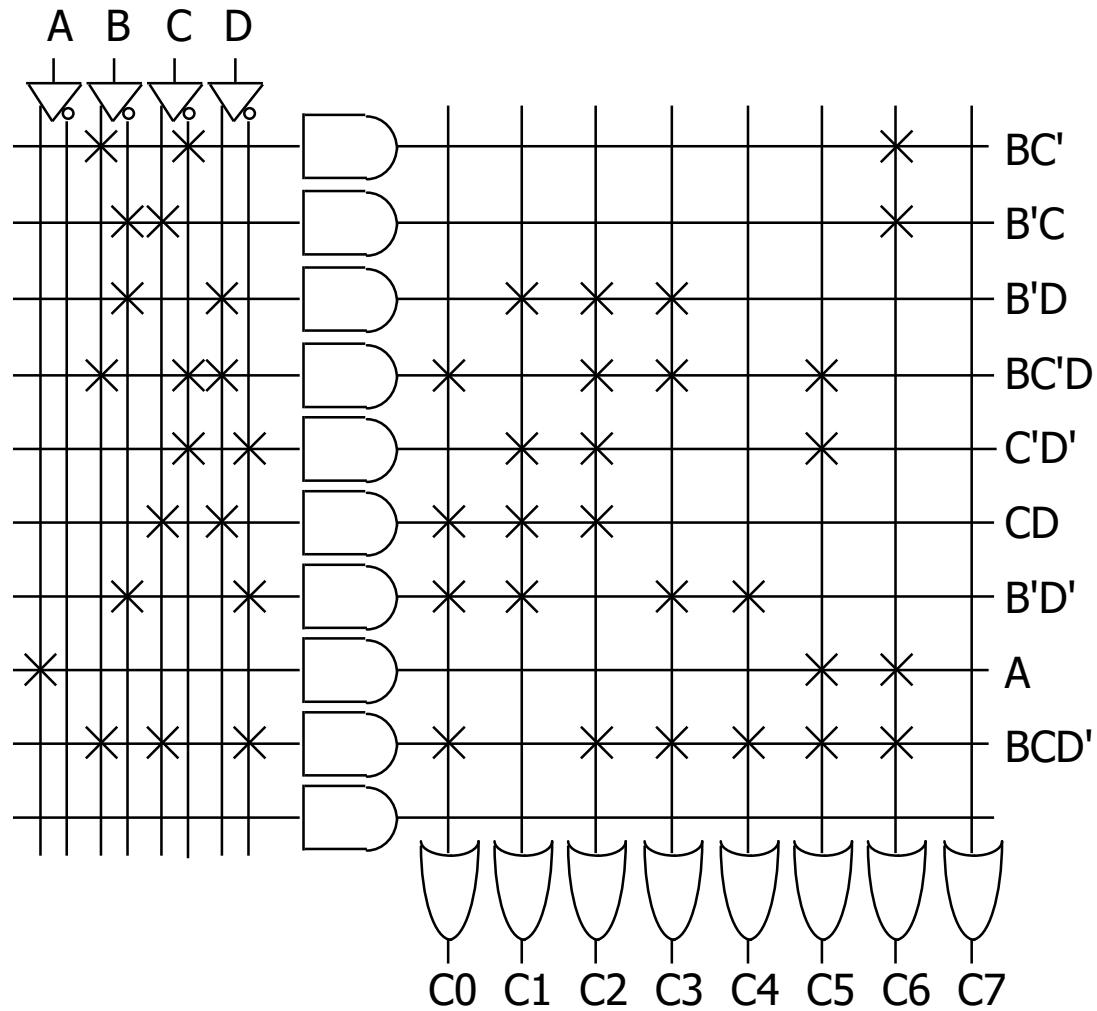



# PAL vs. Discrete Gate Implementation

- Limit of 4 product terms per output
  - ◆ decomposition of functions with larger number of terms
  - ◆ do not share terms in PAL anyway  
(although there are some with some shared terms)

$$C2 = B + C' + D$$

$$C2 = B' D + B C' D + C' D' + C D + B C D'$$

$$C2 = B' D + B C' D + C' D' + W$$

$W = C D + B C D'$  need another input and another output

- Decompose into multi-level logic (hopefully with CAD support)
  - ◆ find common sub-expressions among functions

$$C0 = C3 + A' B X' + A D Y$$

$$C1 = Y + A' C5' + C' D' C6$$

$$C2 = C5 + A' B' D + A' C D$$

$$C3 = C4 + B D C5 + A' B' X'$$

$$C4 = D' Y + A' C D'$$

$$C5 = C' C4 + A Y + A' B X$$

$$C6 = A C4 + C C5 + C4' C5 + A' B' C$$

$$X = C' + D'$$

$$Y = B' C'$$

# Logical Function Unit

- Multi-purpose function block
  - ◆ 3 *control inputs* to specify operation to perform on operands
  - ◆ 2 *data inputs* for operands
  - ◆ 1 *output* of the same bit-width as operands


C0	C1	C2	Function	Comments
0	0	0	1	always 1
0	0	1	$A + B$	logical OR
0	1	0	$(A \bullet B)'$	logical NAND
0	1	1	$A \text{ xor } B$	logical xor
1	0	0	$A \text{ xnor } B$	logical xnor
1	0	1	$A \bullet B$	logical AND
1	1	0	$(A + B)'$	logical NOR
1	1	1	0	always 0

3 control inputs: C0, C1, C2  
2 data inputs: A, B  
1 output: F

# Formalize the Problem

C0	C1	C2	A	B	F
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

 choose implementation technology  
 5-variable K-map to discrete gates  
 multiplexor implementation




# Production Line Control

---

- Rods of *varying length* ( $\pm 10\%$ ) travel on conveyor belt
  - ◆ mechanical arm pushes rods within spec ( $\pm 5\%$ ) to one side
  - ◆ second arm pushes rods too long to other side
  - ◆ rods that are too short stay on belt
  - ◆ 3 light barriers (light source + photocell) as sensors
  - ◆ *design combinational logic* to activate the arms
- Understanding the problem
  - ◆ *inputs* are three sensors
  - ◆ *outputs* are two arm control signals
  - ◆ assume sensor reads "1" when tripped, "0" otherwise
  - ◆ call sensors A, B, C
 
# Sketch of Problem

- Position of sensors
  - ◆ A to B distance = specification – 5%
  - ◆ A to C distance = specification + 5%



# Formalize the Problem

- Truth table
  - ◆ show don't cares

A	B	C	Function
0	0	0	do nothing
0	0	1	do nothing
0	1	0	do nothing
0	1	1	do nothing
1	0	0	too short
1	0	1	don't care
1	1	0	in spec
1	1	1	too long

logic implementation now straightforward  
just use three 3-input AND gates

"***too short***" =  $AB'C'$   
(only first sensor tripped)

"***in spec***" =  $A B C'$   
(first two sensors tripped)

"***too long***" =  $A B C$   
(all three sensors tripped)


# Calendar Subsystem

- Determine number of days in a month (to control watch display)
  - ◆ used in controlling the display of a wrist-watch LCD screen
  - ◆ *inputs:* month, leap year flag
  - ◆ *outputs:* number of days
- Use software implementation to help understand the problem

```
integer number_of_days ( month, leap_year_flag) {  
    switch (month) {  
        case 1: return (31);  
        case 2: if (leap_year_flag == 1)  
                then return (29)  
                else return (28);  
        case 3: return (31);  
        case 4: return (30);  
        case 5: return (31);  
        case 6: return (30);  
        case 7: return (31);  
        case 8: return (31);  
        case 9: return (30);  
        case 10: return (31);  
        case 11: return (30);  
        case 12: return (31);  
        default: return (0);  
    }  
}
```
 
# Formalize the Problem

- Encoding:
  - ♦ binary number for month: 4 bits
  - ♦ 4 wires for 28, 29, 30, and 31one-hot – only one true at any time
- Block diagram:



month	leap	28	29	30	31
0000	–	–	–	–	–
0001	–	0	0	0	1
0010	0	1	0	0	0
0010	1	0	1	0	0
0011	–	0	0	0	1
0100	–	0	0	1	0
0101	–	0	0	0	1
0110	–	0	0	1	0
0111	–	0	0	0	1
1000	–	0	0	0	1
1001	–	0	0	1	0
1010	–	0	0	0	1
1011	–	0	0	1	0
1100	–	0	0	0	1
1101	–	–	–	–	–
111–	–	–	–	–	–



# Choose Implementation Target & Mapping

## ■ Discrete gates

♦  $28 =$   
 $m8' m4' m2 m1' \text{ leap}'$

♦  $29 =$   
 $m8' m4' m2 m1' \text{ leap}$

♦  $30 =$   
 $m8' m4 m1' + m8 m1$

♦  $31 =$   
 $m8' m1 + m8 m1'$

## ■ Can translate to S-o-P or P-o-S

month	leap	28	29	30	31
0000	—	—	—	—	—
0001	—	0	0	0	1
0010	0	1	0	0	0
0011	1	0	1	0	0
0100	—	0	0	1	0
0101	—	0	0	0	1
0110	—	0	0	1	0
0111	—	0	0	0	1
1000	—	0	0	0	1
1001	—	0	0	1	0
1010	—	0	0	0	1
1011	—	0	0	1	0
1100	—	0	0	0	1
1101	—	—	—	—	—
111—	—	—	—	—	—

# Leap Year Flag

---

- Determine *value of leap year flag* given the year
  - ◆ For years after 1582 (Gregorian calendar reformation),
  - ◆ leap years are all the years divisible by 4,
  - ◆ except that years divisible by 100 are not leap years,
  - ◆ but years divisible by 400 are leap years.
- Encoding the year:
  - ◆ *binary* – easy for divisible by 4,  
but difficult for 100 and 400 (not powers of 2)
  - ◆ *BCD* – easy for 100,  
but more difficult for 4, what about 400?
- Parts:
  - ◆ construct a circuit that determines if the year is divisible by 4
  - ◆ construct a circuit that determines if the year is divisible by 100
  - ◆ construct a circuit that determines if the year is divisible by 400
  - ◆ combine the results of the previous three steps to yield the leap year flag

# Activity: Divisible-by-4 Circuit

---

# Divisible-by-100 and Divisible-by-400

- Divisible-by-100 just requires checking that all bits of two low-order digits are all 0:

$$YT8' YT4' YT2' YT1' \cdot YO8' YO4' YO2' YO1'$$

- Divisible-by-400 combines the divisible-by-4 (applied to the thousands and hundreds digits) and divisible-by-100 circuits

$$(YM1' YH2' YH1' + YM1 YH2 YH1')$$

$$\cdot (YT8' YT4' YT2' YT1' \cdot YO8' YO4' YO2' YO1' )$$


# Combining to Determine Leap Year Flag

---

- Label results of previous three circuits: D4, D100, and D400

$$\begin{aligned}\text{leap\_year\_flag} &= D4 (D100 \cdot D400')' \\ &= D4 \cdot D100' + D4 \cdot D400 \\ &= D4 \cdot D100' + D400\end{aligned}$$

# Implementation of Leap Year Flag

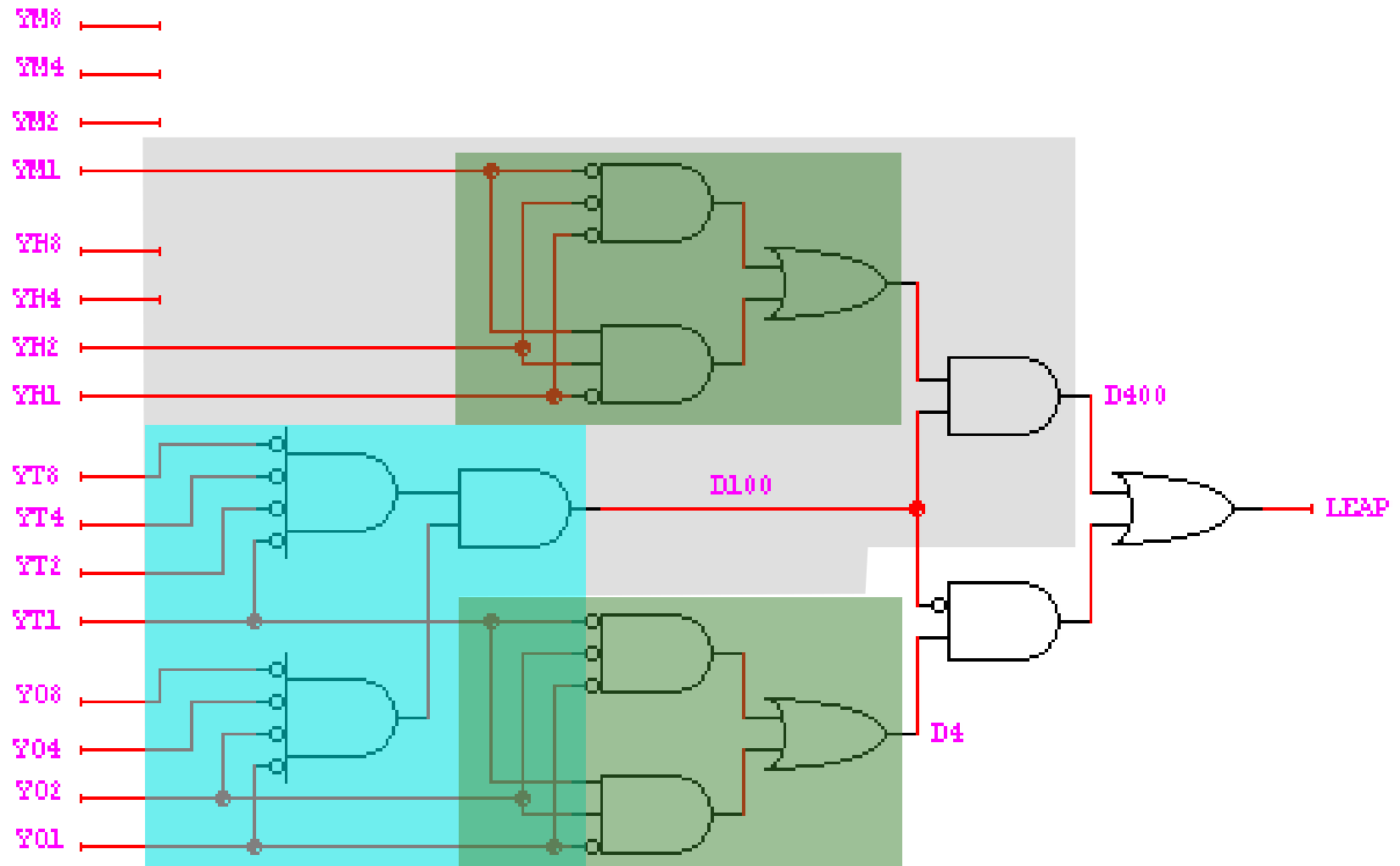

# Arithmetic Circuits

---

- Excellent examples of combinational logic design
- Time vs. space trade-offs
  - ◆ *doing things fast* may require more logic and thus more space
  - ◆ example: carry lookahead logic
- Arithmetic and logic units
  - ◆ general-purpose building blocks
  - ◆ critical components of processor datapaths
  - ◆ used within most computer instructions

# Number Systems

---

- Representation of positive numbers is the same in most systems
- Major *differences* are in how negative numbers are represented
- *Representation of negative numbers* come in three major schemes
  - ◆ sign and magnitude
  - ◆ 1s complement
  - ◆ 2s complement
- Assumptions
  - ◆ we'll assume a 4 bit machine word
  - ◆ 16 different values can be represented
  - ◆ roughly half are positive, half are negative



# Sign and Magnitude

- High order bit dedicated to *sign* (positive or negative)

- ◆ sign: 0 = positive (or zero), 1 = negative

- Rest represent the *absolute value* or magnitude

- ◆ three low order bits: 0 (000) thru 7 (111)

- Range for n bits


- ◆  $\pm 2^{n-1} - 1$  (two representations for 0)

- Cumbersome addition/subtraction

- ◆ must compare magnitudes to determine sign of result

0 100 = + 4

1 100 = - 4

 

# 1s Complement

- If N is a positive number, then the *negative* of N (its 1s complement or N' ) is  $N' = (2^n - 1) - N$ 
  - ◆ example: 1s complement of 7

$$2^4 = 10000$$

$$1 = 00001$$

$$2^4 - 1 = \underline{1111}$$

$$7 = \underline{0111}$$

$$1000 = -7 \text{ in 1s complement form}$$


- ◆ shortcut: simply compute bit-wise complement ( 0111 -> 1000 )

# 1s Complement

- Subtraction implemented by 1s complement and then addition
- Two representations of 0
  - ◆ causes some complexities in addition
- High-order bit can act as sign bit

0 100 = + 4

1 011 = - 4

 


# 2s Complement

- 1s complement with negative numbers shifted one position clockwise
  - ◆ only one representation for 0
  - ◆ one more negative number than positive numbers
  - ◆ high-order bit can act as sign bit

0 100 = + 4

1 100 = - 4

 

# 2s Complement

- If N is a positive number, then the *negative* of N (its 2s complement or  $N^*$ ) is  $N^* = 2^n - N$

- ◆ example: 2s complement of 7

$$2^4 = 10000$$

$$\text{subtract } 7 = \underline{0111}$$

$$1001 = \text{repr. of } -7$$

- ◆ example: 2s complement of  $-7$

$$2^4 = 10000$$

$$\text{subtract } -7 = \underline{1001}$$

$$0111 = \text{repr. of } 7$$

- ◆ shortcut: 2s complement = bit-wise complement + 1

- $0111 \rightarrow 1000 + 1 \rightarrow 1001$  (representation of  $-7$ )

- $1001 \rightarrow 0110 + 1 \rightarrow 0111$  (representation of  $7$ )

# 2s Complement Add and Sub

- Simple addition and subtraction
  - ◆ simple scheme makes 2s complement the virtually unanimous choice for integer number systems in computers

$$\begin{array}{r}
 \text{4} \quad 00 \quad 0100 \\
 + 3 \quad 0011 \\
 \hline
 7 \quad 0111
 \end{array}$$

$$\begin{array}{r}
 \text{4} \quad 0100 \\
 - 3 \quad 1101 \\
 \hline
 1 \quad 10001
 \end{array}$$

# Why Can the Carry-out Be Ignored?

---

- *Can't ignore it completely*
  - ◆ needed to check for overflow
- If carry-into-sign = carry-out: ignore the carry
- If carry-into-sign  $\neq$  carry-out: overflow
  - ◆ Result is out of range
  - ◆ Bigger than given range

# Why Can the Carry-out Be Ignored?

- When there is no overflow, carry-out may be true but can be ignored

- ◆  $M + N$  when  $N > M$ :

$$M^* + N = (2^n - M) + N = 2^n + (N - M)$$

- $(N - M)$  is what we need
- *ignoring carry-out* is just like subtracting  $2^n$

- ◆  $-M + -N$  where  $N + M \leq 2^{n-1}$

$$(-M) + (-N) = M^* + N^* = (2^n - M) + (2^n - N) = 2^n - (M + N) + 2^n$$



- $2^n - (M + N)$  is what we need
- *ignoring the carry*, it is just the 2s complement representation for  $-(M + N)$



# Overflow in 2s Complement Add/Sub
  
## ■ Overflow conditions

- ◆ add two positive numbers to get a negative number
- ◆ add two negative numbers to get a positive number



# Overflow Conditions

- Overflow when carry into sign bit position is not equal to carry-out

$$\begin{array}{r}
 5 \\
 \underline{-3} \\
 -8
 \end{array}
 \qquad
 \begin{array}{r}
 0\ 1\ 1\ 1 \\
 0\ 1\ 0\ 1 \\
 \underline{0\ 0\ 1\ 1} \\
 1\ 0\ 0\ 0
 \end{array}$$

overflow

$$\begin{array}{r}
 -7 \\
 \underline{-2} \\
 7
 \end{array}
 \qquad
 \begin{array}{r}
 1\ 0\ 0\ 0 \\
 1\ 0\ 0\ 1 \\
 \underline{1\ 1\ 1\ 0} \\
 1\ 0\ 1\ 1\ 1
 \end{array}$$

overflow

$$\begin{array}{r}
 5 \\
 \underline{+2} \\
 7
 \end{array}
 \qquad
 \begin{array}{r}
 0\ 0\ 0\ 0 \\
 0\ 1\ 0\ 1 \\
 \underline{0\ 0\ 1\ 0} \\
 0\ 1\ 1\ 1
 \end{array}$$

no overflow


$$\begin{array}{r}
 -3 \\
 \underline{-5} \\
 -8
 \end{array}
 \qquad
 \begin{array}{r}
 1\ 1\ 1\ 1 \\
 1\ 1\ 0\ 1 \\
 \underline{1\ 0\ 1\ 1} \\
 1\ 1\ 0\ 0\ 0
 \end{array}$$

no overflow

# Circuits for Binary Addition


- Half adder (add 2 1-bit numbers)
  - ◆  $\text{Sum} = A_i' B_i + A_i B_i' = A_i \text{ xor } B_i$
  - ◆  $\text{Cout} = A_i B_i$
- Full adder (carry-in to cascade for multi-bit adders)
  - ◆  $\text{Sum} = C_i \text{ xor } A \text{ xor } B$
  - ◆  $\text{Cout} = B C_i + A C_i + A B = C_i (A + B) + A B$

A <sub>i</sub>	B <sub>i</sub>	Sum	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

A <sub>i</sub>	B <sub>i</sub>	C <sub>in</sub>	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Full Adder Implementations

 

usually interested in adding more than two bits

this motivates the need for the full adder

# Full Adder Implementations

A	B	CI	S	CO
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

		A B			
CI	S	00	01	11	10
		0	1	0	1
S	1	1	0	1	0

		A B			
CI	CO	00	01	11	10
		0	0	1	0
CO	1	0	1	1	1



$$S = CI \text{ xor } A \text{ xor } B$$

$$CO = B \text{ CI} + A \text{ CI} + A B = CI (A + B) + A B$$

# Full Adder Implementations

- Standard approach


- 6 gates
- 2 XORs, 2 ANDs, 2 ORs

  

- Alternative implementation

- 5 gates
- half adder is an XOR gate and AND gate
- 2 XORs, 2 ANDs, 1 OR
 
$$\text{Cout} = A B + \text{Cin} (A \text{ xor } B) = A B + B \text{Cin} + A \text{Cin}$$



# Full Adder Implementations

Full adder is constructed by using Half Adders

■  $S = A \text{ xor } B \text{ xor } C_{in}$

$$C = B C_i + A C_i + A B$$


$$= B C_i (A + A') + A C_i (B + B') + A B$$

$$= \textcolor{red}{A B C_i} + A' B C_i + \cancel{A B C_i} + A B' C_i + \textcolor{red}{A B}$$

$$= \textcolor{red}{A B (C_i + 1)} + A' B C_i + A B' C_i$$


$$= A B + C_i (A' B + A B')$$

$$= A B + C_i (A \text{ xor } B)$$

 
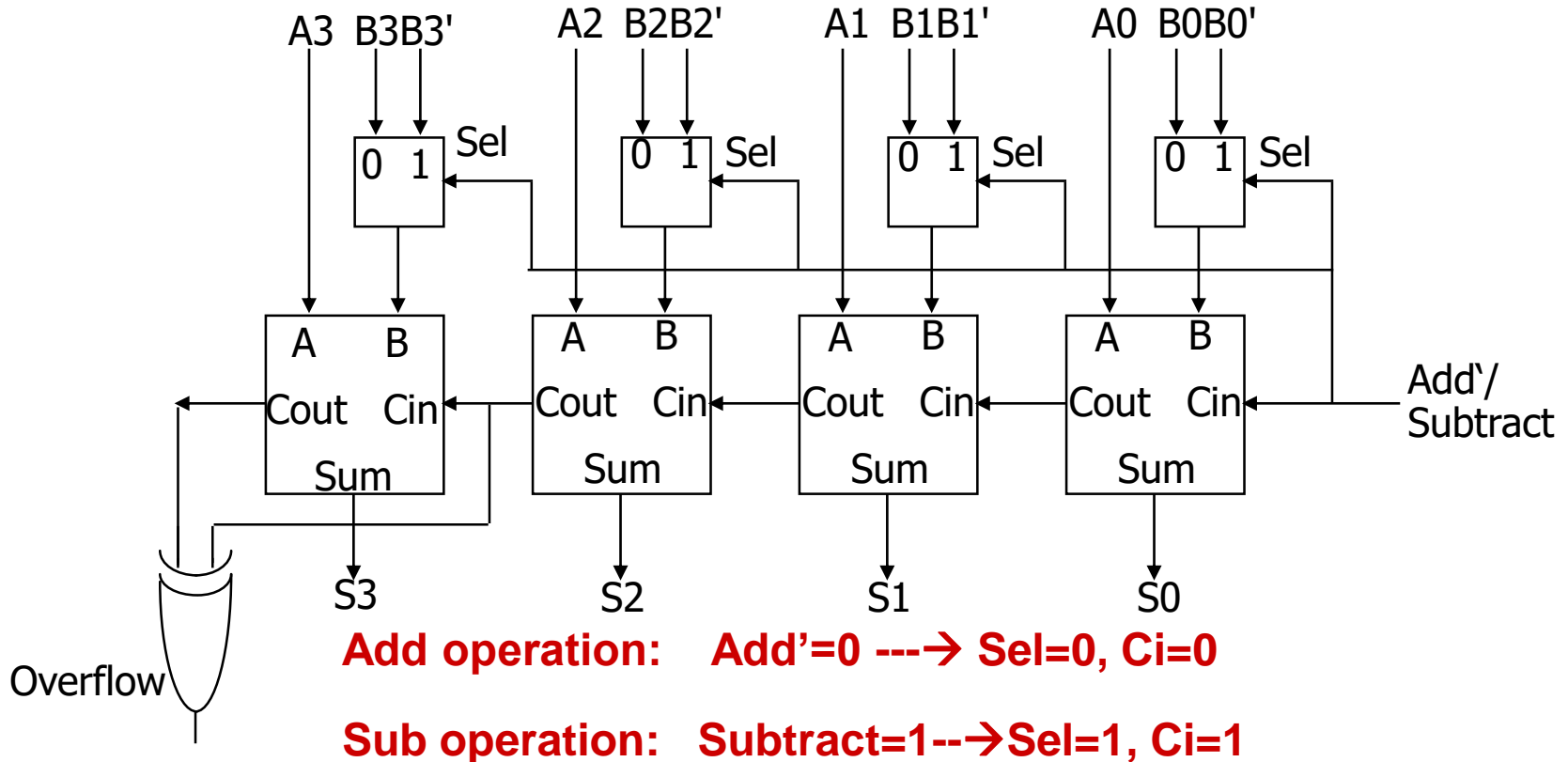
# Adder/Subtractor



- Use an adder to do subtraction thanks to 2s complement representation
  - ◆  $A - B = A + (-B) = A + B' + 1$
  - ◆ control signal selects B or 2s complement of B





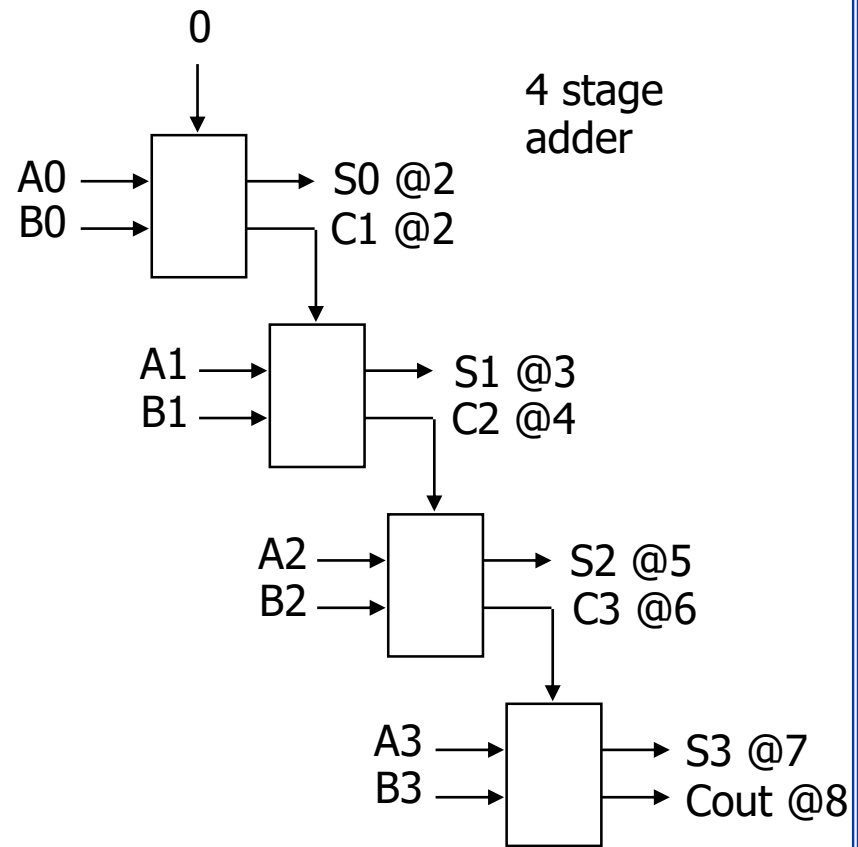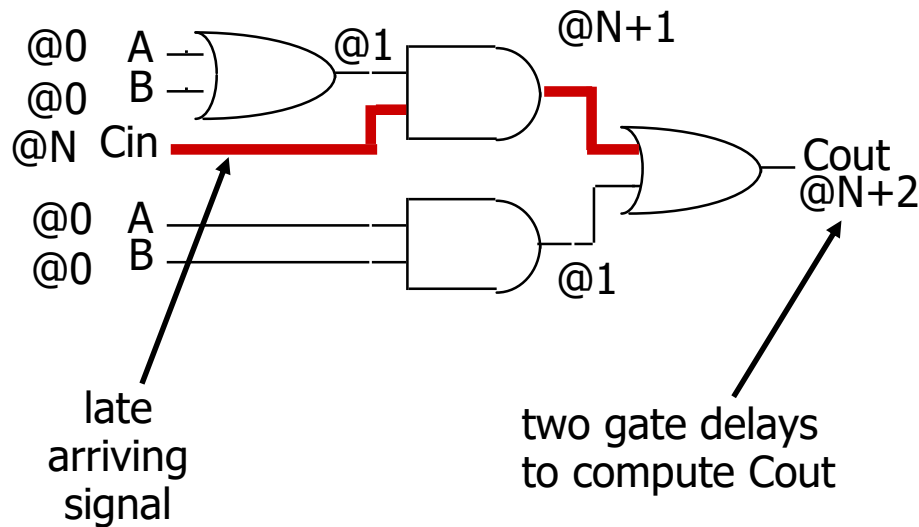
# Ripple-carry Adders

- Critical delay
  - ◆ the propagation of carry from low to high order stages


 
# Ripple-carry Adders

- Critical delay
  - ◆ the propagation of carry from low to high order stages
  - ◆ 1111 + 0001 is the worst case addition
  - ◆ carry must propagate through all bits



# Carry-lookahead Logic

---

- Carry generate:  $G_i = A_i B_i$ 
  - ◆ must generate carry when  $A = B = 1$
- Carry propagate:  $P_i = A_i \text{ xor } B_i$ 
  - ◆ carry-in will equal carry-out here
- *Sum and Cout* can be re-expressed in terms of generate/propagate:
  - ◆  $S_i = A_i \text{ xor } B_i \text{ xor } C_i$   
 $= P_i \text{ xor } C_i$
  - ◆  $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$   
 $= A_i B_i + C_i (A_i + B_i)$   
 $= A_i B_i + C_i (A_i \text{ xor } B_i)$   
 $= G_i + C_i P_i$





# Carry-lookahead Logic

---


- Re-express the carry logic as follows:
  - ◆  $C_1 = G_0 + P_0 C_0$
  - ◆  $C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$
  - ◆  $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$
  - ◆  $C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$
- Each of the carry equations can be implemented with two-level logic
  - ◆ all inputs are now directly derived from data inputs and not from intermediate carries
  - ◆ this allows computation of all sum outputs to proceed in parallel
    
# Carry-lookahead Implementation

- Adder with propagate and generate outputs





increasingly complex  
logic for carries

 
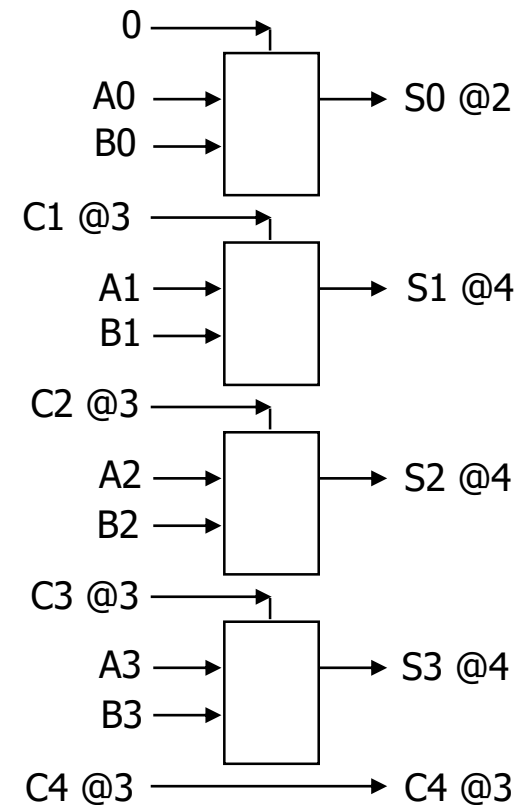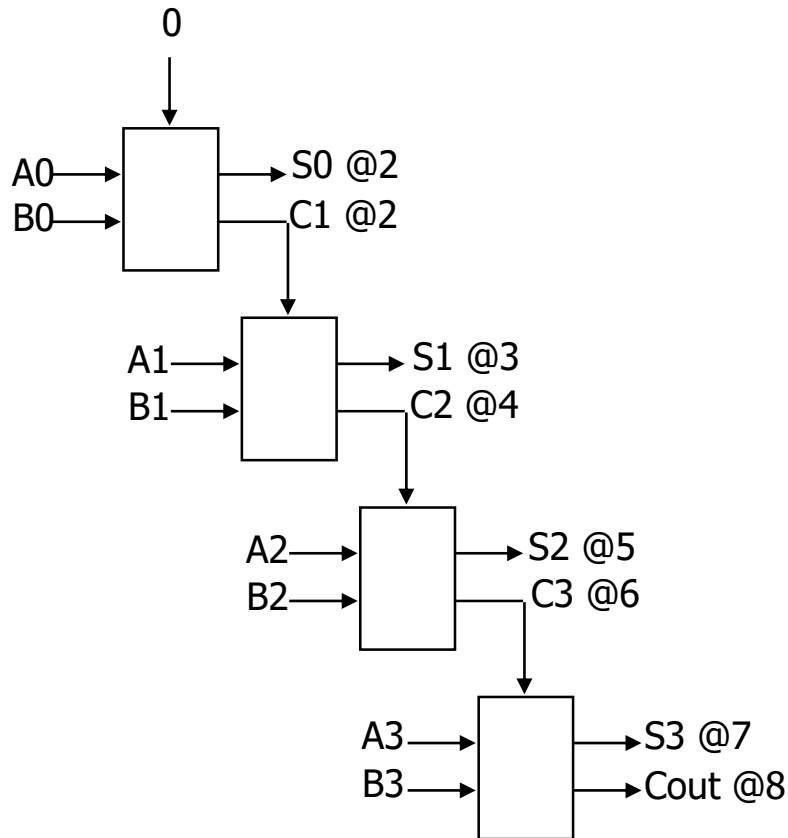
# Carry-lookahead Implementation


- Carry-lookahead logic generates individual carries
  - ◆ sums computed much more quickly in parallel
  - ◆ however, cost of carry logic increases with more stages



# Carry-lookahead Adder /w cascaded carry-lookahead logic

 
## ■ Carry-lookahead adder

- ◆ 4 four-bit adders with internal carry lookahead  $G = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$
- ◆ second level carry lookahead unit extends lookahead to 16 bits


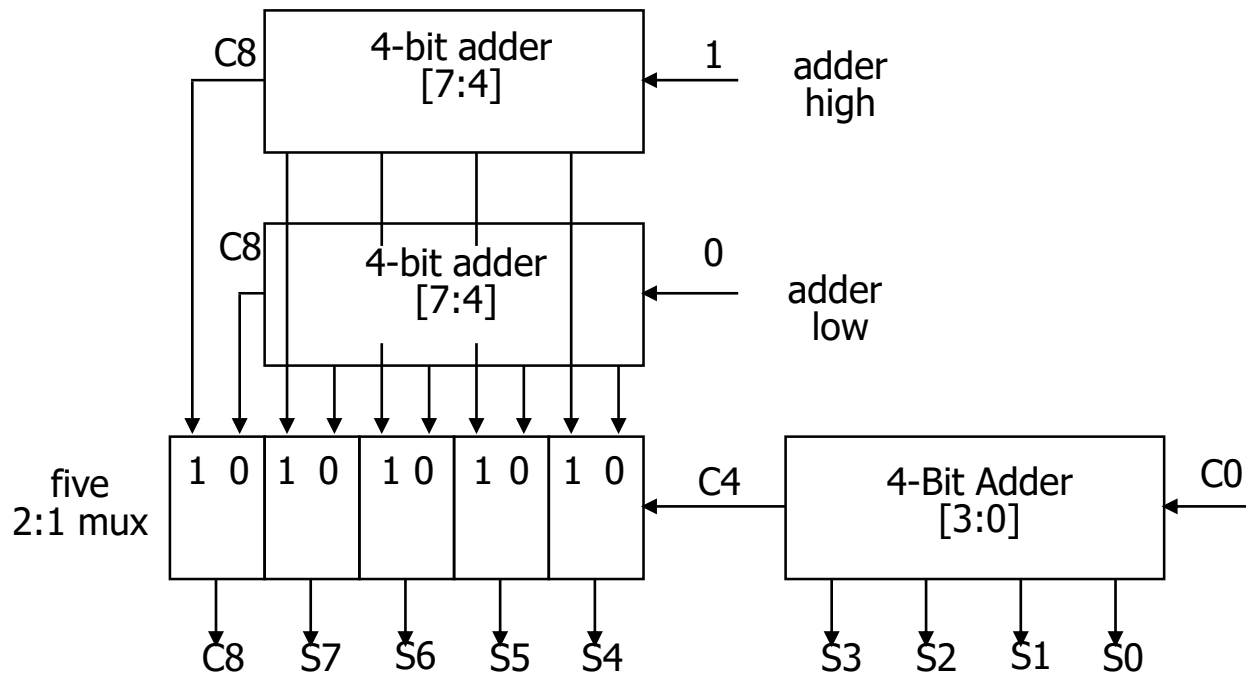
# Carry-select Adder

- *Redundant hardware* to make carry calculation go faster
  - ◆ compute two high-order sums in parallel while waiting for carry-in
  - ◆ one assuming carry-in is 0 and another assuming carry-in is 1
  - ◆ select correct result once carry-in is finally computed





# Arithmetic Logic Unit Design Specification

**M = 0, logical bitwise operations**

<b>S1</b>	<b>S0</b>	<b>Function</b>	<b>Comment</b>
<b>0</b>	<b>0</b>	<b><math>F_i = A_i</math></b>	<b>input <math>A_i</math> transferred to output</b>
<b>0</b>	<b>1</b>	<b><math>F_i = \text{not } A_i</math></b>	<b>complement of <math>A_i</math> transferred to output</b>
<b>1</b>	<b>0</b>	<b><math>F_i = A_i \text{ xor } B_i</math></b>	<b>compute XOR of <math>A_i, B_i</math></b>
<b>1</b>	<b>1</b>	<b><math>F_i = A_i \text{ xnor } B_i</math></b>	<b>compute XNOR of <math>A_i, B_i</math></b>

**M = 1, C0 = 0, arithmetic operations**

<b>0</b>	<b>0</b>	<b><math>F = A</math></b>	<b>input A passed to output</b>
<b>0</b>	<b>1</b>	<b><math>F = \text{not } A</math></b>	<b>complement of A passed to output</b>
<b>1</b>	<b>0</b>	<b><math>F = A \text{ plus } B</math></b>	<b>sum of A and B</b>
<b>1</b>	<b>1</b>	<b><math>F = (\text{not } A) \text{ plus } B</math></b>	<b>sum of B and complement of A</b>

**M = 1, C0 = 1, arithmetic operations**

<b>0</b>	<b>0</b>	<b><math>F = A \text{ plus } 1</math></b>	<b>increment A</b>
<b>0</b>	<b>1</b>	<b><math>F = (\text{not } A) \text{ plus } 1</math></b>	<b>twos complement of A</b>
<b>1</b>	<b>0</b>	<b><math>F = A \text{ plus } B \text{ plus } 1</math></b>	<b>increment sum of A and B</b>
<b>1</b>	<b>1</b>	<b><math>F = (\text{not } A) \text{ plus } B \text{ plus } 1</math></b>	<b>B minus A</b>

**logical and arithmetic operations**  
**not all operations appear useful, but "fall out" of internal logic**


# Arithmetic Logic Unit Design

- Sample ALU – truth table

M	S1	S0	Ci	Ai	Bi	Fi	Ci+1
0	0	0	X	0	X	0	X
			X	1	X	1	X
			X	0	X	1	X
	0	1	X	1	X	0	X
			X	0	0	1	X
			X	1	0	1	X
	1	0	X	0	0	1	X
			X	1	1	0	X
			X	0	1	0	X
	1	1	X	0	0	1	X
			X	1	0	0	X
			X	1	1	1	X
1	0	0	0	0	X	0	X
			0	1	X	1	X
			0	0	X	1	X
	0	1	0	1	X	0	X
			0	0	0	1	0
			0	1	0	1	0
	1	0	0	0	1	0	1
			0	1	1	0	1
			0	0	0	1	0
	1	1	0	0	1	0	0
			0	1	0	0	0
			0	1	1	1	0
1	0	0	1	0	X	1	0
			1	1	X	0	1
			1	0	X	0	1
	0	1	1	1	X	1	0
			1	0	0	1	0
			1	1	0	0	1
	1	0	1	0	1	0	1
			1	1	1	1	1
			1	0	0	0	1
	1	1	1	0	1	1	1
			1	1	0	1	0
			1	1	1	0	1

 
# Arithmetic Logic Unit Design

- Sample ALU – multi-level discrete gate logic implementation



# Arithmetic Logic Unit Design
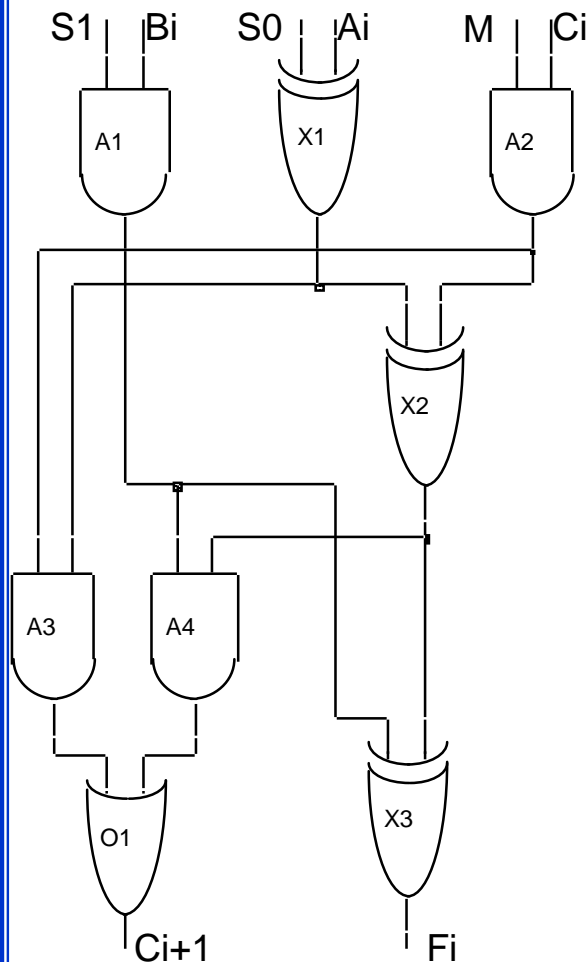
## ■ Sample ALU – clever multi-level implementation



first-level gates

use S0 to complement Ai

S0 = 0 causes gate X1 to pass Ai

S0 = 1 causes gate X1 to pass Ai'

use S1 to block Bi

S1 = 0 causes gate A1 to make Bi go forward as 0  
(don't want Bi for operations with just A)

S1 = 1 causes gate A1 to pass Bi

use M to block Ci

M = 0 causes gate A2 to make Ci go forward as 0  
(don't want Ci for logical operations)

M = 1 causes gate A2 to pass Ci

other gates

for M=0 (logical operations, Ci is ignored)

$$F_i = S_1 B_i \text{ xor } (S_0 \text{ xor } A_i)$$

$$= S_1' S_0' (A_i) + S_1' S_0 (A_i') +$$

$$S_1 S_0' (A_i B_i' + A_i' B_i) + S_1 S_0 (A_i' B_i' + A_i B_i)$$


for M=1 (arithmetic operations)

$$F_i = S_1 B_i \text{ xor } ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$

$$C_{i+1} = C_i (S_0 \text{ xor } A_i) + S_1 B_i ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$

just a full adder with inputs S0 xor Ai, S1 Bi, and Ci

# BCD Addition

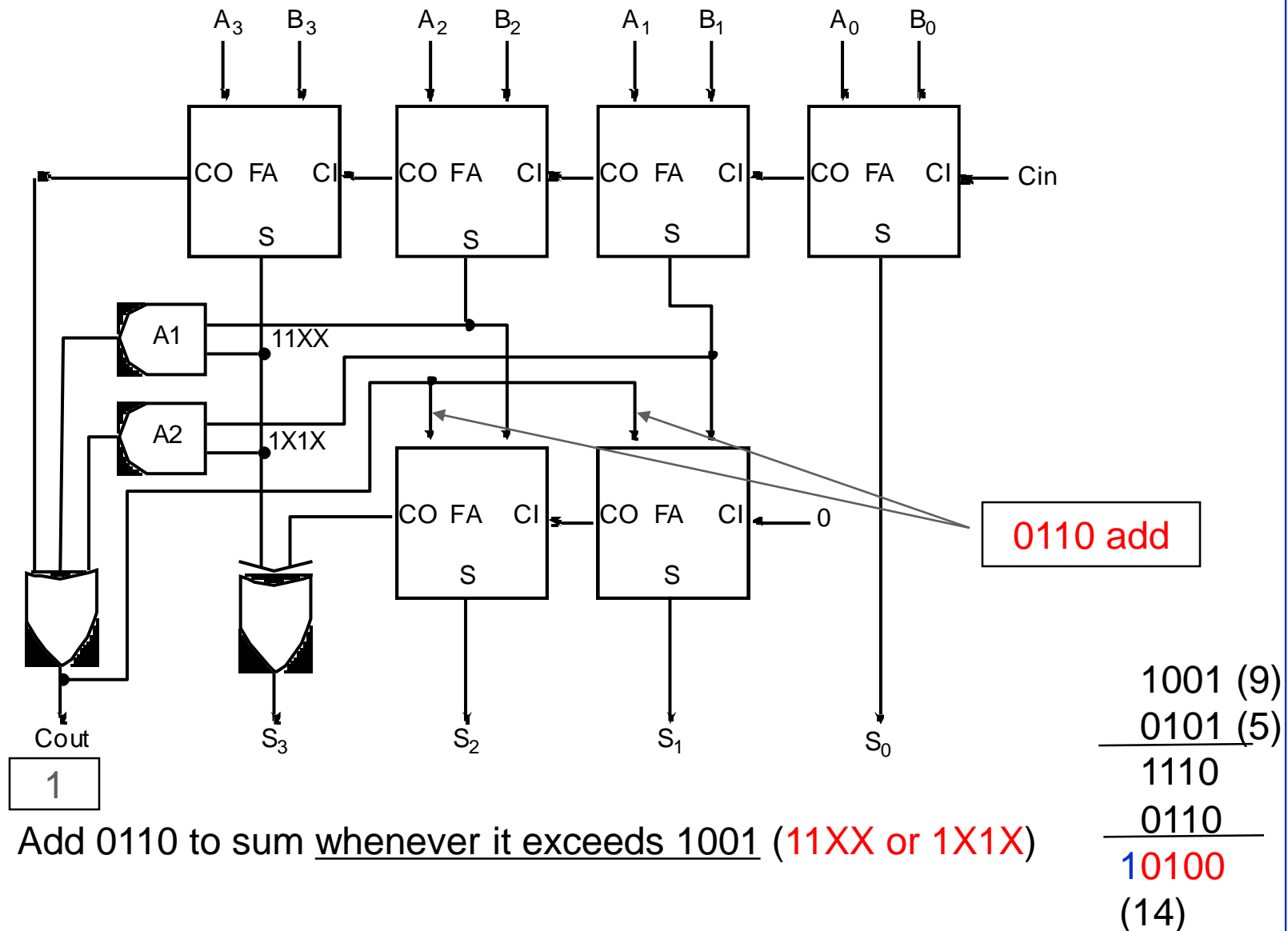

# Summary for EX of Combinational Logic

- Combinational logic design process
  - ◆ *formalize problem*: encodings, truth-table, equations
  - ◆ *choose implementation technology* (ROM, PAL, PLA, discrete gates)
  - ◆ *implement by following the design procedure* for that technology
- Binary number representation
  - ◆ positive numbers the same
  - ◆ difference is in how negative numbers are represented
  - ◆ 2s complement easiest to handle: one representation for zero, slightly complicated complementation, simple addition
- Circuits for binary addition
  - ◆ basic half-adder and full-adder
  - ◆ carry lookahead logic
  - ◆ carry-select
- ALU Design
  - ◆ specification, implementation