

CH-2: Combinational **Logic Design**

Contemporary Logic Design

YONSEI UNIVERSITY

Fall 2016

Combinational Logic

- Basic logic
 - ◆ Boolean algebra, proofs by re-writing, proofs by perfect induction
 - ◆ logic functions, truth tables, and switches
 - ◆ NOT, AND, OR, NAND, NOR, XOR, . . . , minimal set
- Logic realization
 - ◆ two-level logic and canonical forms
 - ◆ incompletely specified functions
- Simplification
 - ◆ uniting theorem
 - ◆ grouping of terms in Boolean functions
- Alternate representations of Boolean functions
 - ◆ cubes
 - ◆ Karnaugh maps

Possible Logic Functions of 2-Vars

- There are 16 possible functions for 2 input variables:
 - in general, there are 2^{2^n} functions of n inputs



X	Y	16 possible functions (F0–F15)															
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
		0		X		Y		X <u>xor</u> Y		X <u>or</u> Y		X <u>nor</u> Y not (X <u>or</u> Y)		X = Y		not Y	
		X <u>and</u> Y												not X		X <u>nand</u> Y not (X <u>and</u> Y)	

Cost of Different Logic Functions

- Different functions are easier or harder to implement
 - ◆ each has a cost associated with the number of switches needed
 - ◆ 0 (F0) and 1 (F15): require 0 switches, directly connect output to low/high
 - ◆ X (F3) and Y (F5): require 0 switches, output is one of inputs
 - ◆ X' (F12) and Y' (F10): require 2 switches for "inverter" or NOT-gate
 - ◆ X **nor** Y (F4) and X **nand** Y (F14): require 4 switches
 - ◆ X **or** Y (F7) and X **and** Y (F1): require 6 switches
 - ◆ $X = Y$ (F9) and $X \oplus Y$ (F6): require 16 switches
 - ◆ thus, because **NOT**, **NOR**, and **NAND** are the cheapest they are the functions we implement the most in practice

Minimal Set of Functions

- Can we implement all logic functions from NOT, NOR, and NAND?
 - ◆ For example, implementing $X \text{ nor } Y$ is the same as implementing $\text{not } (X \text{ nand } Y)$
- In fact, we can do it with only NOR or only NAND
 - ◆ NOT is just a NAND or a NOR with both inputs tied together

X	Y	X nor Y
0	0	1
1	1	0

X	Y	X nand Y
0	0	1
1	1	0

- ◆ and NAND and NOR are "duals", that is, its easy to implement one using the other

$$X \text{ nand } Y \equiv \text{not } ((\text{not } X) \text{ nor } (\text{not } Y))$$

$$X \text{ nor } Y \equiv \text{not } ((\text{not } X) \text{ nand } (\text{not } Y))$$

- But learn this conversion later
 - ◆ Let's look at the mathematical foundation of logic

An Algebraic Structure

- An *algebraic structure* consists of
 - ◆ a set of elements B
 - ◆ binary operations $\{ + , \cdot \}$
 - ◆ and a unary operation $\{ ' \}$
 - ◆ such that the following axioms hold:

1. the set B contains at least two elements: a, b

2. closure: $a + b$ is in B

$a \cdot b$ is in B

3. commutativity: $a + b = b + a$

$a \cdot b = b \cdot a$

4. associativity: $a + (b + c) = (a + b) + c$

$a \cdot (b \cdot c) = (a \cdot b) \cdot c$

5. identity: $a + 0 = a$

$a \cdot 1 = a$

6. distributivity: $a + (b \cdot c) = (a + b) \cdot (a + c)$

$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$

7. complementarity: $a + a' = 1$

$a \cdot a' = 0$

Boolean Algebra

- Boolean algebra
 - ◆ $B = \{0, 1\}$
 - ◆ variables
 - ◆ $+$ is logical OR, \cdot is logical AND
 - ◆ $'$ is logical NOT
- All algebraic axioms hold

Logic Functions and Boolean Algebra

- Any logic function that can be expressed as a truth table can be written as an expression in Boolean algebra using the operators: ', +, and •

X	Y	$X \bullet Y$
0	0	0
0	1	0
1	0	0
1	1	1

X	Y	X'	$X' \bullet Y$
0	0	1	0
0	1	1	1
1	0	0	0
1	1	0	0

X	Y	X'	Y'	$X \bullet Y$	$X' \bullet Y'$	$(X \bullet Y) + (X' \bullet Y')$
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

$$(X \bullet Y) + (X' \bullet Y') \equiv X = Y$$

Boolean expression is true when the variables X and Y have the same value and false, otherwise

X, Y are Boolean algebra variables

Axioms/Theorems of Boolean Algebra

- identity

1. $X + 0 = X$

1D. $X \cdot 1 = X$

- null

2. $X + 1 = 1$

2D. $X \cdot 0 = 0$

- idempotency:

3. $X + X = X$

3D. $X \cdot X = X$

- involution:

4. $(X')' = X$

- complementarity:

5. $X + X' = 1$

5D. $X \cdot X' = 0$

- commutativity:

6. $X + Y = Y + X$

6D. $X \cdot Y = Y \cdot X$

- associativity:

7. $(X + Y) + Z = X + (Y + Z)$

7D. $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$

Axioms/Theorems of Boolean Algebra

- distributivity:

$$8. X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z) \quad 8D. X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

- uniting:

$$9. X \cdot Y + X \cdot Y' = X$$

$$9D. (X + Y) \cdot (X + Y') = X$$

- absorption:

$$10. X + X \cdot Y = X$$

$$10D. X \cdot (X + Y) = X$$

$$11. (X + Y') \cdot Y = X \cdot Y$$

$$11D. (X \cdot Y') + Y = X + Y$$

- factoring:

$$12. (X + Y) \cdot (X' + Z) = \\ X \cdot Z + X' \cdot Y$$

$$12D. X \cdot Y + X' \cdot Z = \\ (X + Z) \cdot (X' + Y)$$

- consensus:

$$13. (X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = \\ X \cdot Y + X' \cdot Z$$

$$13D. (X + Y) \cdot (Y + Z) \cdot (X' + Z) = \\ (X + Y) \cdot (X' + Z)$$

Axioms/Theorems of Boolean Algebra

- de Morgan's theorme:

$$14. (X + Y + \dots)' = X' \cdot Y' \cdot \dots \quad 14D. (X \cdot Y \cdot \dots)' = X' + Y' + \dots$$

- generalized de Morgan's:

$$15. f'(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) = f(X_1', X_2', \dots, X_n', 1, 0, \cdot, +)$$

- For any given Boolean EQ, its inverted EQ

- ◆ AND is changed into OR
- ◆ OR is changed into AND
- ◆ Each variable is changed into its inverted form

Axioms/Theorems of Boolean Algebra

■ *Duality*

- ◆ a dual of a Boolean expression is derived by replacing
• by +, + by •, 0 by 1, and 1 by 0, and leaving variables
unchanged
- ◆ any theorem that can be proven is thus *also true* for its dual!
- ◆ a meta-theorem (a theorem about theorems)

■ Duality:

$$16. X + Y + \dots \Leftrightarrow X \cdot Y \cdot \dots$$

■ Generalized duality:

$$17. f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$$

■ Different from deMorgan's Law

- ◆ this is a statement about theorems
- ◆ this is not a way to manipulate (re-write) expressions

Proving Theorems (rewriting)

- Using the axioms of Boolean algebra:

- ◆ e.g., prove the theorem: $X \cdot Y + X \cdot Y' = X$

distributivity (8)	$X \cdot Y + X \cdot Y'$	$=$	$X \cdot (Y + Y')$
complementarity (5)	$X \cdot (Y + Y')$	$=$	$X \cdot (1)$
identity (1D)	$X \cdot (1)$	$=$	$X \checkmark$
	$=$		$X \checkmark$

- ◆ e.g., prove the theorem: $X + X \cdot Y = X$

identity (1D)	$X + X \cdot Y$	$=$	$X \cdot 1 + X \cdot Y$
distributivity (8)	$X \cdot 1 + X \cdot Y$	$=$	$X \cdot (1 + Y)$
identity (2)	$X \cdot (1 + Y)$	$=$	$X \cdot (1)$
identity (1D)	$X \cdot (1)$	$=$	$X \checkmark$

Activity

- Prove the following using the laws of Boolean algebra:

- ◆ $(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Y + X' \cdot Z$

$$(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z)$$

identity

$$(X \cdot Y) + (1) \cdot (Y \cdot Z) + (X' \cdot Z)$$

complementarity

$$(X \cdot Y) + (X' + X) \cdot (Y \cdot Z) + (X' \cdot Z)$$

distributivity

$$(X \cdot Y) + (X' \cdot Y \cdot Z) + (X \cdot Y \cdot Z) + (X' \cdot Z)$$

commutativity

$$(X \cdot Y) + (X \cdot Y \cdot Z) + (X' \cdot Y \cdot Z) + (X' \cdot Z)$$

factoring

$$(X \cdot Y) \cdot (1 + Z) + (X' \cdot Z) \cdot (1 + Y)$$

null

$$(X \cdot Y) \cdot (1) + (X' \cdot Z) \cdot (1)$$

identity

$$(X \cdot Y) + (X' \cdot Z) \checkmark$$

Proving Theorems (perfect induction)

- Using perfect induction (complete truth table):
 - ◆ e.g., de Morgan's:

$(X + Y)' = X' \cdot Y'$
NOR is equivalent to AND
with inputs complemented


X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
NAND is equivalent to OR
with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

A Simple Example: 1-bit Binary Adder

 - Inputs: A , B , *Carry-in*
- Outputs: *Sum*, *Carry-out*



A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



$$S = A' B' \text{Cin} + A' B \text{Cin}' + A B' \text{Cin}' + A B \text{Cin}$$

$$\text{Cout} = A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin}$$

Apply Theorems to Simplify Expressions

- The theorems of Boolean algebra can simplify Boolean expressions
 - ◆ e.g., full adder's carry-out function (same rules apply to any function)

$$\begin{aligned} \text{Cout} &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + \boxed{A B \text{Cin} + A B \text{Cin}} \\ &= \textcolor{red}{A' B \text{Cin} + A B \text{Cin}} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= \textcolor{red}{(A' + A) B \text{Cin}} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= (1) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + \boxed{A B \text{Cin} + A B \text{Cin}} \\ &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + \textcolor{red}{A B \text{Cin} + A B \text{Cin}} \\ &= B \text{Cin} + \textcolor{red}{A (B' + B) Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + \textcolor{red}{A (1) Cin} + \textcolor{red}{A B \text{Cin}'} + \textcolor{red}{A B \text{Cin}} \\ &= B \text{Cin} + A \text{Cin} + \textcolor{red}{A B (\text{Cin}' + \text{Cin})} \\ &= B \text{Cin} + A \text{Cin} + A B (1) \\ &= B \text{Cin} + A \text{Cin} + A B \end{aligned}$$

adding extra terms
creates new factoring
opportunities

Activity

- Fill in the truth-table for a circuit that checks that a 4-bit number is divisible by 2, 3, or 5

X8	X4	X2	X1	By2	By3	By5
0	0	0	0	1	1	1
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	0	1	1	0	1	0

- Write down Boolean expressions for By2, By3, and By5

Activity

X8	X4	X2	X1	By2	By3	By5
0	0	0	0	1	1	1
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	1
0	1	1	0	1	1	0
0	1	1	1	0	0	0
1	0	0	0	1	0	0
1	0	0	1	0	1	0
1	0	1	0	1	0	1
1	0	1	1	0	0	0
1	1	0	0	1	1	0
1	1	0	1	0	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	1


$$\begin{aligned}
 \text{By2} &= X8'X4'X2'X1' + \\
 &X8'X4'X2X1' \\
 &\quad + X8'X4X2'X1' + X8'X4X2X1' \\
 &\quad + X8X4'X2'X1' + X8X4'X2X1' \\
 &\quad + X8X4X2'X1' + X8X4X2X1' \\
 &= X1'
 \end{aligned}$$

$$\begin{aligned}
 \text{By3} &= X8'X4'X2'X1' + X8'X4'X2X1 \\
 &\quad + X8'X4X2X1' + X8X4'X2'X1 \\
 &\quad + X8X4X2'X1' + X8X4X2X1
 \end{aligned}$$

$$\begin{aligned}
 \text{By5} &= X8'X4'X2'X1' + X8'X4X2'X1 \\
 &\quad + X8X4'X2X1' + X8X4X2X1
 \end{aligned}$$

Boolean Expressions to Logic Gates

■ NOT X' \underline{X} $\sim X$

 


X	Y
0	1
1	0

■ AND $X \cdot Y$ XY $X \wedge Y$



X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1


■ OR $X + Y$ $X \vee Y$

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1


Boolean Expressions to Logic Gates

■ NAND

 

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

■ NOR

 

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0


■ XOR $X \oplus Y$



X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

$X \text{ xor } Y = X Y' + X' Y$
 X or Y but not both
 ("inequality", "difference")

■ XNOR $X = Y$

 


X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

$X \text{ xnor } Y = X Y + X' Y'$
 X and Y are the same
 ("equality", "coincidence")

Boolean Expressions to Logic Gates

- More than one way to map expressions to gates

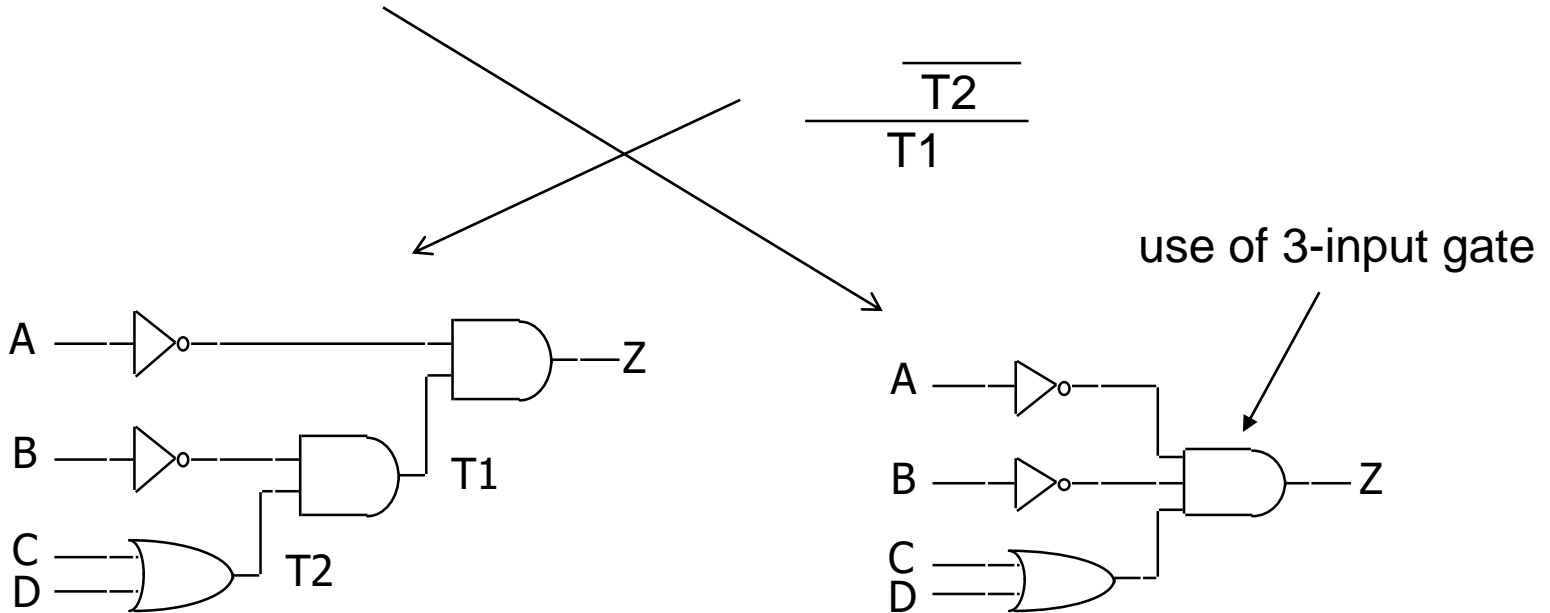
◆ e.g., $Z = A' \cdot B' \cdot (C + D) = (A' \cdot (B' \cdot (C + D)))$



Literal: each appearance of a variable or its complement in an expression

Waveform View of Logic Functions

 
- Just another way for truth table
 - ◆ but note how edges don't line up exactly
 - ◆ it takes time for a gate to switch its output!



change in Y takes time to "propagate" through gates

Different Realizations of a Function

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

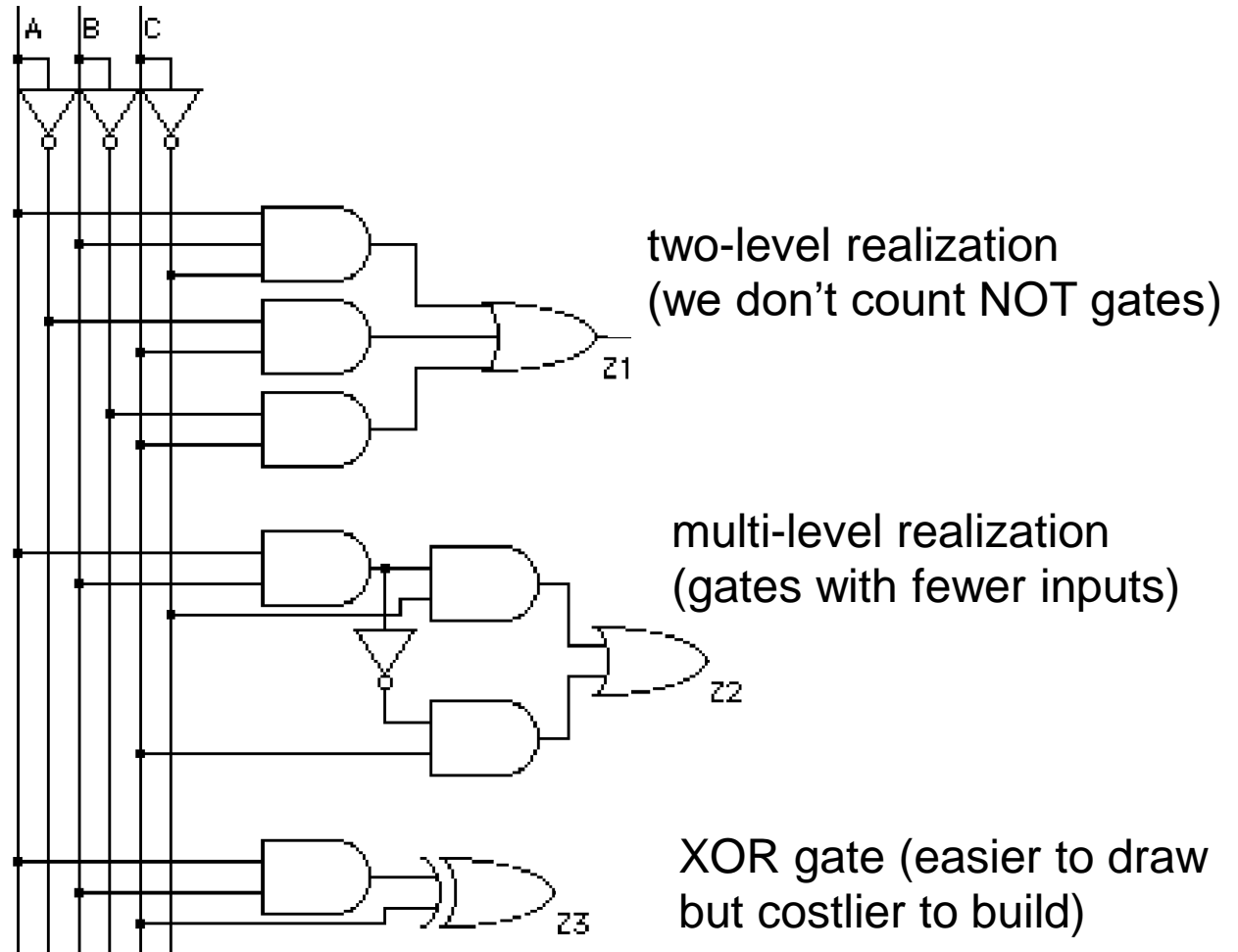

Different Realizations of a Function

$$Z = A'B'C + A'BC + AB'C + ABC'$$

$$\begin{aligned} Z1 &= A' C (B'+B) + AB'C + ABC' && (5, B'+B = 1, \text{Complementarity}) \\ &= A' C + AB'C + ABC' \\ &= C (A' + AB') + ABC' && (8D, \text{Distributive law}) \\ &= C ((A' + A) (A' + B')) + ABC' && (5, A'+A = 1, \text{Complementarity}) \\ &= C (A' + B') + ABC' \\ &= ABC' + A' C + B'C \end{aligned}$$

$$\begin{aligned} Z2 &= ABC' + A' C + B'C \\ &= ABC' + C (A' + B') \\ &= ABC' + C (AB)' && (12, A' + B' = (AB)', \text{DeMorgan's Law}) \end{aligned}$$

$$\begin{aligned} Z3 &= ABC' + C (AB)' && (X=AB, Y= C,) \\ &= AB \oplus C \end{aligned}$$

Which Realization is Best?


- Reduce number of inputs
 - ◆ literal: input variable (complemented or not)
 - can approximate the cost of logic gate as 2 transistors per literal
 - why not count inverters?
 - ◆ fewer literals means less transistors
 - smaller circuits
 - ◆ fewer inputs implies faster gates
 - gates are smaller and thus also faster
 - ◆ fan-ins (# of gate inputs) are limited in some technologies
- Reduce number of gates
 - ◆ fewer gates (and the packages they come in) means smaller circuits
 - directly influences manufacturing costs

Which is the Best Realization?

- *Reduce number of levels of gates*
 - ◆ fewer level of gates implies reduced signal propagation delays
 - ◆ minimum delay configuration typically requires more gates
 - wider, less deep circuits
- How do we explore tradeoffs between increased circuit delay and size?
 - ◆ automated tools to generate different solutions
 - ◆ logic minimization: reduce number of gates and complexity
 - ◆ logic optimization: reduce while trading off against delay

Are all Realizations Equivalent?

 - Under the same input stimuli, three alternative implementations have almost the same waveform behavior
 - ◆ delays are different
 - ◆ glitches (hazards) may arise – these could be bad, it depends
 - ◆ variations due to differences in number of gate levels and structure
- The three implementations are functionally equivalent



Implementing Boolean Functions

- Technology independent
 - ◆ canonical forms
 - ◆ two-level forms
 - ◆ multi-level forms
- Technology choices
 - ◆ packages of a few gates
 - ◆ regular logic
 - ◆ two-level programmable logic
 - ◆ multi-level programmable logic

Canonical Forms

- Truth table is the unique signature of a Boolean function
- The same truth table can have many gate realizations
- *Canonical forms*
 - ◆ standard forms for a Boolean expression
 - ◆ provides a unique algebraic signature

Sum-of-products Canonical Forms

- Also known as disjunctive normal form
- Also known as minterm expansion

			F =		001	011	101	110	111
			F =		A'B'C	+ A'BC	+ AB'C	+ ABC'	+ ABC
A	B	C	F	F'					
0	0	0	0	1					
0	0	1	1	0					
0	1	0	0	1					
0	1	1	1	0					
1	0	0	0	1					
1	0	1	1	0					
1	1	0	1	0					
1	1	1	1	0					

F' = A'B'C' + A'BC' + AB'C'


Sum-of-products Canonical Form

■ Product term (or minterm)

- ◆ ANDed product of literals – input combination for which output is true
- ◆ each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms	
0	0	0	$A'B'C'$	m0
0	0	1	$A'B'C$	m1
0	1	0	$A'BC'$	m2
0	1	1	$A'BC$	m3
1	0	0	$AB'C'$	m4
1	0	1	$AB'C$	m5
1	1	0	ABC'	m6
1	1	1	ABC	m7

short-hand notation for
minterms of 3 variables



F in canonical form:

$$\begin{aligned}
 F(A, B, C) &= \Sigma m(1,3,5,6,7) \\
 &= m1 + m3 + m5 + m6 + m7 \\
 &= A'B'C + A'BC + AB'C + ABC' + ABC
 \end{aligned}$$

canonical form \neq minimal form

$$\begin{aligned}
 F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\
 &= (A'B' + A'B + AB' + AB)C + ABC' \\
 &= ((A' + A)(B' + B))C + ABC' \\
 &= C + ABC' \\
 &= ABC' + C \\
 &= AB + C
 \end{aligned}$$

Product-of-sums Canonical Form

- Also known as conjunctive normal form
- Also known as maxterm expansion

					$F =$	000	010	100
					$F =$	$(A + B + C)$	$(A + B' + C)$	$(A' + B + C)$
A	B	C	F	F'				
0	0	0	0	1				
0	0	1	1	0				
0	1	0	0	1				
0	1	1	1	0				
1	0	0	0	1				
1	0	1	1	0				
1	1	0	1	0				
1	1	1	1	0				


$$F' = (A + B + C') (A + B' + C') (A' + B + C') (A' + B' + C) (A' + B' + C')$$

Product-of-sums Canonical Form

- Sum term (or maxterm)
 - ◆ ORed sum of literals – input combination for which output is false
 - ◆ each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms	
0	0	0	$A+B+C$	M0
0	0	1	$A+B+C'$	M1
0	1	0	$A+B'+C$	M2
0	1	1	$A+B'+C'$	M3
1	0	0	$A'+B+C$	M4
1	0	1	$A'+B+C'$	M5
1	1	0	$A'+B'+C$	M6
1	1	1	$A'+B'+C'$	M7

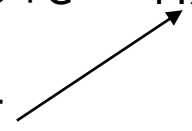short-hand notation for
maxterms of 3 variables



F in canonical form:

$$\begin{aligned}
 F(A, B, C) &= \prod M(0,2,4) \\
 &= M0 \bullet M2 \bullet M4 \\
 &= (A + B + C) (A + B' + C) (A' + B + C)
 \end{aligned}$$

canonical form \neq minimal form

$$\begin{aligned}
 F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\
 &= (A + B + C) (A + B' + C) \\
 &\quad (A + B + C) (A' + B + C) \\
 &= (A + C) (B + C)
 \end{aligned}$$

S-o-P, P-o-S, and de Morgan's Theorem

- Sum-of-products

- ◆ $F' = A'B'C' + A'BC' + AB'C' \rightarrow F' \text{ in SOP}$

- Apply de Morgan's

- ◆ $(F')' = (A'B'C' + A'BC' + AB'C')' = (A'B'C')' \cdot (A'BC')' \cdot (AB'C')'$

- ◆ $F = (A + B + C)(A + B' + C)(A' + B + C)$
 $\rightarrow F \text{ in POS}$

- Product-of-sums $\rightarrow F' \text{ in POS}$


- ◆ $F' = (A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C')$

- Apply de Morgan's

- ◆ $(F')' = ((A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C'))'$
 $= (A + B + C')' + (A + B' + C')' + (A' + B + C')' + (A' + B' + C)' + (A' + B' + C)'$


- ◆ $F = A'B'C + A'BC + AB'C + ABC' + ABC$
 $\rightarrow F \text{ in SOP}$

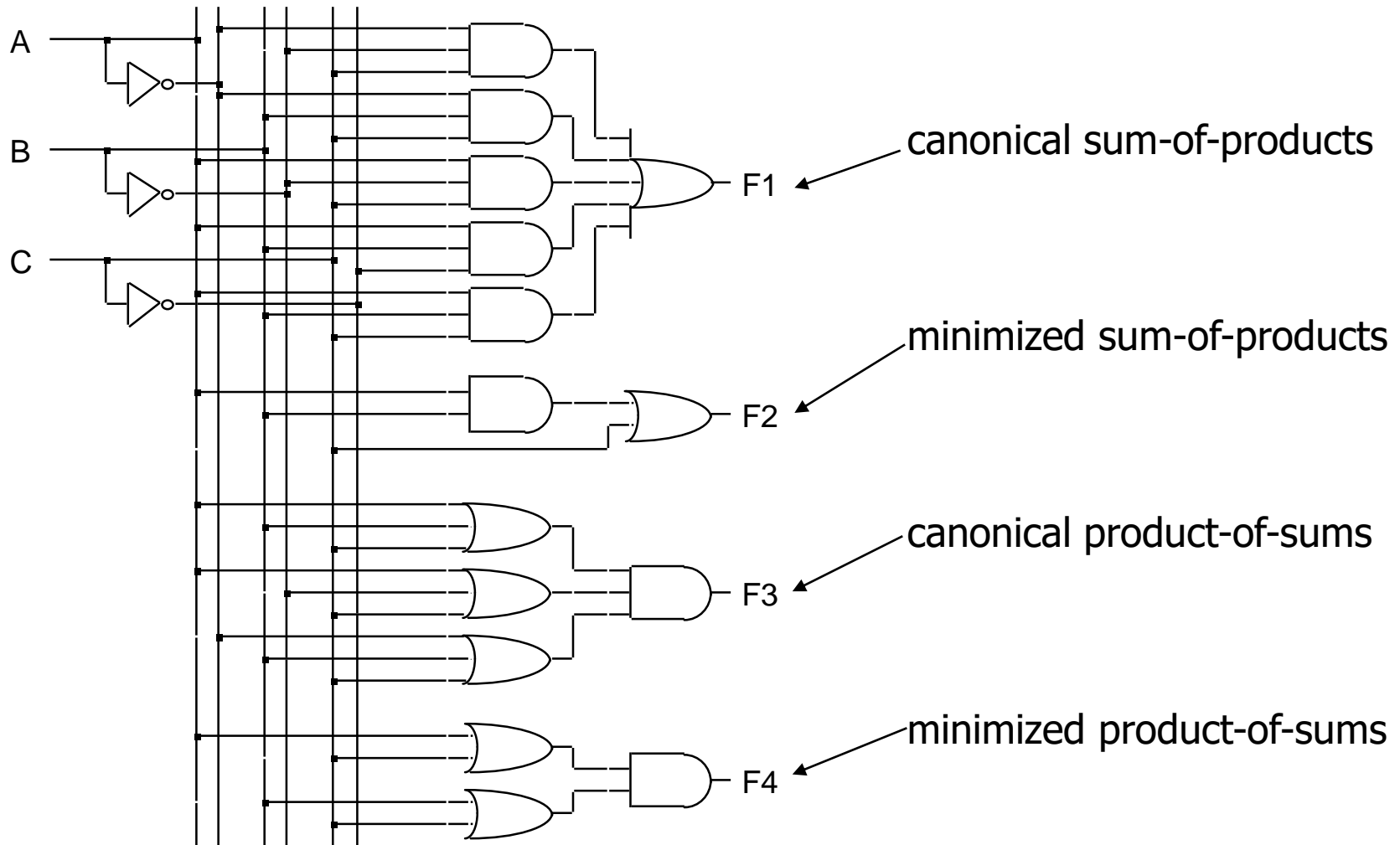Four 2-level implementations: $F = AB + C$



Waveforms for the Four Alternatives

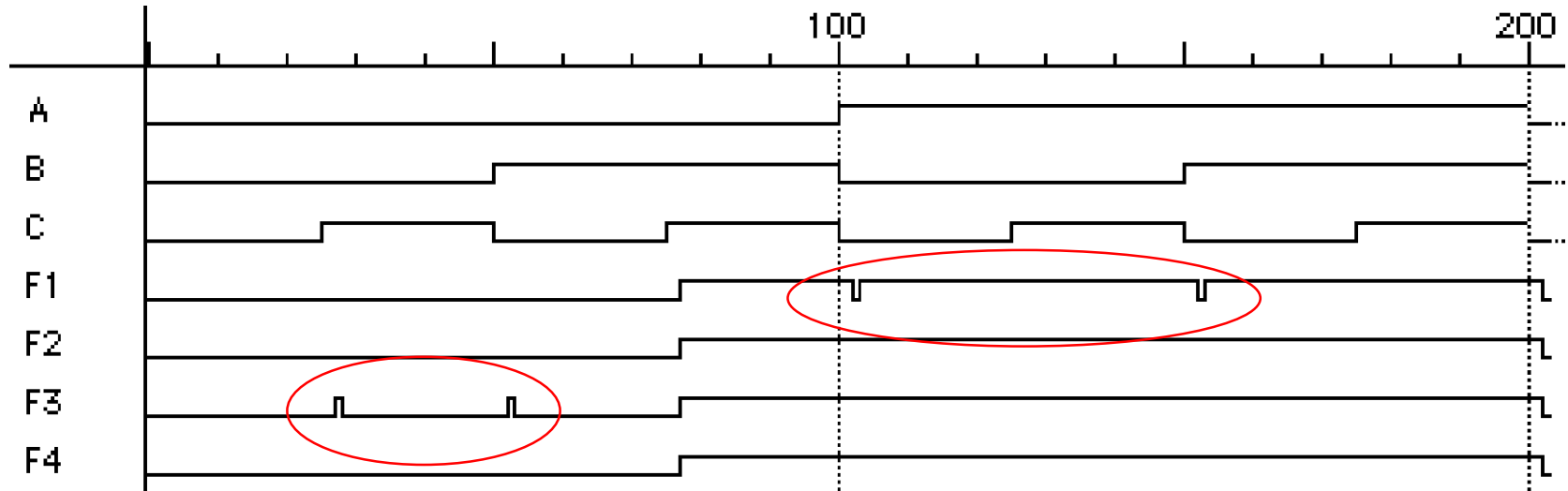- Waveforms are essentially identical
 - ◆ except for timing hazards (glitches)
 - ◆ delays almost identical (modeled as a delay per level, not type of gate or number of inputs to gate)



Mapping between Canonical Forms

- Minterm to maxterm conversion
 - ◆ use maxterms whose indices do not appear in minterm expansion
 - ◆ e.g., $F(A,B,C) = \sum m(1,3,5,6,7) = \prod M(0,2,4)$
- Maxterm to minterm conversion
 - ◆ use minterms whose indices do not appear in maxterm expansion
 - ◆ e.g., $F(A,B,C) = \prod M(0,2,4) = \sum m(1,3,5,6,7)$
- Minterm expansion of F to minterm expansion of F'
 - ◆ use minterms whose indices do not appear
 - ◆ e.g., $F(A,B,C) = \sum m(1,3,5,6,7) \quad F'(A,B,C) = \sum m(0,2,4)$
- Maxterm expansion of F to maxterm expansion of F'
 - ◆ use maxterms whose indices do not appear
 - ◆ e.g., $F(A,B,C) = \prod M(0,2,4) \quad F'(A,B,C) = \prod M(1,3,5,6,7)$

Incompletely Specified Functions

■ Example: binary coded decimal increment by 1

- ◆ BCD digits encode the decimal digits 0 – 9
in the bit patterns 0000 – 1001

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

off-set of W

on-set of W

don't care (DC) set of W

these inputs patterns should
never be encountered in practice
– **"don't care"** about associated
output values, can be exploited
in minimization

Notation for Incompletely Specified Fts

- Don't cares and canonical forms
 - ◆ so far, only represented on-set
 - ◆ need two of the three sets (on-set, off-set, dc-set)
- Canonical representations of the BCD increment by 1 function:
 - ◆ $Z = m_0 + m_2 + m_4 + m_6 + m_8 + d_{10} + d_{11} + d_{12} + d_{13} + d_{14} + d_{15}$
 - ◆ $Z = \Sigma [m(0,2,4,6,8) + d(10,11,12,13,14,15)]$
 - ◆ $Z = M_1 \cdot M_3 \cdot M_5 \cdot M_7 \cdot M_9 \cdot D_{10} \cdot D_{11} \cdot D_{12} \cdot D_{13} \cdot D_{14} \cdot D_{15}$
 - ◆ $Z = \Pi [M(1,3,5,7,9) \cdot D(10,11,12,13,14,15)]$

Simplification of 2-level Combi-Logic

- Finding a minimal sum of products or product of sums realization
 - ◆ exploit don't care information in the process
- Algebraic simplification
 - ◆ not an algorithmic/systematic procedure
 - ◆ how do you know when the minimum realization has been found?
- Computer-aided design tools
 - ◆ precise solutions require very long computation times, especially for functions with many inputs (> 10)
 - ◆ heuristic methods employed – "educated guesses" to reduce amount of computation and yield good if not best solutions
- Hand methods still relevant
 - ◆ to understand automatic tools and their strengths and weaknesses
 - ◆ ability to check results (on small examples)

The Uniting Theorem

- Key tool to simplification: $A (B' + B) = A$
- Essence of simplification of two-level logic
 - ◆ find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements

$$F = A'B' + AB' = (A' + A)B' = B'$$





A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

B has the same value in both on-set rows
– B remains

A has a different value in the two rows
– A is eliminated

Boolean Cubes

    
- Visual technique for indentifying when the uniting theorem can be applied
- n input variables = n -dimensional "cube"



Mapping Truth Tables to Boolean Cubes

- Uniting theorem combines two "faces" of a cube into a larger "face"
- Example:

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

 


ON-set = solid nodes
OFF-set = empty nodes
DC-set = x'd nodes

Three Variable Example

- Binary full-adder carry-out logic

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 


the on-set is completely covered by the combination (OR) of the subcubes of lower dimensionality - note that "111" is covered three times

$$Cout = BCin + AB + ACin$$

Higher Dimensional Cubes

- Sub-cubes of higher dimension than 2

 

$$F(A,B,C) = \sum m(4,5,6,7)$$

on-set forms a square
i.e., a cube of dimension 2

*represents an expression in one variable
i.e., 3 dimensions – 2 dimensions*

A is asserted (true) and unchanged
B and C vary

This subcube represents the
literal A

m-dimensional Cubes

- In a 3-cube (three variables):
 - ◆ a 0-cube, i.e., a single node, yields a term in 3 literals
 - ◆ a 1-cube, i.e., a line of two nodes, yields a term in 2 literals
 - ◆ a 2-cube, i.e., a plane of four nodes, yields a term in 1 literal
 - ◆ a 3-cube, i.e., a cube of eight nodes, yields a constant term "1"
- In general,
 - ◆ an m -subcube within an n -cube ($m < n$) yields a term with $n - m$ literals

Karnaugh Maps

- Flat map of Boolean cube
 - ◆ wrap-around at edges
 - ◆ hard to draw and visualize for more than 4 dimensions
 - ◆ virtually impossible for more than 6 dimensions
- Alternative to truth-tables to help visualize adjacencies
 - ◆ guide to applying the uniting theorem
 - ◆ on-set elements with only one variable changing value are adjacent unlike the situation in a linear truth-table

		A	
		0	1
B	0	0 1	2 1
	1	1 0	3 0

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

Karnaugh Maps

- Numbering scheme based on Gray-code
 - ◆ e.g., 00, 01, 11, 10
 - ◆ only a single bit changes in code for adjacent map cells

		AB			
		00	01	11	10
C	0	0	2	6	4
	1	1	3	7	5

B

		AB			
		00	01	11	10
C	0	0	2	6	4
	1	1	3	7	5

B



		AB			
		00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
C	11	3	7	15	11
	10	2	6	14	10

B

$$13 = 1101 = ABC'D$$

Adjacencies in Karnaugh Maps

  - Wrap from first to last column
- Wrap top row to bottom row



Karnaugh Map Examples

■ $F =$

■ $C_{out} =$

■ $f(A,B,C) = \Sigma m(0,4,5,7)$

	0	1
A		
0	1	1
1	0	0
B		

B'

	00	01	11	10
AB				
0	0	0	1	0
1	0	1	1	1
Cin				
			B	

$AB + AC_{in} + BC_{in}$

	00	01	11	10
AB				
0	1	0	0	1
1	0	0	1	1
C				
			B	

$AC + B'C' + AB'$

obtain the complement of the function by covering 0s with subcubes

More Karnaugh Map Examples

		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	0	1	1

B

$$G(A,B,C) = A$$

		AB			
		00	01	11	10
C	0	1	0	0	1
	1	0	0	1	1

B

$$F(A,B,C) = \sum m(0,4,5,7) = AC + B'C'$$

		AB			
		00	01	11	10
C	0	0	1	1	0
	1	1	1	0	0

B

F' simply replace 1's with 0's and vice versa

$$F'(A,B,C) = \sum m(1,2,3,6) = BC' + A'C$$

Karnaugh map: 4-variable Example


■ $F(A,B,C,D) = \Sigma m(0,2,3,5,6,7,8,10,11,14,15)$

$F =$

$$C + A'BD + B'D'$$

AB \ CD	00	01	11	10
00	1	0	0	1
01	0	1	0	0
11	1	1	1	1
10	1	1	1	1

Diagram labels: A is above the last two columns (11, 10); B is below the last two columns (11, 10); C is to the left of the last two rows (11, 10); D is to the right of the last two rows (11, 10).

 

find the smallest number of the largest possible
subcubes to cover the ON-set
(fewer terms with fewer inputs per term)


Karnaugh Maps: don't cares

■ $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$

◆ without don't cares

□ $f =$

$$A'D + B'C'D$$

 

Karnaugh Maps: don't cares

■ $f(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$

◆ $f = A'D + B'C'D$

without don't cares

◆ $f =$

with don't cares

$A'D + C'D$


AB		00	01	11	10
CD	A				
	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
C	10	0	X	0	0
	B				

by using don't care as a "1"
a 2-cube can be formed
rather than a 1-cube to cover
this node

don't cares can be treated as
1s or 0s
depending on which is more
advantageous

Activity

 
- Minimize the function $F = \sum m(0, 2, 7, 8, 14, 15) + d(3, 6, 9, 12, 13)$



$$F = \cancel{AC'} + \cancel{A'C} + \cancel{BC} + \cancel{AB} + \cancel{A'B'D'} + \cancel{B'C'D'}$$

$$F = BC + A'B'D' + B'C'D'$$

$$F = A'C + AB + B'C'D'$$

 

Combinational Logic Summary

- Logic functions, truth tables, and switches
 - ◆ NOT, AND, OR, NAND, NOR, XOR, . . . , minimal set
- Axioms and theorems of Boolean algebra
 - ◆ proofs by re-writing and perfect induction
- Gate logic
 - ◆ networks of Boolean functions and their time behavior
- Canonical forms
 - ◆ two-level and incompletely specified functions
- Simplification
 - ◆ a start at understanding two-level simplification
- Later
 - ◆ automation of simplification
 - ◆ multi-level logic
 - ◆ time behavior
 - ◆ hardware description languages
 - ◆ design case studies