 


### Exercise 3.1


(a)  $f(V,W,X,Y,Z) = \prod M(0,4,18,19,22,23,25,29)$



The simplified function has 11 literals:

$$f = WY + V'W'Y + V'Z + V'Y + WZ'$$

 (b)  $f(A,B,C,D) = \sum m(0,1,4,5,12,13)$



The simplified function has 4 literals:

$$f = A'C' + BC'$$

(c)  $f(A,B,C,D,E) = \sum m(0,4,18,19,22,23,25,29)$


		BC			
A=0	DE	00	01	11	10
	00	1	1		
	01				
	11				
	10				

		BC			
A=1	DE	00	01	11	10
	00				
	01			1	1
	11	1	1		
	10	1	1		

The simplified function has 11 literals:

$$f = AB'D + A'B'D'E' + ABD'E$$

 (d)  $f(A,B,C,D,E,F) = \sum m(3,7,12,14,15,19,23,27,28,29,31,35,39,44,45,46,48,49,50,52,53,55,56,57,59)$



The simplified function has 46 literals:

$$f = A'C'EF + C'DEF + B'CDF + A'DEF + A'BCDE' + BCD'EF' + ABC'E' + ABD'E' + ABC'D'EF' + AB'CDE' + AB'C'EF$$

### **Exercise 3.2**

(a) The following are prime implicants:

$$WY, V'W'Y, V'Z, V'Y, WZ'$$

All of the elements are also essential primes because they each contain a '1' that is not covered by any of the other elements.

(b) The following are prime implicants:

$$A'C', BC'$$

Both of the elements are also essential primes because they each contain a '1' that is not covered by any of the other elements.

(c) The following are prime implicants:

$$AB'D, A'B'D'E', ABD'E$$

All of the elements are also essential primes because they each contain a '1' that is not covered by any of the other elements.


(d) The following are prime implicants:

$$A'C'EF, C'DEF, B'CDF, A'DEF, A'BCDE', BCD'EF', ABC'E', ABD'E', \\ ABC'D'EF', AB'CDE', AB'C'EF$$

All of the elements are also essential primes because they each contain a '1' that is not covered by any of the other elements.

### Exercise 3.3

 
(a)  $f(W,X,Y,Z) = \prod M(4,7,8,11) * \prod D(1,2,13,14)$



The simplified function is:

$$f = A'B' + AB + C'D + CD'$$

 
(b)  $f(A,B,C,D) = \sum m(0,1,4,10,11,14) + \sum d(5,15)$



The simplified function is:

$$f = A'C' + AC$$

 
(c)  $f(A,B,C,D) = \sum m(1,2,3,5,8,13) + \sum d(0)$



The simplified function is:

$$f = A'B' + B'C'D' + BC'D$$

 (d)  $f(A,B,C,D,E) = \sum m(3,7,12,14,15,19,23,27,28,29,31) + \sum d(4,5,6,13,30)$



The simplified function is:

$$f = A'C + B'DE + BCE' + AC'DE$$

### **Exercise 3.4**

(a) The following are prime implicants:

$$A'B', AB, C'D, CD'$$

All of the elements are also essential primes because they each contain a '1' that is not covered by any of the other elements.

In this function, all of the don't-cares are set to one.

(b) The following are prime implicants:

$$A'C', AC$$

All of the elements are also essential primes because they each contain a '1' that is not covered by any of the other elements.

In this function, both of the don't-cares are set to one.

(c) The following are prime implicants:

$$A'B', B'C'D', BC'D$$

All of the elements are also essential primes because they each contain a '1' that is not covered by any of the other elements.

In this function, the single don't-care was set to one.

(d) The following are prime implicants:

$$A'C, B'DE, BCE', AC'DE$$

All of the elements are also essential primes because they each contain a '1' that is not covered by any of the other elements.

In this function, all of the don't-cares are set to one.

### Exercise 3.5

(a)  $F(A,B,C) = \sum m(1,2,6,7)$

C \ AB	AB			
	00	01	11	10
00		1	1	
01	1		1	

The simplified function is:

$$F = BC' + AB + A'B'C$$

(b)  $F(A,B,C,D) = \sum m(0,1,3,9,11,12,14,15)$

CD \ AB	AB			
	00	01	11	10
00	1		1	
01	1			1
11	1		1	1
10			1	

The simplified function is:

$$F = B'D + A'B'C' + ACD + ABD'$$



(c)  $F(A,B,C,D) = \sum m(2,4,5,6,7,8,10,13)$

AB \ CD	00	01	11	10
00		0		0
01		0	0	
11		0		
10	0	0		0

The simplified function is:

$$F = A'B + BC'D + A'CD' + AB'D$$

(d)  $F(A,B,C,D) = (ABC + A'B')(C + D)$

AB \ CD	00	01	11	10
00				
01	1			
11	1		1	
10	1		1	

The simplified function is:

$$F = ABC + A'B'C + A'B'D$$

(e)  $F(A,B,C,D) = (A' + B + C)(A + B + C' + D)(A + B' + C + D)(A' + B')$


AB \ CD		00	01	11	10
CD	00		1	1	1
	01			1	1
	11			1	
	10	1		1	

The simplified function is:

$$F = AC' + AB + BC'D' + A'B'CD'$$

### Exercise 3.6

(a)  $f(X,Y,Z) = \Sigma m(2,3,4,5)$

 

The resulting simplified function is:

$$f = X'Y + XY'$$

(b)  $f(A,B,C,D) = \Sigma m(1,5,7,8,9,13,15) + \Sigma d(4,12,14)$

Column 1	Column 2	Column 3
0001√	0-01√	--01*
0100√	-001√	-10-*
1000√	010-√	1-0-*
	-100√	
0101√	100-√	-1-1*
1001√	1-00√	11--*
1100√		
	01-1√	
0111√	-101√	
1101√	1-01√	
1110√	110-√	
	11-0√	
1111√		
	-111√	
	11-1√	
	111-√	

√ implicant  
\* prime implicant

	1	5	7	8	9	13	15
12,13,14,15 (11--)						X	X
1,5,7,9,13,15 (--01)	X	X	X		X	X	X
4,5,12,13 (-10-)		X				X	
5,7,13,15 (-1-1)		X	X			X	X
8,9,12,13 (1-0-)				X	X	X	

Initial prime implicant chart

	1	5	7	8	9	13	15
12,13,14,15 (11--)						X	X
1,5,7,9,13,15 (--01)	X	X	X		X	X	X
4,5,12,13 (-10-)		X				X	
5,7,13,15 (-1-1)		X	X			X	X
8,9,12,13 (1-0-)				X	X	X	

Final configuration

The resulting simplified function is:

$$f = AB + C'D + AC'$$

(c)  $f(A,B,C,D) = \sum m(1,2,3,4,5,6,7,8,9,10,11,12)$

Column 1	Column 2	Column 3
0001√	00-1√	0--1*
0010√	0-01√	-0-1*
0100√	-001√	0-1-*
1000√	001-√	-01-*
	0-10√	
0011√	-010√	01--*
0101√	01-0√	10--*
0110√	-100√	
1001√	100-√	
1010√	10-0√	
1100√	1-00√	
0111√	0-11√	

	1011√	-011√	01-1√	011-√	10-1√	101-√						
	√ implicant * prime implicant											
	1	2	3	4	5	6	7	8	9	10	11	12
1,3,5,7 (0--1)	X		X		X		X					
1,3,9,11 (-0-1)	X		X						X			X
2,3,6,7 (0-1-)		X	X			X	X					
2,3,10,11 (-01-)		X	X							X	X	
4,5,6,7 (01--)				X	X	X	X					
8,9,10,11 (10--)								X	X	X	X	
4,12 (-100)				X								X
8,12 (1-00)								X				

Initial prime implicant chart

	1	2	3	4	5	6	7	8	9	10	11	12
1,3,5,7 (0--1)	X		X		X		X					
1,3,9,11 (-0-1)	X		X						X			X
2,3,6,7 (0-1-)		X	X			X	X					
2,3,10,11 (-01-)		X	X							X	X	
4,5,6,7 (01--)				X	X	X	X					
8,9,10,11 (10--)								X	X	X	X	
4,12 (-100)				X								X
8,12 (1-00)								X				

Final configuration

The resulting simplified function is:

$$f = B'D + B'C + A'B + AC'D'$$


(d)  $f(A,B,C,D) = \Sigma m(1,2,3,4,9,10,11,12) + \Sigma d(0,13,14,15)$

Column 1	Column 2	Column 3
0000√	000-√	00--*
	00-0*	
0001√	0-00*	-0-1*
0010√		-01-*
0100√	-001√	
	-010√	1--1*
0011√	001-√	11--*
1001√	-100*	
1010√		
1100√	-0-11√	
	10-1√	
1011√	1-01√	
1101√	110-√	
1110√	11-0√	
1111√	1-11√	
	11-1√	
	111-√	

√ implicant  
\* prime implicant

	1	2	3	4	9	10	11	12
2 (00-0)		X						
4 (0-00)				X				
4,12 (-100)				X				X
1,2,3 (00--)	X	X	X					
1,3,9,11 (-0-1)	X		X		X		X	
2,3,10,11 (-01-)		X	X			X	X	
9,11 (1--1)					X		X	
12 (11--)								X

Initial prime implicant chart

 


The resulting simplified function is:


$$f = BC'D' + B'D + B'C$$

### Exercise 3.8


(a)  $F(A,B,C,D) = (ABC + A'B')(C + D)$

 

Initial Circuit

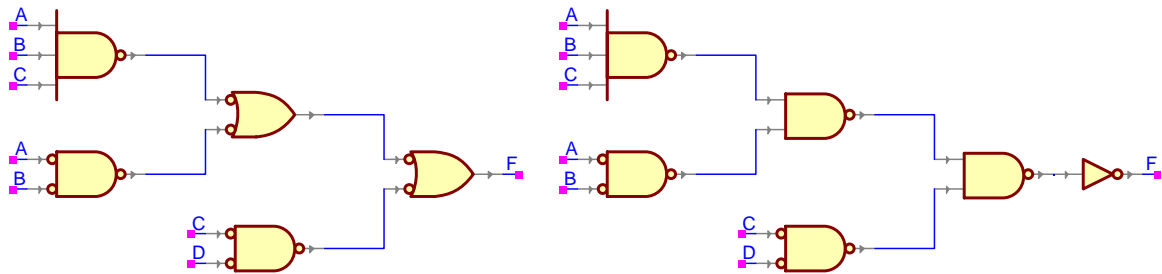




NAND Gate Implementation

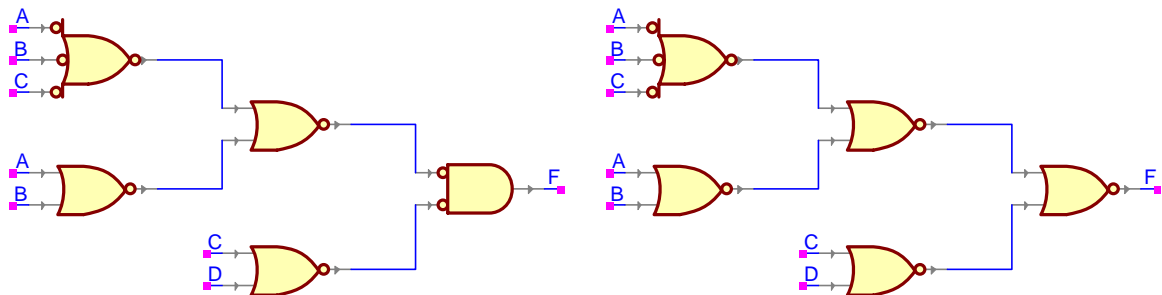


NOR Gate Implementation



 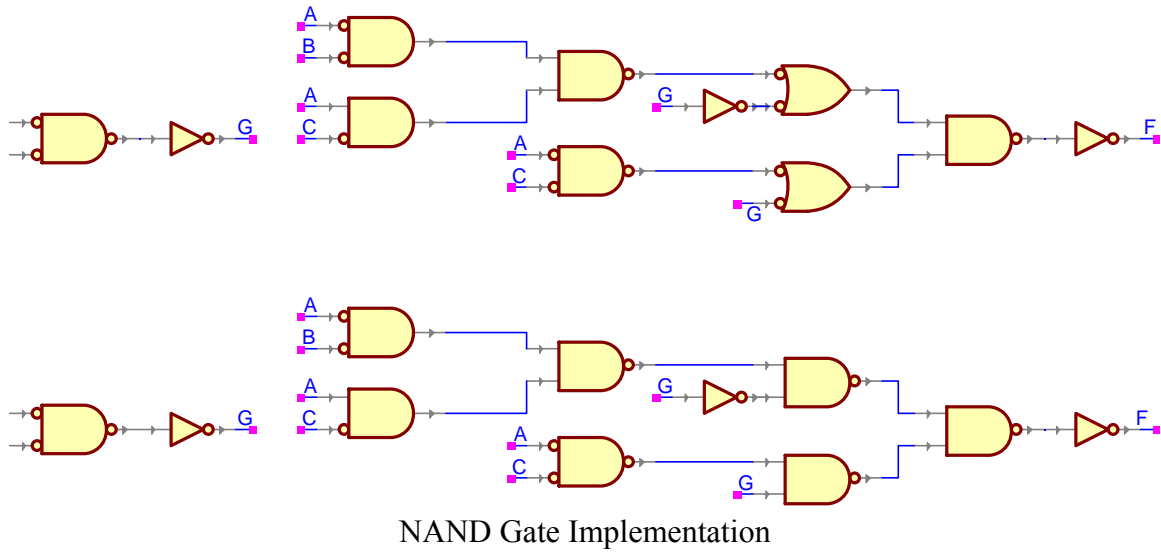 
(b)  $G(B,C) = B'C'$       $F(A,B,C,G) = [(A + B)(A' + C) + G](A'C' + G)$



 
(c)  $F(A,B,C,D) = [(A' + B' + C)(B + C')(A + B' + D')] + ACD' + BC'D$



Initial Circuit

 


NAND Gate Implementation


 


NOR Gate Implementation

 
(d)  $H(A,B) = A + B'$     $G(B,C,D) = BC' + D$     $F(A,B,G,H) = (A + G)(B + H)'$



Initial Circuit

  


NAND Gate Implementation

 


NOR Gate Implementation

### Exercise 3.9

(a)  $F = AB'C' + A'C + A'B$

 


Initial Circuit

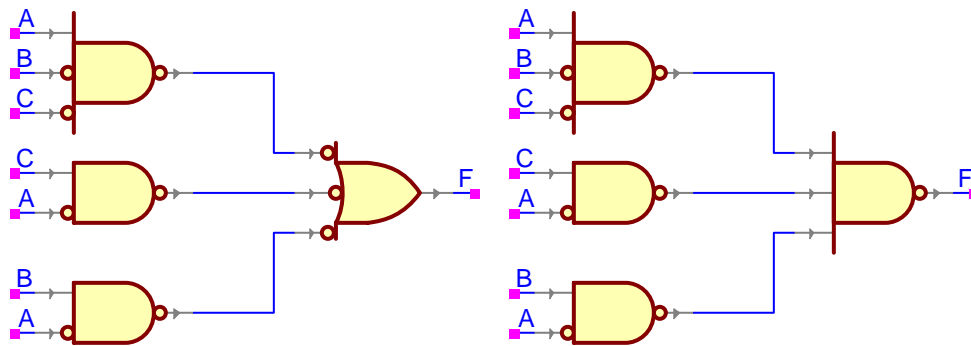


NAND Gate Implementation

 (b)  $F = (A' + B' + C')(A' + B')(A' + C')$




Initial Circuit

 


NAND Gate Circuit

(c)  $F = A'B + A + C' + D'$

 


Initial Circuit

 


NAND Gate Implementation

(d)  $F = (AB)'(A'C)'$

 


Initial Circuit

 


NAND Gate Implementation

(e)  $F = (AB + A'C')'$

 


Initial Circuit

 


NAND Gate Implementation

### Exercise 3.10

(a)  $F = (A + B)(A' + C)$

 


Initial Circuit

 


NOR Gate Implementation

(b)  $F = [(A + B)(A' + C)]'$

 


Initial Circuit

 


NOR Gate Implementation

(c)  $F = (A + B)'(A' + C)'$

 


Initial Circuit

 


NOR Gate Implementation

(d)  $F = (A + B)(A' + C + D)(A' + C')$

 


Initial Circuit

 


NOR Gate Implementation

(e)  $F = (A + B)(B' + C)(A' + C')$

 

Initial Circuit




 


NOR Gate Implementation

### Exercise 3.11

 
(a)  $F(A,B,C_{in}) = AB + BC_{in} + AC_{in}$



Initial Circuit

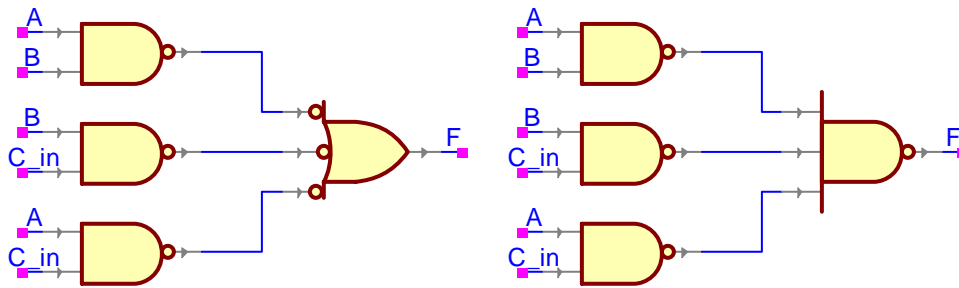


NAND Gate Implementation

 


NOR Gate Implementation

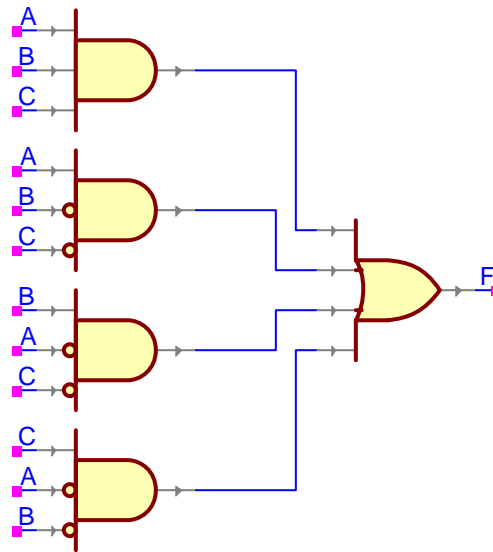
(b)  $F(A,B,C_{in}) = A \text{ xor } B \text{ xor } C_{in}$



Initial Circuit

 

NAND Gate Implementation

 

NOR Gate Implementation

(c) The function,  $F$ , is true when the 2-bit value  $AB$  is strictly less than the 2-bit quantity  $CD$ .


Truth table for  $F$ :

A	B	C	D	$F(AB < CD)$
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0


K-map for F:

CD \ AB	AB			
	00	01	11	10
00				
01	1			
11	1	1		1
10	1	1		1


$$F = A'C + A'B'D + B'CD$$

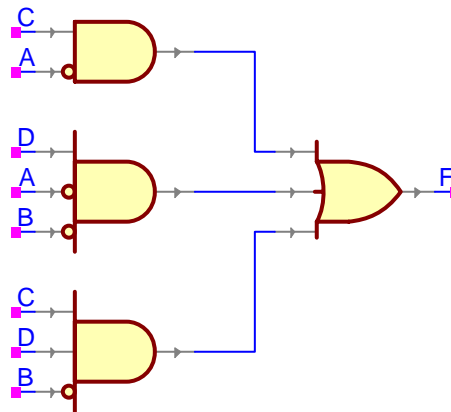

Initial Circuit

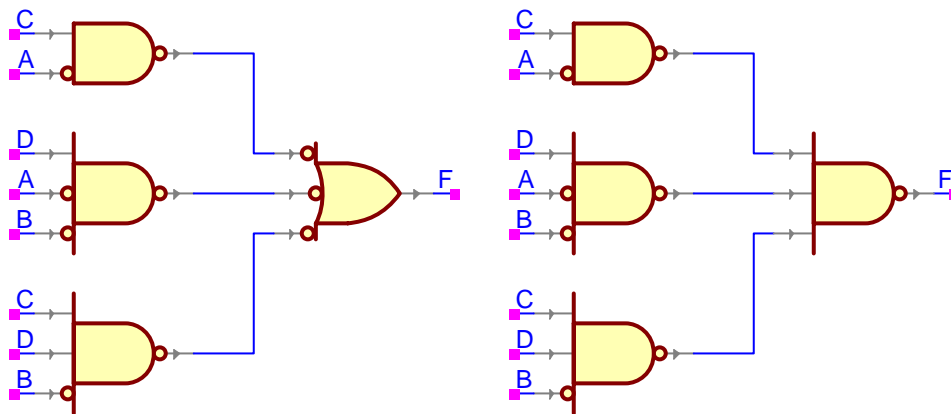


NAND Gate Implementation

 



NOR Gate Implementation

### Exercise 3.12

(a)  $Z = (AB + CD)E + F$

 


Initial Circuit

  


NAND/NOR Gate Implementation

(b)  $Z = (AB + C)E + DG$

 


Initial Circuit

 


NAND/NOR Gate Implementation

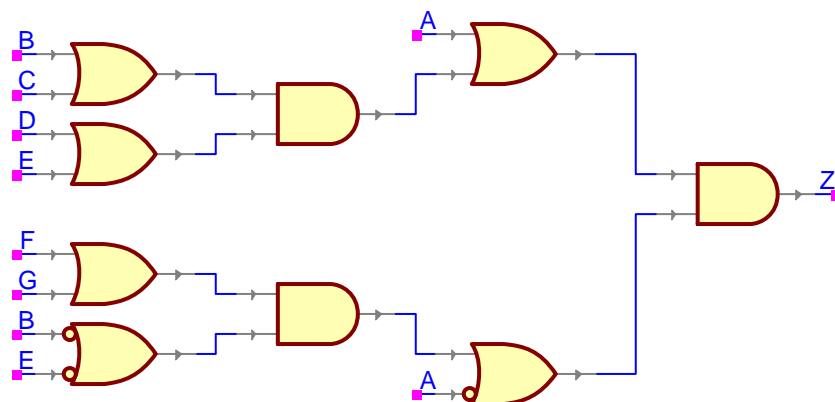
(c)  $Z = \{A + [(B + C)(D + E)]\} \{[(F + G)(B' + E')] + A'\}$



Initial Circuit

 




 


NAND/NOR Gate Implementation

(d)  $Z = (A + B)(C + D) + EF$

 


Initial Circuit


 


NAND/NOR Gate Implementation

(e)  $Z = (AB)'(B' + C)D' + A'$

 

NAND/NOR Gate Implementation

  

NAND/NOR Gate Implementation

### **Exercise 3.13**

We will show the multi-level forms for the full adder are equivalent to the two-level forms using Boolean algebra.

Recall from Section 2.2 that the two-level functions for Sum and Cout are:

$$\text{Sum} = AB'Cin' + A'BCin' + A'B'Cin + ABCin$$

$$\text{Cout} = ABCin + ABCin' + AB'Cin + A'BCin$$

The multi-level functions for Sum and Cout are:

$$\text{Sum} = Cin'X' + CinX$$

$$\text{Cout} = AB + CinY$$

$$X = A'B' + AB$$

$$Y = A + B$$

We'll start by negating X to get X' and then substitute these into the function for Sum:

$$X' = (A'B' + AB)' = (A'B')'(AB)' = (A + B)(A' + B') = AB' + A'B$$

$$\begin{aligned}\text{Sum} &= Cin(AB' + A'B) + Cin(A'B' + AB) \Rightarrow \\ &AB'Cin' + A'BCin' + A'B'Cin + ABCin\end{aligned}$$

Next, we'll manipulate Y to get it into the correct form. We will do this by multiplying Y by  $(A + A')$  and  $(B + B')$ . Recall that this is equivalent to multiplying by one in Boolean algebra.

$$\begin{aligned}Y &= (A + B)(A + A')(B + B') \Rightarrow \\ &AAB + AAB' + AA'B + AA'B' + ABB + ABB' + A'BB + A'BB'\end{aligned}$$

Also recall that multiplying a term by its complement yields 0 and  $AA$  is equivalent to  $A$ . So, after removing terms that evaluate to zero and combining terms, we are left with:

$$Y = AB + AB' + A'B$$

Before we substitute Y into Cout, we have to multiply Cout by  $(Cin + Cin')$ .

$$\text{Cout} = (AB + CinY)(Cin + Cin') = ABCin + ABCin' + CinCinY + CinCin'Y$$

Or simply:

$$\text{Cout} = ABCin + ABCin' + CinY$$

Now we can substitute Y into Cout.

$$\begin{aligned}\text{Cout} &= ABCin + ABCin' + Cin(AB + AB' + A'B) \Rightarrow \\ &ABCin + ABCin' + AB'Cin + A'BCin\end{aligned}$$

**Exercise 3.14**

We will use a truth table to show that the multi-level form of the 2-bit adder is equivalent to the multi-level form. The multi-level functions for the 2-bit adder are:

$$Z = B'D + BD'$$

$$Y = W'A'C + W'AC' + WAC + WA'C'$$

$$X = AC + W(A + C)$$

$$W = BD$$

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	1
0	1	0	0	0	0	0	1
0	1	0	1	1	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0
1	0	0	1	0	0	1	1
1	0	1	0	0	1	0	0
1	0	1	1	0	1	0	1
1	1	0	0	0	0	1	1
1	1	0	1	1	1	0	0
1	1	1	0	0	1	0	1
1	1	1	1	1	1	1	0

### Exercise 3.15

(a) Boolean representation of the circuit:

$$Z = (B \text{ xor } C)(A \text{ xor } C)' + (A \text{ xor } B)(B \text{ xor } C)'$$

(b) Truth table:

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

(c) Sum-of-products function:

$$Z = \sum m(1,3,4,6)$$


(d) K-map:

		AB			
		00	01	11	10
C	00			1	1
	01	1	1		
 
### Exercise 3.16


$$F(A,B,C,D) = (A + (BC))(C' + D)$$

$$G(A,B,C,D) = ((A + B')D) + (A + (BC))$$




Initial Circuits

(a) NAND-only implementations:

 

(b) NOR-only implementations:

 

(c) Truth tables for F and G:

A	B	C	D	F	G
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	0	0
0	0	1	1	0	1
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	0	1
1	0	1	1	1	1
1	1	0	0	1	1

1	1	0	1	1	1
1	1	1	0	0	1
1	1	1	1	1	1

K-Maps for F and G:

AB \ CD	00	01	11	10
00			1	1
01			1	1
11		1	1	1
10				

K-Map for F

$$F = AC' + AD + BCD$$

AB \ CD	00	01	11	10
00			1	1
01	1		1	1
11	1	1	1	1
10		1	1	1

K-Map for G

$$G = A + BC + B'D$$

(d) To find the simplified product-of-sums form, we get the sum-of-products for the 0's in the k-maps and then negate them.

AB \ CD	00	01	11	10
00			1	1
01			1	1
11		1	1	1
10				

K-Map for

$$F' = A'C' + A'B' + CD'$$

AB \ CD	00	01	11	10
00			1	1
01	1		1	1
11	1	1	1	1
10		1	1	1

K-Map for

$$G' = ABC' + A'B'D'$$

$$F'' = (A'C' + A'B' + CD')' = (A'C')'(A'B')'(CD')' \Rightarrow$$

$$F = (A + C)(A + B)(C' + D)$$

$$G'' = (ABC' + A'B'D')' = (ABC')'(A'B'D')' \Rightarrow$$

$$G = (A' + B' + C)(A + B + D)$$

(e) The implementation complexities for the sum-of products implementations are:

F has 7 literals with two 2-input AND, one 3-input AND, and one 3-input OR gates.

G has 5 literals with two 2-input AND, and one 3-input OR gates.

The complexities for the product-of-sums implementations are:

F has 6 literals with three 2-input AND and one 3-input OR gates.

G also has 6 literals with two 3-input AND and one 2-input OR gates.

So in both cases the product-of-sums implementation was less complex.




### Exercise 3.17

$$F(A,B,C,D,E) = (((AB) + C)(D + E)) + (A'D')$$


$$G(A,B,C) = (ABC')$$

$$H(A,B,C,D) = (D + G)G'$$

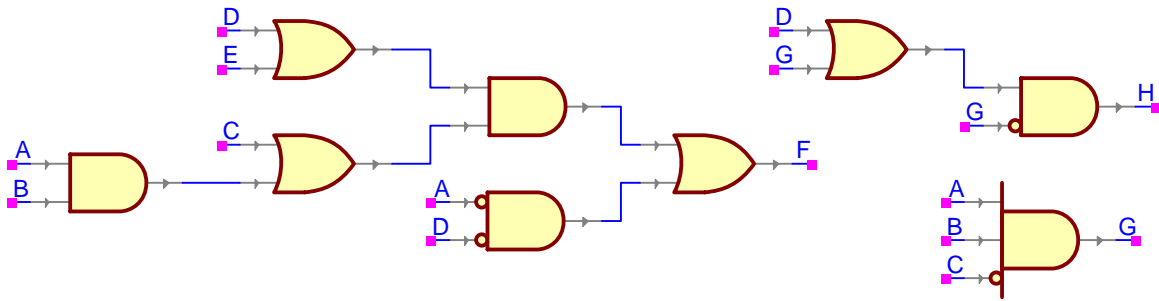


Initial Circuits

(a) NAND-only implementations:

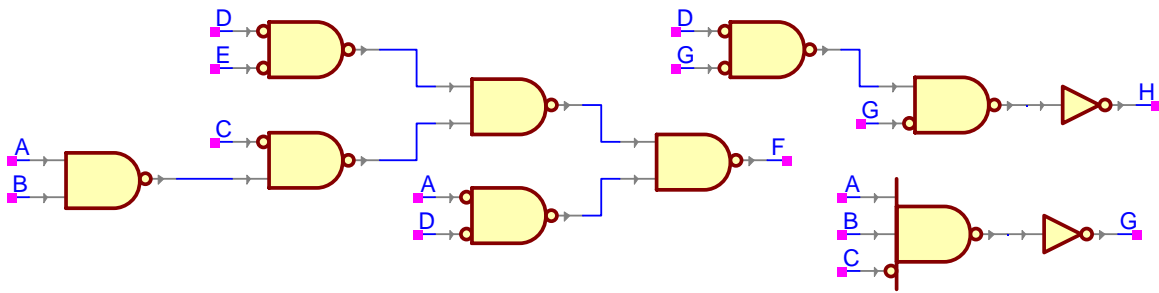

(b) NOR-only implementations:

 

(c) Minimized Sum-of-Products:

Truth tables for F, G, and H:



A	B	C	D	E	F	G	H
0	0	0	0	0	1	0	0
0	0	0	0	1	1	0	0
0	0	0	1	0	0	0	1
0	0	0	1	1	0	0	1
0	0	1	0	0	1	0	0
0	0	1	0	1	1	0	0
0	0	1	1	0	1	0	1
0	0	1	1	1	1	0	1
0	1	0	0	0	1	0	0
0	1	0	0	1	1	0	0
0	1	0	1	0	0	0	1
0	1	0	1	1	0	0	1
0	1	1	0	0	1	0	0
0	1	1	0	1	1	0	0
0	1	1	1	0	1	0	1
0	1	1	1	1	1	0	1
1	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0
1	0	0	1	0	0	0	1
1	0	0	1	1	0	0	1
1	0	1	0	0	0	0	0
1	0	1	0	1	1	0	0
1	0	1	1	0	1	0	1
1	0	1	1	1	1	0	1
1	1	0	0	0	0	1	0
1	1	0	0	1	1	1	0
1	1	0	1	0	1	1	0
1	1	0	1	1	1	1	0
1	1	1	0	0	0	0	0
1	1	1	0	1	1	0	0
1	1	1	1	0	1	0	1
1	1	1	1	1	1	0	1

$$F(A,B,C,D,E) = \Sigma m(0,1,4,5,6,7,8,9,12,13,14,15,21,22,23,25,26,27,29,30,31)$$

$$G(A,B,C) = \Sigma m(6)$$

$$H(A,B,C,D) = \Sigma m(1,3,5,7,9,11,15)$$

K-Maps:

  

$$F(A,B,C,D,E) = A'D' + CE + CD + ABD + ABE$$

$$G(A,B,C) = ABC'$$

$$H(A,B,C,D) = A'D + B'D + CD$$

(d) Minimized Product-of-Sums:

$$F' = A'C'D + B'C'DE' + AB'C' + AD'E'$$

$$F'' = (A'C'D)'(B'C'DE')'(AB'C')'(AD'E')'$$

$$F(A,B,C,D,E) = (A + C + D')(B + C + D' + E)(A' + B + C)(A' + D + E)$$

$$G' = A' + B' + C$$

$$G'' = (A' + B' + C)'$$

$$G(A,B,C) = ABC'$$

$$H' = D' + ABC'$$

$$H'' = (D')'(ABC')'$$

$$H(A,B,C,D) = D(A' + B' + C)$$

### Exercise 3.18

(a) The K-map for this function shows that there are adjacent groups of 1's without a circle:

		AB			
		00	01	11	10
C	00		1	1	
	01	1	1		

Hazard

		AB			
		00	01	11	10
C	00		1	1	
	01	1	1		

Hazard free

$$F(A,B,C) = A'B + A'C + BC'$$

(b) The K-map for F:

		AB			
		00	01	11	10
CD	00	1	1		
	01		1	1	1
	11		1		1
	10		1	1	

$$F(A,B,C,D) = A'C'D' + AC'D + AB'D + BC'D + BCD' + A'B$$

(c) The K-map for F:

		AB			
		00	01	11	10
C	00				1
	01		1	1	1

$$F(A,B,C) = AB' + AC + BC$$

(d) The K-map for F:

AB \ CD	00	01	11	10
00	0			0
01	0	0	0	0
11	0	0	0	
10				

$$F(A,B,C,D) = BD' + CD' + AB'C$$

(e) The K-map for F:

		BC			
		00	01	11	10
A=0	DE 00	1	1	1	
	01	1			
	11	1	1	1	1
	10				
A=1	DE 00	1	1	1	
	01	1			
	11				
	10				

$$F(A,B,C,D,E) = A'DE + B'D'E' + B'C'D' + B'C'E + CD'E'$$


### **Exercise 3.19**

In this output response waveform,  $T_1$  represents the output of the first XOR gate and  $T_2$  represents the output of the first NAND gate. The propagation delay for the XOR gate is 10 time units and the delay for the NAND gate is 10 time units. We are assuming that  $T_{PHL}$  is equal to  $T_{PLH}$ .

Here is the truth table for F and G:

A	B	F	G
0	0	1	0
0	1	1	1
1	0	1	1
1	1	0	1

Output response waveform:

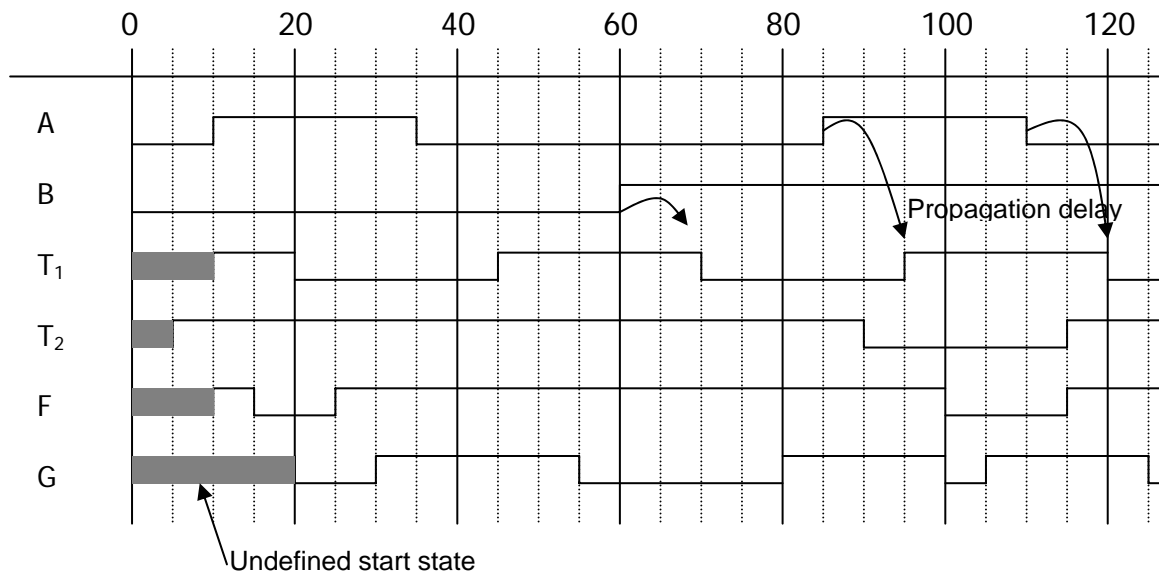

### Exercise 3.20

(a) The steady-state starting condition for the circuit is as follows:


$$A = 1$$

$$B = 1$$

$$C = 0$$

$$D = 0$$

 (b) Output response wave form after time T:







### **Exercise 3.21**

In each of the output waveforms, the oscillating signal from the switch is A, and the output from the NOR gate is F.

 - (a) This circuit oscillates when the switch is open and is steady when the switch is closed.



- (b) This circuit does not oscillate when the switch is open or closed. The initial output of the NOR gate could either be high or low when the switch is open.

 



**Exercise 3.22**

(a) Here is the truth table for  $R_0$  and  $R_1$ :

Note that since division by zero will never be requested, there are eight don't-cares for both  $R_1$  and  $R_0$ .

$D_2$	$D_1$	$D_0$	$C_1$	$C_0$	$R_1$	$R_0$
0	0	0	0	0	X	X
0	0	0	0	1	0	1
0	0	0	1	0	1	0
0	0	0	1	1	1	1
0	0	1	0	0	X	X
0	0	1	0	1	0	0
0	0	1	1	0	1	0
0	0	1	1	1	1	1
0	1	0	0	0	X	X
0	1	0	0	1	0	0
0	1	0	1	0	0	0
0	1	0	1	1	1	1
0	1	1	0	0	X	X
0	1	1	0	1	0	0
0	1	1	1	0	0	1
0	1	1	1	1	0	0
1	0	0	0	0	X	X
1	0	0	0	1	0	0
1	0	0	1	0	0	0
1	0	0	1	1	0	1
1	0	1	0	0	X	X
1	0	1	0	1	0	0
1	0	1	1	0	0	1
1	0	1	1	1	1	0
1	1	0	0	0	X	X
1	1	0	0	1	0	0
1	1	0	1	0	0	0
1	1	0	1	1	0	0
1	1	1	0	0	X	X
1	1	1	0	1	0	0
1	1	1	1	0	0	1
1	1	1	1	1	0	1


(b) K-Maps for  $R_1$  and  $R_0$ :

  


$$R_1 = D_2'D_1'C_1 + D_2'D_0'C_1C_0 + D_1'D_0C_1C_0$$

$$R_0 = D_2'D_1'D_0'C_0 + D_2'D_1'C_1C_0 + D_2'D_0'C_1C_0 + D_1'D_0'C_1C_0 + D_1D_0C_1C_0' + D_2D_1D_0C_1 + D_2D_0C_0'$$

(c) Circuit Schematics:

 

Initial Circuits

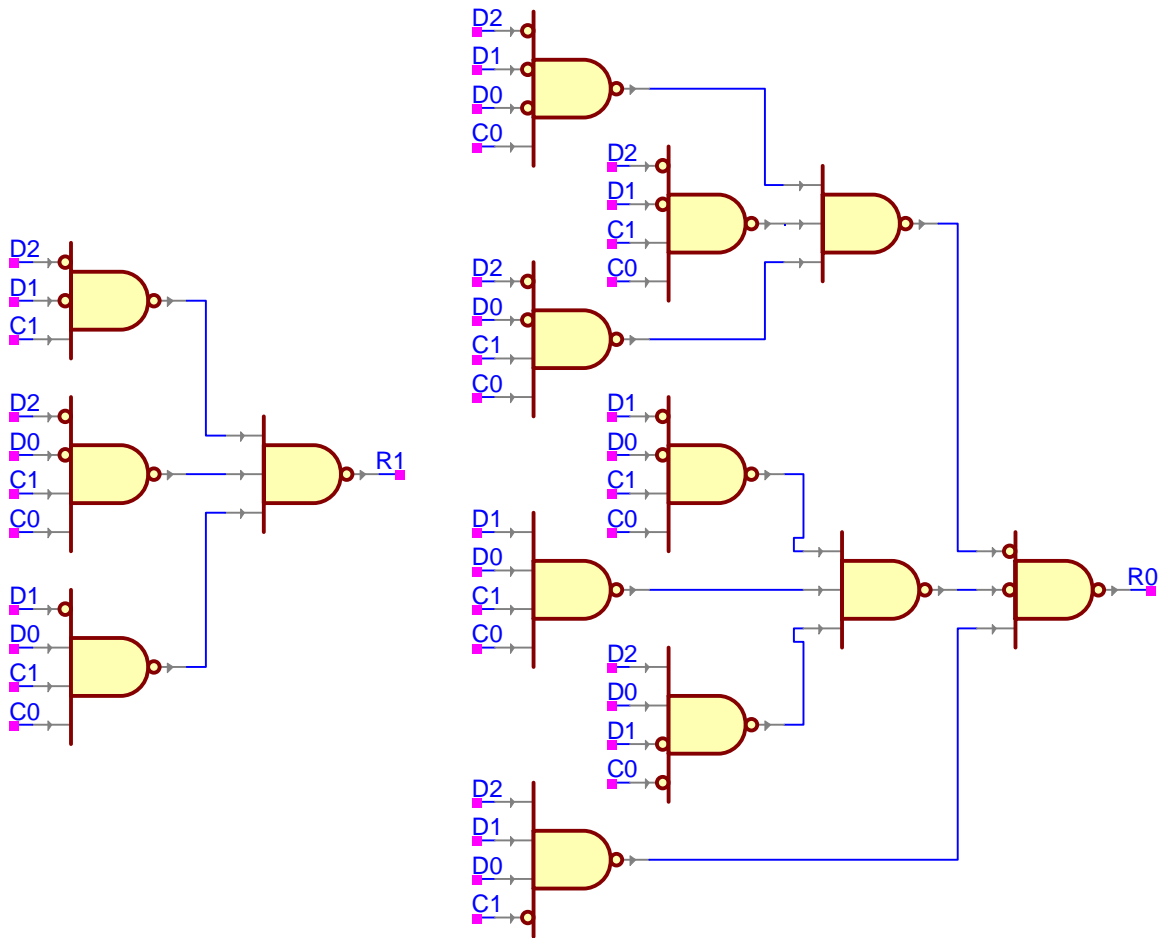

NAND-gate implementation

- (d) There is a definite advantage when sharing expressions with this design. A lot of the expressions share subexpressions, which makes the overall design less expensive as well as reducing the fan-in to some of the logic gates.

$$R_1 = C_1(D_2'D_1' + C_0(D_2'D_0' + D_1'D_0))$$

$$R_0 = C_1C_0(D_2'D_1' + D_2'D_0' + D_1'D_0') + D_1D_0(C_1C_0' + D_2C_1) + D_1'(D_2'D_0'C_0 + D_2D_0C_0')$$

### Exercise 3.23

- (a) Since division by zero is illegal, we will assume that this will not happen. If it does, we don't care what happens. Here is the truth table for WX and YZ:

A	B	C	D	W	X	Y	Z
0	0	0	0	X	X	X	X
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	1
0	1	0	0	X	X	X	X
0	1	0	1	0	1	0	0
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	X	X	X	X
1	0	0	1	1	0	0	0
1	0	1	0	0	1	0	0
1	0	1	1	0	0	1	1
1	1	0	0	X	X	X	X
1	1	0	1	1	1	0	0
1	1	1	0	0	1	0	1
1	1	1	1	0	1	0	0

- (b) Minimized sum-of-products:

$$W(A,B,C,D) = \Sigma m(9,13) + \Sigma d(0,4,8,12)$$

$$X(A,B,C,D) = \Sigma m(5,10,13,14,15) + \Sigma d(0,4,8,12)$$

$$Y(A,B,C,D) = \Sigma m(2,3,6,7,11) + \Sigma d(0,4,8,12)$$

$$Z(A,B,C,D) = \Sigma m(1,3,7,11,14) + \Sigma d(0,4,8,12)$$

AB \ CD	00	01	11	10
00	X	X	X	X
01			1	1
11				
10				

K-Map for

AB \ CD	00	01	11	10
00	X	X	X	X
01		1	1	
11			1	
10			1	1

K-Map for

AB \ CD		00	01	11	10
CD	00	X	X	X	X
	01				
	11	1	1		1
	10	1	1		

K-Map for Y

AB \ CD		00	01	11	10
CD	00	X	X	X	X
	01	1			
	11	1	1		1
	10			1	

K-Map for Z

$$W(A,B,C,D) = AC'$$

$$X(A,B,C,D) = AB + BC' + AD'$$

$$Y(A,B,C,D) = A'C + B'CD$$

$$Z(A,B,C,D) = ABC' + A'CD + A'B'D + B'CD$$

(c) Minimized product-of-sums:

$$W' = A' + C$$

$$W'' = (A' + C)'$$

$$W = AC'$$

$$X' = B'D + A'C$$

$$X'' = (B'D + A'C)' = (B'D)'(A'C)'$$

$$X = (B + D')(A + C')$$

$$Y' = C' + AB + AD'$$

$$Y'' = (C' + AB + AD')' = (C')'(AB)'(AD')'$$

$$Y = C(A' + B')(A' + D)$$

$$Z' = A'D' + BC' + AC' + B'D' + ABD$$

$$Z'' = (A'D' + BC' + AC' + B'D' + ABD)' = (A'D')'(BC')'(AC')'(B'D')'(ABD)'$$

$$Z = (A + D)(B' + C)(A' + C)(B + D)(A' + B' + D')$$

### Exercise 3.24

(a) Truth tables for By2, By3, and By6:

A	B	C	D	By2	By3	By6
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	0
0	1	1	0	1	1	1
0	1	1	1	0	0	0
1	0	0	0	1	0	0
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	0	1	1	0	0	0
1	1	0	0	X	X	X
1	1	0	1	X	X	X
1	1	1	0	X	X	X
1	1	1	1	X	X	X

(b) Minimized sum-of-products:

$$\text{By2} = \Sigma m(2,4,6,8,10) + \Sigma d(12,13,14,15)$$

$$\text{By3} = \Sigma m(3,6,9) + \Sigma d(12,13,14,15)$$

$$\text{By6} = \Sigma m(6) + \Sigma d(12,13,14,15)$$

AB \ CD	00	01	11	10
00		1	X	1
01			X	
11			X	
10	1	1	X	1

K-Map for By2

AB \ CD	00	01	11	10
00			X	
01			X	1
11	1		X	
10		1	X	

K-Map for By3



		AB			
		00	01	11	10
CD	00			X	
	01			X	
	11			X	
	10		1	X	

K-Map for By6

$$\text{By2}(A,B,C,D) = AD' + BD' + C D'$$

$$\text{By3}(A,B,C,D) = AC'D + BCD' + A'B'CD$$

$$\text{By6}(A,B,C,D) = BCD'$$

- (c) Yes, By2 could be simplified by factoring out the  $D'$ . Also, By3 could be simplified by using the result from By6 for its second expression.

### Exercise 3.25

(a) Truth table for X, Y, and Z:

A	B	C	D	X	Y	Z
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	0
0	1	1	1	0	1	1
1	0	0	0	0	0	1
1	0	0	1	0	1	0
1	0	1	0	0	1	0
1	0	1	1	0	1	1
1	1	0	0	0	1	0
1	1	0	1	0	1	1
1	1	1	0	0	1	1
1	1	1	1	1	0	0

(b) Minimized sum-of-products:

$$X(A,B,C) = \Sigma m(15)$$

$$Y(A,B,C) = \Sigma m(3,5,6,7,9,10,11,12,13,14)$$

$$Z(A,B,C) = \Sigma m(1,2,4,7,8,11,13,14)$$

AB \ CD		AB			
		00	01	11	10
00	CD			1	
01	CD		1	1	1
11	CD	1	1		1
10	CD		1	1	1

K-Map for Y

AB \ CD		AB			
		00	01	11	10
00	CD		1		1
01	CD	1		1	
11	CD		1		1
10	CD	1		1	

K-Map for Z

Since X only has one minterm, there is no need to construct a K-map for it.

$$X(A,B,C) = ABCD$$

$$Y(A,B,C) = ABC' + AC'D + BC'D + B'CD + A'BC + ACD'$$

$$Z(A,B,C) = A'B'C'D + A'B'CD' + A'BC'D' + A'BCD + AB'C'D' + AB'CD + ABC'D + ABCD'$$

(c) Minimized product-of-sums:

$$X' = A' + B' + C' + D'$$

$$X'' = (A' + B' + C' + D')'$$

$$X = ABCD$$

$$Y' = A'C'D' + A'B'C' + A'B'D' + B'C'D' + ABCD$$

$$Y'' = (A'C'D' + A'B'C' + A'B'D' + B'C'D' + ABCD)'$$

$$Y = (A + C + D)(A + B + C)(A + B + D)(B + C + D)(A' + B' + C' + D')$$

$$Z' = A'B'C'D' + A'B'CD + A'BC'D + ABC'D' + A'BCD' + ABCD + AB'C'D + AB'CD'$$

$$Z'' = (A'B'C'D' + A'B'CD + A'BC'D + ABC'D' + A'BCD' + ABCD + AB'C'D + AB'CD')'$$

$$Z = (A + B + C + D)(A + B + C' + D')(A + B' + C + D')(A' + B' + C + D)(A + B' + C' + D)(A' + B' + C' + D')(A' + B + C + D')(A' + B + C' + D)$$

### Exercise 3.26

(a) Truth table for the 3-bit sum XYZ:

A	B	C	D	X	Y	Z
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

(b) Minimized sum-of-products:

$$X(A,B,C,D) = \Sigma m(7,10,11,13,14,15)$$

$$Y(A,B,C,D) = \Sigma m(2,3,5,6,8,9,12,15)$$


$$Z(A,B,C,D) = \Sigma m(1,3,4,6,9,11,12,14)$$

AB \ CD		AB			
		00	01	11	10
00	CD				
01	CD			1	
11	CD		1	1	1
10	CD			1	1

K-Map for X

AB \ CD		AB			
		00	01	11	10
00	CD			1	1
01	CD		1		1
11	CD	1		1	
10	CD	1	1		

K-Map for Y

 

$$X(A,B,C,D) = AC + BCD + ABD$$

$$Y(A,B,C,D) = AC'D' + AB'C' + A'B'C + A'CD' + A'BC'D + ABCD$$


$$Z(A,B,C,D) = BD' + B'D$$

- (c) The full adder has a worse delay than the 2-bit adder that was designed in this problem. The critical path for the 2-bit adder in this exercise is 2 gate delays because it was implemented with two-level logic. The critical path for the full adder is the carry out, which is  $n + 2$ , where  $n$  is the number of bits being summed. So a 2-bit full adder would have a delay of 4 gates.


**Exercise 3.27**

Truth table for the generalized 2-bit adder:


Cin	A	B	C	D	Cout	Y	Z
0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	1
0	0	0	1	0	0	1	0
0	0	0	1	1	0	1	1
0	0	1	0	0	0	0	1
0	0	1	0	1	0	1	0
0	0	1	1	0	0	1	1
0	0	1	1	1	1	0	0
0	1	0	0	0	0	1	0
0	1	0	0	1	0	1	1
0	1	0	1	0	1	0	0
0	1	0	1	1	1	0	1
0	1	1	0	0	0	1	1
0	1	1	0	1	1	0	0
0	1	1	1	0	1	0	1
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	1
1	0	0	0	1	0	1	0
1	0	0	1	0	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	0	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	0	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	0	0	1	1
1	1	0	0	1	1	0	0
1	1	0	1	0	1	0	1
1	1	0	1	1	1	1	0
1	1	1	0	0	1	0	0
1	1	1	0	1	1	0	1
1	1	1	1	0	1	1	0
1	1	1	1	1	1	1	1

 

K-Map for Y

 

K-Map for Z

 

K-Map for  $C_{out}$

$$C_{out}(A,B,C,D,C_{in}) = AC + ABD + BCD + ADC_{in} + BCC_{in} + ABC_{in} + CDC_{in}$$

$$Y(A,B,C,D,C_{in}) = A'B'CC_{in}' + A'CD'C_{in}' + AC'D'C_{in}' + AB'C'C_{in}' + AB'C'D' + A'B'CD' + A'BC'D + ABCD + A'BC'C_{in} + A'C'DC_{in} + ACDC_{in} + ABCC_{in}$$

$$Z(A,B,C,D,C_{in}) = BD'C_{in}' + B'DC_{in} + BDC_{in} + B'D'C_{in}$$



### **Exercise 3.28**

Verilog has the modulo operator, %, that provides the functionality that we are trying to achieve in Exercise 3.22. The verilog module looks as follows:

```
module remainder(input wire [2:0] D, input wire [1:0] C, output wire [1:0] R);  
    //Taking the mod of D with C will give us the remainder of dividing D by C  
    assign R = D % C;  
endmodule
```

### **Exercise 3.29**

The 2-bit combinational divider from Exercise 3.23 can be implemented in verilog as follows:

```
module divider(input wire A, input wire B, input wire C, input wire D,
               output wire W, output wire X, output wire Y, output wire Z);

    //Registers to store the 2-bit input and outputs
    wire [1:0] in_1, in_2;
    reg [1:0] quotient, remainder;

    //Assign the appropriate bits to the operands
    assign in_1[1] = A;
    assign in_1[0] = B;
    assign in_2[1] = C;
    assign in_2[0] = D;

    //Combinational block
    always@(*)
        begin
            quotient = in_1 / in_2;
            remainder = in_1 % in_2;
        end

    //Assign the output bits the appropriate values
    assign W = quotient[1];
    assign X = quotient[0];
    assign Y = remainder[1];
    assign Z = remainder[0];

endmodule
```

### **Exercise 3.30**

This module determines if the input value is divisible by 2, 3, and 6 by taking the modulo of the input with 2, 3, and 6 and sets the outputs to the appropriate value. Note that this works with any input value from  $0000_2$  to  $1111_2$ .

```
module div_by_2_3_6(input wire A, input wire B, input wire C, input wire D,
    output reg By2, output reg By3, output reg By6);

    //A place to store the input
    wire [3:0] value;

    //Assign value with the input by taking each bit, shifting it left by
    //the appropriate amount and ORing them together.
    assign value = (A << 3) | (B << 2) | (C << 1) | D;

    //Combinational block
    always@(*)
        begin
            //Check if divisible by 2
            if((value % 2) == 0)
                By2 = 1;
            else
                By2 = 0;

            //Check if divisible by 3
            if((value % 3) == 0)
                By3 = 1;
            else
                By3 = 0;

            //Check if divisible by 6
            if((value % 6) == 0)
                By6 = 1;
            else
                By6 = 0;
        end
endmodule
```

### **Exercise 3.31**

This module works by adding each of the bits, A, B, C, and D together and storing the result into a 3-bit register, which is parsed into separate bits for the output.

```
module ones_count(input wire A, input wire B, input wire C, input wire D,
    output wire X, output wire Y, output wire Z);

    //A place to store the 3-bit output
    wire [2:0] out;

    //Add each bit together
    assign out = A + B + C + D;

    //Parse the output into seperate bits
    assign X = out[2];
    assign Y = out[1];
    assign Z = out[0];

endmodule
```

### **Exercise 3.32**

This module adds the two 2-bit inputs together by shifting the high-order bit of the inputs to the left once and OR's it with the low-order bit then adds the result to the other input.

```
module adder(input wire A, input wire B, input wire C, input wire D,
             output wire X, output wire Y, output wire Z);

    //A place to store the 3-bit output
    wire [2:0] sum;

    //Shift the high-order bit left once, OR it with the low-order
    //bit for each input, and sum the results
    assign sum = ((A << 1) | B) + ((C << 1) | D);

    //Parse the output into seperate bits
    assign X = sum[2];
    assign Y = sum[1];
    assign Z = sum[0];

endmodule
```