

# **CH-8: Finite State Machine** **Optimization**

*Contemporary Logic Design*

YONSEI UNIVERSITY

Fall 2016



# Finite State Machine Optimization

---

- State minimization
  - ◆ *fewer states* require fewer state bits
  - ◆ *fewer bits* require fewer logic equations
- Encodings: state, inputs, outputs
  - ◆ state encoding with *fewer bits* has fewer equations to implement
    - however, each may be more complex
  - ◆ state encoding with *more bits* (e.g., one-hot) has *simpler equations*
    - complexity directly related to complexity of state diagram
  - ◆ input/output encoding may or may not be under designer control

# Finite State Machine Optimization

- State minimization

  

- **Odd Parity Checker:** two alternative state diagrams
  - Identical output behavior on all input strings
  - FSMs are *equivalent*, but require different implementations
  - Design state diagram without any concern for # of states, Reduce later

# Algorithmic Approach to State Minimization

---

- **Goal** – *identify and combine states that have equivalent behavior*
- *Equivalent states:*
  - ◆ same output
  - ◆ for all input combinations, states transition to same or equivalent states
- Algorithm sketch to find equivalent states
  - ◆ 1. place all states in one set
  - ◆ 2. initially partition set based on output behavior
  - ◆ 3. successively partition resulting subsets based on next state transitions
  - ◆ 4. repeat (3) until no further partitioning is required
    - states left in the same set are equivalent
  - ◆ polynomial time procedure

# State Minimization: Row Matching Method

## ■ Sequence detector EX for 1010 or 0110

- ◆ single input X, output Z
- ◆ taking inputs grouped four at a time, output 1 if last four inputs were the string 1010 or 0110

1<sup>st</sup> bit → Example I/O Behavior:

X = 0010 0110 1100 1010 0011 ...  
Z = 0000 0001 0000 0001 0000 ...

**Upper bound on FSM complexity:**


Fifteen states (1 + 2 + 4 + 8)

Thirty transitions (2 + 4 + 8 + 16)

sufficient to recognize any binary string of length four!

# State Minimization: Row Matching Method

- State diagram for example FSM

 

# State Minimization: Row Matching Method

## ■ Initial State Transition Table:

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	0	0
0	S <sub>1</sub>	S <sub>3</sub>	S <sub>4</sub>	0	0
1	S <sub>2</sub>	S <sub>5</sub>	S <sub>6</sub>	0	0
00	S <sub>3</sub>	S <sub>7</sub>	S <sub>8</sub>	0	0
01	S <sub>4</sub>	S <sub>9</sub>	S <sub>10</sub>	0	0
10	S <sub>5</sub>	S <sub>11</sub>	S <sub>12</sub>	0	0
11	S <sub>6</sub>	S <sub>13</sub>	S <sub>14</sub>	0	0
000	S <sub>7</sub>	S <sub>0</sub>	S <sub>0</sub>	0	0
001	S <sub>8</sub>	S <sub>0</sub>	S <sub>0</sub>	0	0
010	S <sub>9</sub>	S <sub>0</sub>	S <sub>0</sub>	0	0
011	S <sub>10</sub>	S <sub>0</sub>	S <sub>0</sub>	1	0
100	S <sub>11</sub>	S <sub>0</sub>	S <sub>0</sub>	0	0
101	S <sub>12</sub>	S <sub>0</sub>	S <sub>0</sub>	1	0
110	S <sub>13</sub>	S <sub>0</sub>	S <sub>0</sub>	0	0
111	S <sub>14</sub>	S <sub>0</sub>	S <sub>0</sub>	0	0

# State Minimization: Row Matching Method

## ■ Initial State Transition Table:

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_7$	$S_8$	0	0
01	$S_4$	$S_9$	$S_{10}$	0	0
10	$S_5$	$S_{11}$	$S_{12}$	0	0
11	$S_6$	$S_{13}$	$S_{14}$	0	0
000	$S_7$	$S_0$	$S_0$	0	0
001	$S_8$	$S_0$	$S_0$	0	0
010	$S_9$	$S_0$	$S_0$	0	0
011	$S_{10}$	$S_0$	$S_0$	1	0
100	$S_{11}$	$S_0$	$S_0$	0	0
101	$S_{12}$	$S_0$	$S_0$	1	0
110	$S_{13}$	$S_0$	$S_0$	0	0
111	$S_{14}$	$S_0$	$S_0$	0	0



# State Minimization: Row Matching Method

## ■ Initial State Transition Table:

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_7$	$S_8$	0	0
01	$S_4$	$S_9$	$S'_{10}$	0	0
10	$S_5$	$S_{11}$	$S'_{10}$	0	0
11	$S_6$	$S_{13}$	$S_{14}$	0	0
000	$S_7$	$S_0$	$S_0$	0	0
001	$S_8$	$S_0$	$S_0$	0	0
010	$S_9$	$S_0$	$S_0$	0	0
011 or 101	$S'_{10}$	$S_0$	$S_0$	1	0
100	$S_{11}$	$S_0$	$S_0$	0	0
110	$S_{13}$	$S_0$	$S_0$	0	0
111	$S_{14}$	$S_0$	$S_0$	0	0

# State Minimization: Row Matching Method

## ■ Initial State Transition Table:

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S_7$	$S_8$	0	0
01	$S_4$	$S_9$	$S'_{10}$	0	0
10	$S_5$	$S_{11}$	$S'_{10}$	0	0
11	$S_6$	$S_{13}$	$S_{14}$	0	0
011 or	000	$S_0$	$S_0$	0	0
	001	$S_0$	$S_0$	0	0
	010	$S_0$	$S_0$	0	0
	101	$S_0$	$S_0$	1	0
	100	$S_0$	$S_0$	0	0
	110	$S_0$	$S_0$	0	0
	111	$S_0$	$S_0$	0	0

# State Minimization: Row Matching Method

## ■ Initial State Transition Table:

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S'_7$	$S'_7$	0	0
01	$S_4$	$S'_7$	$S'_{10}$	0	0
10	$S_5$	$S'_7$	$S'_{10}$	0	0
11	$S_6$	$S'_7$	$S'_7$	0	0
not (011 or 101)	$S'_7$	$S_0$	$S_0$	0	0
011 or 101	$S'_{10}$	$S_0$	$S_0$	1	0

# State Minimization: Row Matching Method

## ■ Initial State Transition Table:


Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S_1$	$S_2$	0	0
0	$S_1$	$S_3$	$S_4$	0	0
1	$S_2$	$S_5$	$S_6$	0	0
00	$S_3$	$S'_7$	$S'_7$	0	0
01	$S_4$	$S'_7$	$S'_{10}$	0	0
10	$S_5$	$S'_7$	$S'_{10}$	0	0
11	$S_6$	$S'_7$	$S'_7$	0	0
not (011 or 101)	$S'_7$	$S_0$	$S_0$	0	0
011 or 101	$S'_{10}$	$S_0$	$S_0$	1	0

# State Minimization: Row Matching Method

**Final Reduced  
State Transition Table**

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3'	S4'	0	0
1	S2	S4'	S3'	0	0
00 or 11	S3'	S7'	S7'	0	0
01 or 10	S4'	S7'	S10'	0	0
not (011 or 101)	S7'	S0	S0	0	0
011 or 101	S10'	S0	S0	1	0


**Corresponding State  
Diagram**

 

# State Minimization Example

- Sequence detector for 010 or 110

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

 

# Method of Successive Partitions

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

( S0 S1 S2 S3 S4 S5 S6 )

S1 is equivalent to S2

( S0 S1 S2 S3 S5 ) ( S4 S6 )

S3 is equivalent to S5

( S0 S3 S5 ) ( S1 S2 ) ( S4 S6 )

S4 is equivalent to S6

( S0 ) ( S3 S5 ) ( S1 S2 ) ( S4 S6 )

# Method of Successive Partitions

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4'	0	0
1	S2	S5	S4'	0	0
00	S3	S0	S0	0	0
01	S4'	S0	S0	1	0
10	S5	S0	S0	0	0

( S0 S1 S2 S3 S4 S5 S6 )

S1 is equivalent to S2

( S0 S1 S2 S3 S5 ) ( S4 S6 )

S3 is equivalent to S5

( S0 S3 S5 ) ( S1 S2 ) ( S4 S6 )

S4 is equivalent to S6

( S0 ) ( S3 S5 ) ( S1 S2 ) ( S4 S6 )



# Method of Successive Partitions

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3'	S4'	0	0
1	S2	S3'	S4'	0	0
00	S3'	S0	S0	0	0
01	S4'	S0	S0	1	0

( S0 S1 S2 S3 S4 S5 S6 )

S1 is equivalent to S2

( S0 S1 S2 S3 S5 ) ( S4 S6 )

S3 is equivalent to S5

( S0 S3 S5 ) ( S1 S2 ) ( S4 S6 )

S4 is equivalent to S6

( S0 ) ( S3 S5 ) ( S1 S2 ) ( S4 S6 )

# Method of Successive Partitions

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1'	S3'	S4'	0	0
00	S3'	S0	S0	0	0
01	S4'	S0	S0	1	0

( S0 S1 S2 S3 S4 S5 S6 )

( S0 S1 S2 S3 S5 ) ( S4 S6 )

( S0 S3 S5 ) ( S1 S2 ) ( S4 S6 )

( S0 ) ( S3 S5 ) ( S1 S2 ) ( S4 S6 )

S1 is equivalent to S2


S3 is equivalent to S5

S4 is equivalent to S6

# Minimized FSM

- State minimized sequence detector for 010 or 110

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1'	S1'	0	0
0 + 1	S1'	S3'	S4'	0	0
X0	S3'	S0	S0	0	0
X1	S4'	S0	S0	1	0

 

# Row Matching Method


- Straightforward to understand and easy to implement
- Problem: does not yield the most reduced state table!

Example: 3 State Odd Parity Checker

Present State	Next State		Output
	X=0	X=1	
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	0
S <sub>1</sub>	S <sub>1</sub>	S <sub>2</sub>	1
S <sub>2</sub>	S <sub>2</sub>	S <sub>1</sub>	0

We know S<sub>0</sub>, S<sub>2</sub> can be combined

 
**No way to combine states S<sub>0</sub> and S<sub>2</sub> based on Next State Criterion!**



 
# Implication Chart Method

- Enumerate all possible combinations of states taken two at a time

Next States  
Under all  
Input  
Combinations



 Naive Data Structure:  
 $X_{ij}$  will be the same as  $X_{ji}$   
Also, can eliminate the diagonal



Implication Chart

# Implication Chart Method

Fill in the Implication Chart

Entry  $X_{ij}$  : Row is  $S_i$ , Column is  $S_j$

**$S_i$  is equivalent to  $S_j$**  if outputs are the same and next states are equivalent

$X_{ij}$  contains the next states of  $S_i$ ,  $S_j$  which must be equivalent if  $S_i$  and  $S_j$  are equivalent


If  $S_i$ ,  $S_j$  have different output behavior, then  $X_{ij}$  is crossed out

Example:


$S_0$  transitions to  $S_1$  on 0,  $S_2$  on 1;

$S_1$  transitions to  $S_3$  on 0,  $S_4$  on 1;

 So square  $X_{\langle 0,1 \rangle}$  contains entries  $S_1$ - $S_3$  (transition on zero)  
 $S_2$ - $S_4$  (transition on one)



# Implication Chart Method

 

Input Sequence		Present State		Next State		Output	
				X=0	X=1	X=0	X=1
Reset		S <sub>0</sub>		S <sub>1</sub>	S <sub>2</sub>	0	0
0		S <sub>1</sub>		S <sub>3</sub>	S <sub>4</sub>	0	0
1		S <sub>2</sub>		S <sub>5</sub>	S <sub>6</sub>	0	0
00		S <sub>3</sub>		S <sub>0</sub>	S <sub>0</sub>	0	0
01		S <sub>4</sub>		S <sub>0</sub>	S <sub>0</sub>	1	0
10		S <sub>5</sub>		S <sub>0</sub>	S <sub>0</sub>	0	0
11		S <sub>6</sub>		S <sub>0</sub>	S <sub>0</sub>	1	0

# Implication Chart Method


**Results of First Marking Pass**

**Second Pass (Adds No New Information)**

**S3 and S5 are equivalent**

**S4 and S6 are equivalent**

**This implies that S1 and S2 are too!**

 


Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	$S_0$	$S'_1$	$S'_1$	0	0
0 or 1	$S'_1$	$S'_3$	$S'_4$	0	0
00 or 10	$S'_3$	$S_0$	$S_0$	0	0
01 or 11	$S'_4$	$S_0$	$S_0$	1	0

**Reduced State  
Transition Table**



# More Complex State Minimization

- Multiple input example

 

inputs here


present state	00	01	10	11	output
S0	S0	S1	S2	S3	1
S1	S0	S3	S1	S4	0
S2	S1	S3	S2	S4	1
S3	S1	S0	S4	S5	0
S4	S0	S1	S2	S5	1
S5	S1	S4	S0	S5	0

symbolic state transition table

# Minimized FSM
 
## ■ Implication chart method

- ◆ cross out incompatible states based on outputs
- ◆ then cross out more cells if indexed chart entries are already crossed out



present state	next state				output
	00	01	10	11	
S0'	S0'	S1	S2	S3'	1
S1	S0'	S3'	S1	S3'	0
S2	S1	S3'	S2	S0'	1
S3'	S1	S0'	S0'	S3'	0


minimized state table  
(S0==S4) (S3==S5)

# Odd Parity EX

- Example: 3 State Odd Parity Checker

Present State	Next State		Output
	X=0	X=1	
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	0
S <sub>1</sub>	S <sub>1</sub>	S <sub>2</sub>	1
S <sub>2</sub>	S <sub>2</sub>	S <sub>1</sub>	0

 **S<sub>0</sub>, S<sub>2</sub> cannot be combined by using row matching method**




# Implication Chart Method

## ■ Example: 3 State Odd Parity Checker

Does the method solve the problem with the odd parity checker.

Implication Chart


 


**$S_0$  is equivalent to  $S_2$   
since nothing contradicts this assertion!**

# Minimized FSM

## ■ Example: 3 State Odd Parity Checker

Reduced State  
Diagram

  


# Implication Chart Summary

---

1. *Construct implication chart, one square for each combination of states taken two at a time*
2. *Square labeled  $S_i, S_j$ , if outputs differ, then square gets "X". Otherwise write down implied state pairs for all input combinations*
3. *Advance through chart top-to-bottom and left-to-right. If square  $S_i, S_j$  contains next state pair  $S_m, S_n$  and that pair labels a square already labeled "X", then  $S_i, S_j$  is labeled "X".*
4. *Continue executing Step 3 until no new squares are marked with "X".*
5. *For each remaining unmarked square  $S_i, S_j$ , then  $S_i$  and  $S_j$  are equivalent.*

# Minimizing States May Not Yield Best Circuit

 - Example: edge detector - outputs 1 when last two input changes from 0 to 1




X	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>1</sub> <sup>+</sup>	Q <sub>0</sub> <sup>+</sup>
0	0	0	0	0
0	0	1	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	1	1	1
–	1	0	0	0

$$Q_1^+ = X \text{ (} Q_1 \text{ xor } Q_0 \text{)}$$


$$Q_0^+ = X \text{ } Q_1' \text{ } Q_0'$$
 
# Another Implementation of Edge Detector

- "Ad hoc" solution - not minimal but cheap and fast


 
$$\begin{aligned}Q_1^+ &= Q_0 \\Q_0^+ &= X \\O_{ut} &= Q_1^+ Q_0\end{aligned}$$





# State Assignment

---

- Choose bit vectors to assign to each “symbolic” state
  - ◆ for  $n$  state bits for  $m$  states there are  $2^n! / (2^n - m)!$   
[ $\log n \leq m \leq 2^n$ ]
  - ◆  $2^n$  codes possible for 1st state,  $2^n - 1$  for 2nd,  $2^n - 2$  for 3rd, ...
  - ◆ huge number even for small values of  $n$  and  $m$ 
    - intractable for state machines of any size
    - heuristics are necessary for practical solutions
  - ◆ optimize some metrics for the combinational logic
    - size (amount of logic and number of FFs)
    - speed (depth of logic and fanout)
    - dependencies (decomposition)


# State Assignment Strategies

---

- Possible strategies
  - ◆ *sequential* – just number states as they appear in the state table
  - ◆ *random* – pick random codes
  - ◆ *one-hot* – use as many state bits as there are states (bit=1 → state)
  - ◆ *output* – use outputs to help encode states
  - ◆ *heuristic* – rules of thumb that seem to work in most cases
- No guarantee of optimality – another intractable problem
 
# Pencil & Paper Heuristic Methods

- **State Maps:** similar in concept to K-maps  
If state X transitions to state Y, then assign "close" assignments to X and Y



State Name	Assignment		
	$Q_2$	$Q_1$	$Q_0$
$S_0$	0	0	0
$S_1$	1	0	1
$S_2$	1	1	1
$S_3$	0	1	0
$S_4$	0	1	1

Assignment

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	$S_0$		$S_4$	$S_3$
1		$S_1$	$S_2$	

State Map

State Name	Assignment		
	$Q_2$	$Q_1$	$Q_0$
$S_0$	0	0	0
$S_1$	0	0	1
$S_2$	0	1	0
$S_3$	0	1	1
$S_4$	1	1	1

Assignment

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	$S_0$	$S_1$	$S_3$	$S_2$
1			$S_4$	

State Map

# Pencil & Paper Heuristic Methods

## Minimum Bit Distance Criterion

<i>Transition</i>	<i>First Assignment Bit Changes</i>	<i>Second Assignment Bit Changes</i>
S0 to S1:	2	1
S0 to S2:	3	1
S1 to S3:	3	1
S2 to S3:	2	1
S3 to S4:	1	1
S4 to S1:	2	2
	<hr/>	<hr/>
	13	7

Traffic light controller: HG = 00, HY = 01, FG = 11, FY = 10  
yields minimum distance encoding but not best assignment!


# Heuristics for State Assignment

- Adjacent codes to states that share a common next state

- ◆ group 1's in next state map

I	Q	Q <sup>+</sup>	O
i	a	c	j
i	b	c	k

$$c = i * a + i * b$$

 


- Adjacent codes to states that share a common ancestor state

- ◆ group 1's in next state map

I	Q	Q <sup>+</sup>	O
i	a	b	j
k	a	c	l

$$b = i * a$$

$$c = k * a$$

 

- Adjacent codes to states that have a common output behavior


- ◆ group 1's in output map

I	Q	Q <sup>+</sup>	O
i	a	b	j
i	c	d	j

$$j = i * a + i * c$$


$$b = i * a$$

$$d = i * c$$

 

# Heuristics for State Assignment

## ■ Example: 3-bit Sequence Detector

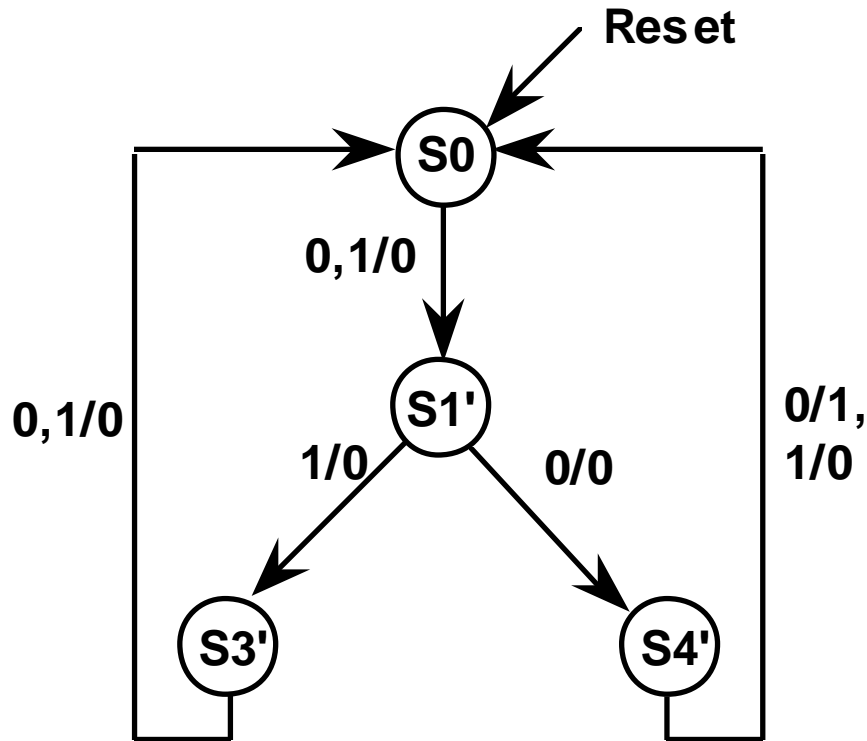

**Highest Priority: (S3', S4')**

**Medium Priority: (S3', S4')**

**Lowest Priority:**

0/0: (S0, S1', S3')

1/0: (S0, S1', S3', S4')

# Heuristics for State Assignment

## ■ Example: 3-bit Sequence Detector

$Q_0 \backslash Q_1$	0	1
0	$S_0$	$S_1'$
1	$S_3'$	$S_4'$

Reset State = 00


Highest Priority Adjacency

$Q_0 \backslash Q_1$	0	1
0	$S_0$	$S_3'$
1	$S_1'$	$S_4'$

Not much difference in these two assignments
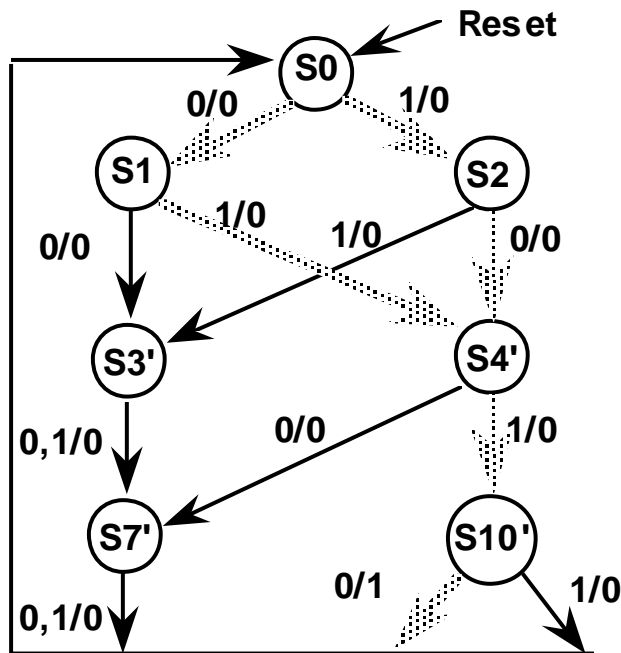
# Heuristics for State Assignment

- Another Example: 4 bit String Recognizer



**Highest Priority: (S3', S4'), (S7', S10')**

**Medium Priority:**  
(S1, S2), 2x(S3', S4'), (S7', S10')

**Lowest Priority:**  
0/0: (S0, S1, S2, S3', S4', S7')  
1/0: (S0, S1, S2, S3', S4', S7')



# Heuristics for State Assignment

## ■ Another Example: 4 bit String Recognizer

State Map

Q1 \ Q0	00	01	11	10
0	S0			
1				

Q1 \ Q0	00	01	11	10
0	S0		S3'	
1			S4'	

Q1 \ Q0	00	01	11	10
0	S0		S3'	S7'
1			S4'	S10'

Q1 \ Q0	00	01	11	10
0	S0	S1	S3'	S7'
1		S2	S4'	S10'

(a)

Q1 \ Q0	00	01	11	10
0	S0			
1				

Q1 \ Q0	00	01	11	10
0	S0			
1	S7'			S10'

Q1 \ Q0	00	01	11	10
0	S0		S3'	
1	S7'		S4'	S10'

Q1 \ Q0	00	01	11	10
0	S0	S1	S3'	
1	S7'	S2	S4'	S10'


(b)

00 = Reset = S0

(S3', S4'), (S7', S10')  
placed adjacently,  
Then (S1, S2)

# Heuristics for State Assignment
 
## ■ Effect of Adjacencies on Next State Map



**First encoding exhibits a better clustering of 1's in the next state map**



# General Approach to Heuristic State Assignment

---

- All current methods are variants of this
  - ◆ 1) determine which states “attract” each other (weighted pairs)
  - ◆ 2) generate constraints on codes (which should be in same cube)
  - ◆ 3) place codes on Boolean cube so as to maximize constraints satisfied (weighted sum)
- Different weights make sense depending on whether we are optimizing for two-level or multi-level forms
  
# Why Partition ?

- Mapping FSMs onto programmable logic components:
  - limited number of input/output pins
  - limited number of product terms or other programmable resources



***Example of Input/Output Partitioning:***


**5 outputs depend on 15 inputs**

**5 outputs depend on different overlapping set of 15 inputs**

# Finite State Machine Partitioning

## *Introduction of Idle States*



**Before Partitioning**

 

# Finite State Machine Partitioning

## *Introduction of Idle States*


After Partitioning

  


# Finite State Machine Partitioning
 
## *Rules for Partitioning*

**Rule #1:** Source State Transformation; SA is the Idle State



 
**Rule #2:** Destination State Transformation




# Finite State Machine Partitioning

## Rules for Partitioning
 
### Rule #3: Multiple Transitions with Same Source or Destination



 
### Rule #4: Hold Condition for Idle State





# Finite State Machine Partitioning

## *Another Example*

 


**6 state up/down counter**

**building block has 2 FFs + combinational logic**

# Finite State Machine Partitioning

## 6 State Up/Down Counter

 

Introduction of the two idle state SA, SB

Count sequence S0, S1, S2, S3, S4, S5:

S2 goes to SA and holds, leaves after S5

S5 goes to SB and holds, leaves after S2

Down sequence is similar

# Sequential Logic Optimization Summary

---

- State minimization
  - ◆ straightforward in fully-specified machines
  - ◆ computationally intractable, in general (with don't cares)
- State assignment
  - ◆ many heuristics
  - ◆ best-of-10-random just as good or better for most machines
  - ◆ output encoding can be attractive (especially for PAL implementations)